

# TLE987x/6x

## Hardware Design Guideline

### Application Note

#### About this document

##### Scope and purpose

The Embedded Power ICs integrate on a single-die a 32-bit microcontroller, non-volatile flash memory, analog and mixed signal peripherals, communication interfaces along with the driving stages needed for either relay, half-bridge or full-bridge DC and BLDC motor applications. The Embedded Power is an industry standard microcontroller processor (32-bit Arm® Cortex®-M core) in leading edge automotive qualified technology (130 nm Smart Power process).

The TLE987x/6x family addresses a wide range of smart 3-phase (TLE987x) and 2-phase (TLE986x) brushless DC motor control applications, like engine cooling fans, auxiliary pumps and fans, sunroof, window lift.

This Application Note provides the reader with detailed descriptions about hardware design guidelines for the external components, using the TLE987x/6x devices.

##### Intended audience

This Application Note is addressed to embedded hardware and software developers, who are going to use the TLE987x/6x devices to design ECU (Electronic Control Unit) for BLDC/PMSM motor control applications.

---

\* Arm and Cortex are registered trademarks of Arm Limited, UK

## Table of contents

	<b>About this document</b> .....	<b>1</b>
	<b>Table of contents</b> .....	<b>2</b>
<b>1</b>	<b>TLE987x/6x family</b> .....	<b>4</b>
1.1	TLE987x/6x block diagram .....	4
1.2	TLE987x/6x family comparison .....	5
1.3	Application information .....	6
<b>2</b>	<b>Power Supply Generation Unit (PGU)</b> .....	<b>9</b>
2.1	Block diagram .....	9
2.2	Input voltage VS, preregulator VPRE and reference voltage VAREF .....	10
2.3	VDDP: voltage regulator 5.0 V .....	12
2.4	VDDC: voltage regulator 1.5 V .....	12
2.5	VDDEXT: voltage regulator 5.0 V .....	13
<b>3</b>	<b>Clock Generation Unit (CGU)</b> .....	<b>14</b>
3.1	Block diagram .....	14
3.2	External Input Clock mode .....	15
3.3	External Crystal mode .....	16
3.4	Layout recommendations .....	17
<b>4</b>	<b>LIN transceiver</b> .....	<b>18</b>
<b>5</b>	<b>High-voltage monitor input</b> .....	<b>19</b>
5.1	Block diagram .....	19
5.2	Application hints .....	19
<b>6</b>	<b>Bridge driver (excluding charge pump)</b> .....	<b>20</b>
6.1	Application diagram .....	20
6.2	External components .....	21
6.2.1	Overview .....	21
6.2.2	Details .....	21
6.2.2.1	Gate resistor .....	21
6.2.2.2	Gate-to-source resistor .....	21
6.2.2.3	Gate-to-source capacitor .....	22
6.2.2.4	Gate-to-drain capacitor .....	22
6.2.2.5	DC link capacitors .....	22
6.2.2.6	Snubber .....	23
6.2.2.7	EMC filter capacitor at the SHx pin .....	23
6.2.2.8	Low-pass filter at the VDH pin .....	23
6.2.2.9	Protection diode at the SHx pin .....	23
<b>7</b>	<b>Charge pump</b> .....	<b>24</b>
7.1	Application diagram .....	24
7.2	Charge pump: how it works .....	24
7.2.1	ICP load current calculation .....	27
7.3	Charge pump external capacitors design .....	32
7.3.1	Calculation example .....	33
<b>8</b>	<b>Current Sense Amplifier</b> .....	<b>34</b>
8.1	Block diagram .....	34

8.2	Functional description .....	35
8.2.1	DC characteristics .....	35
8.2.2	AC characteristics .....	37
8.3	Application hints .....	40
8.3.1	Shunt resistor selection .....	40
8.3.2	Filter network selection .....	44
8.3.3	Conclusion .....	47
<b>9</b>	<b>SWD (Serial Wire Debug) interface circuitry .....</b>	<b>49</b>
9.1	Description of the SWD interface .....	49
9.2	Implementing an SWD interface connection to TLE987x/6x .....	49
<b>10</b>	<b>Unused pins .....</b>	<b>50</b>
<b>11</b>	<b>EMI recommendation .....</b>	<b>51</b>
11.1	Recommendations for optimized PCB layout .....	51
11.1.1	Placement of the connectors .....	51
11.1.2	Floor-planning the PCB .....	51
11.1.3	Routing the power supply traces .....	52
11.1.4	Number of PCB layers .....	53
<b>12</b>	<b>Specific PCB design rules for microcontrollers with bridge drivers .....</b>	<b>54</b>
12.1	Input filter .....	55
12.1.1	GND concept .....	56
12.2	Bypass capacitors .....	59
12.3	Layout recommendation for a 3-phase motor bridge .....	59
12.4	Layout recommendation for a current sense shunt .....	61
	<b>Revision history .....</b>	<b>62</b>

## 1 TLE987x/6x family


The TLE987x/6x is a single-chip 3-phase/2-phase motor driver that integrates the industry standard Arm® Cortex®-M3 core, enabling the implementation of advanced motor control algorithms such as field-oriented control.

It includes six (TLE987x) or four (TLE986x) fully integrated NFET drivers optimized to drive a 3-phase or 2-phase motor via external power NFETs, a charge pump enabling low-voltage operation, and programmable current along with current slope control for optimized EMC behavior. Its peripheral set includes a current sense amplifier, a successive approximation ADC optionally synchronized with the Capture and Compare Unit for PWM control, and 16-bit timers. A LIN transceiver to enable communication with the device and several general-purpose I/O units are also integrated. It includes an on-chip linear voltage regulator to supply external loads.

In addition to other products of the TLE987x product family, TLE9879-2QXA40 incorporates two 14-bit Sigma-Delta ADCs, which provide a reliable interface for an external GMR/TMR sensor.

### 1.1 TLE987x/6x block diagram

**Figure 1** shows the block diagram of the TLE987x. The TLE986x differs from the TLE987x since it integrates two bridge drivers, instead of three.

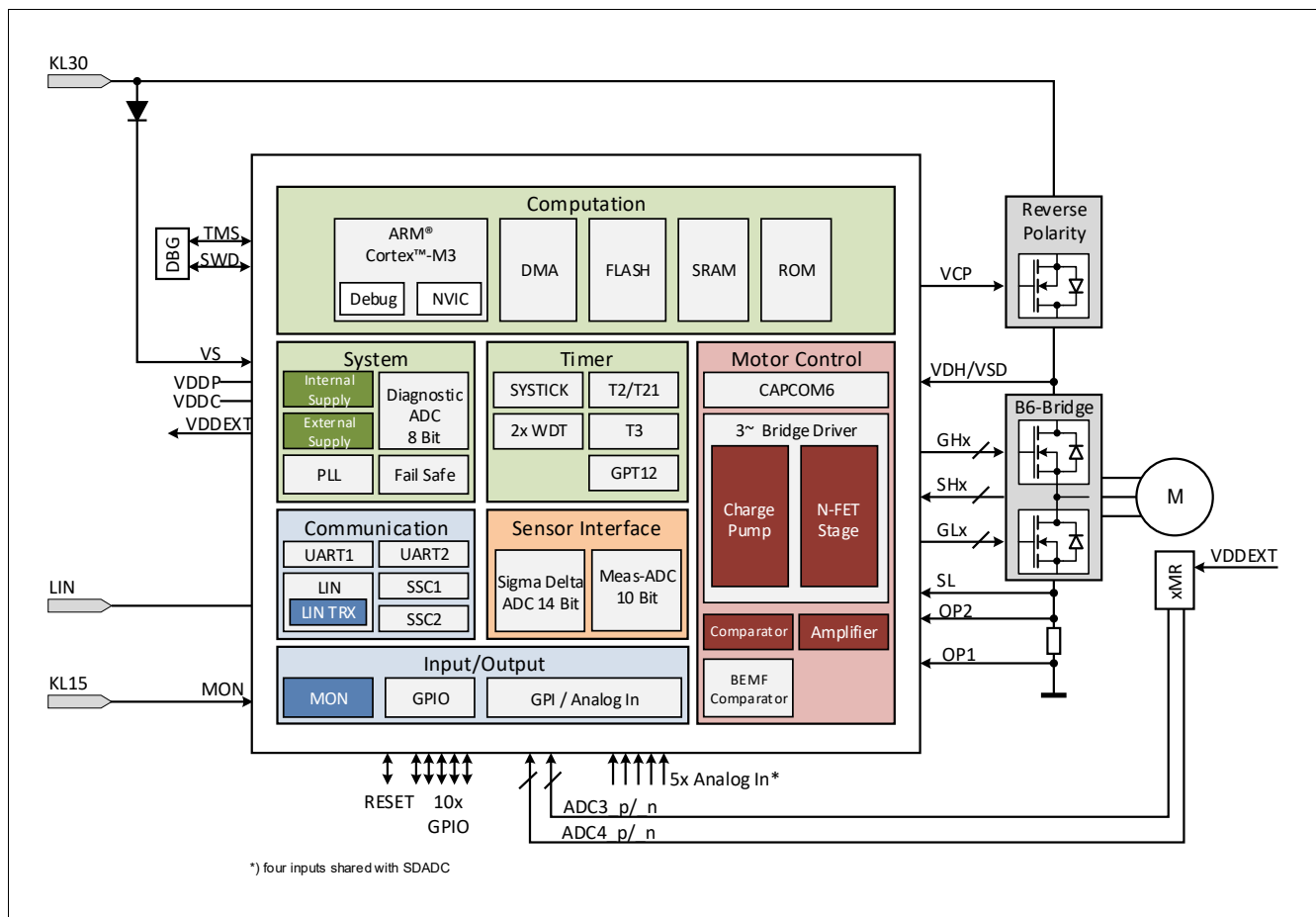

**Figure 1 Block diagram of the TLE987x**

In the variants with the Sigma-Delta ADCs, the XTAL1 and XTAL2 pins for the external oscillator are not available.

**TLE987x/6x family**

## 1.2 TLE987x/6x family comparison

**Table 1** and **Table 2** list the variants available in the TLE987x/6x product family. The versions with the Sigma-Delta ADCs are named using the scheme TLE987x-2Qx.

**Table 1 TLE987x product family variants**


Product	Package	Flash	RAM	Max. operating frequency	Interfaces	T <sub>j</sub> max
TLE9871QXA20	VQFN-48	36 kByte	3 kByte	24 MHz	PWM	150°C
TLE9873QXW40	VQFN-48	48 kByte	3 kByte	40 MHz	PWM + LIN	175°C
TLE9877QXA20	VQFN-48	64 kByte	6 kByte	24 MHz	PWM + LIN	150°C
TLE9877QXA40	VQFN-48	64 kByte	6 kByte	40 MHz	PWM + LIN	150°C
TLE9877QXW40	VQFN-48	64 kByte	6 kByte	40 MHz	PWM + LIN	175°C
TLE9877QTW40	TQFP-48	64 kByte	6 kByte	40 MHz	PWM + LIN	175°C
TLE9879QXA20	VQFN-48	128 kByte	6 kByte	24 MHz	PWM + LIN	150°C
TLE9879-2QXA40	VQFN-48	128 kByte	6 kByte	40 MHz	PWM + LIN	150°C
TLE9879QXA40	VQFN-48	128 kByte	6 kByte	40 MHz	PWM + LIN	150°C
TLE9879QXW40	VQFN-48	128 kByte	6 kByte	40 MHz	PWM + LIN	175°C
TLE9879QTW40	TQFP-48	128 kByte	6 kByte	40 MHz	PWM + LIN	175°C
TLE9872-2QXA40	VQFN-48	256 kByte	8 kByte	40 MHz	PWM + LIN	150°C
TLE9872QXA40	VQFN-48	256 kByte	8 kByte	40 MHz	PWM + LIN	150°C
TLE9872QTW40	TQFP-48	256 kByte	8 kByte	40 MHz	PWM + LIN	175°C

**Table 2 TLE986x product family variants**


Product	Package	Flash	RAM	Max. operating frequency	Interfaces	T <sub>j</sub> max
TLE9861QXA20	VQFN-48	36 kByte	3 kByte	24 MHz	PWM	150°C
TLE9867QXA40	VQFN-48	64 kByte	6 kByte	40 MHz	PWM + LIN	150°C
TLE9867QXA20	VQFN-48	64 kByte	6 kByte	24 MHz	PWM + LIN	150°C
TLE9867QXW20	VQFN-48	64 kByte	6 kByte	24 MHz	PWM + LIN	175°C
TLE9868QXB20	VQFN-48	128 kByte	4 kByte	20 MHz	PWM + LIN	150°C
TLE9869QXA20	VQFN-48	128 kByte	6 kByte	24 MHz	PWM + LIN	150°C
TLE9862QXA40	VQFN-48	256 kByte	8 kByte	40 MHz	PWM + LIN	150°C

### 1.3 Application information

**Figure 2** and **Figure 3** show the TLE987x in an electric-drive application setup controlling a BLDC motor. This is a very simplified example of an application circuit and bill of materials. The function must be verified in the actual application. The TLE986x differs from the TLE987x since it has two bridge drivers, instead of three.

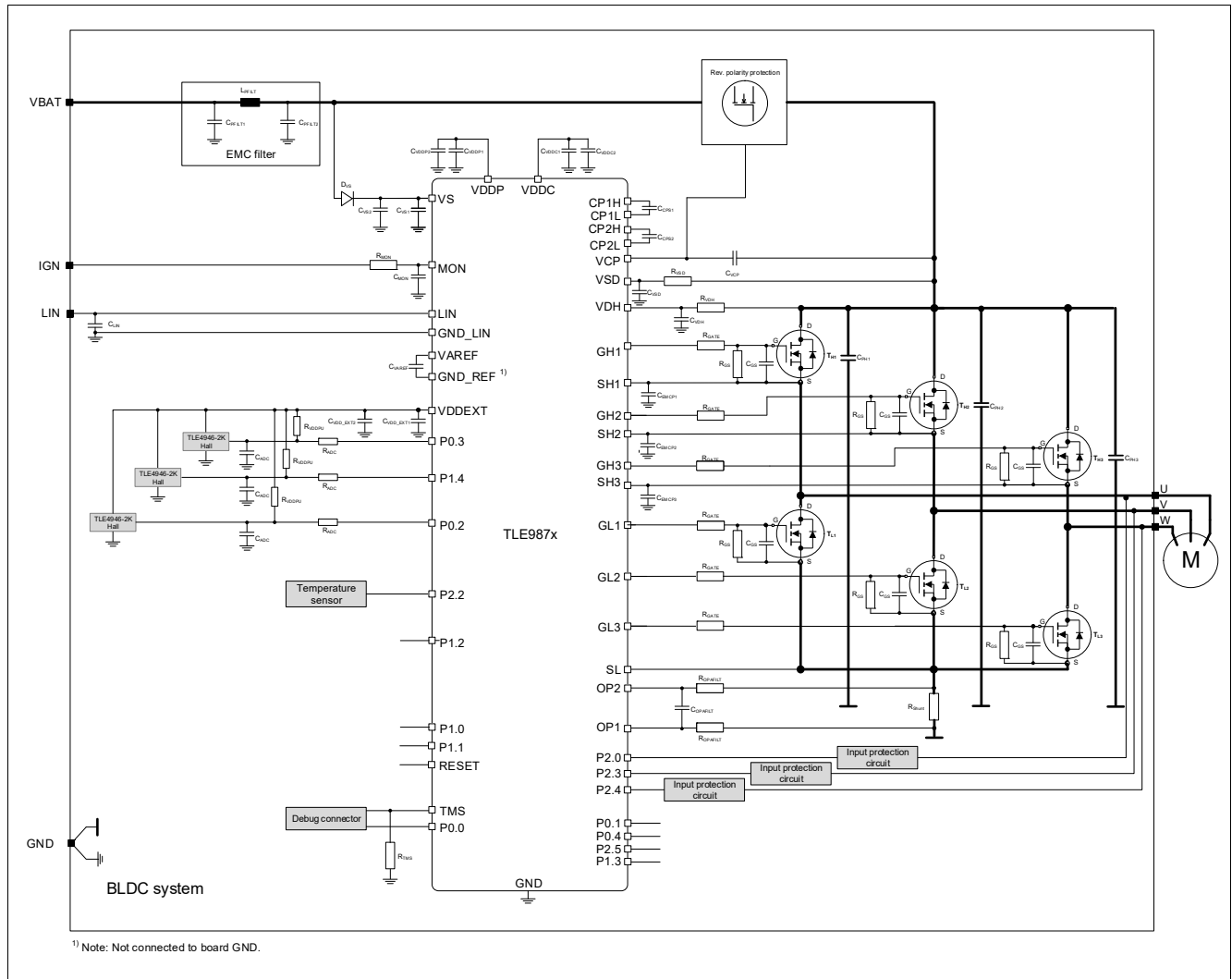

**Figure 2 Application schematic example for TLE987x**

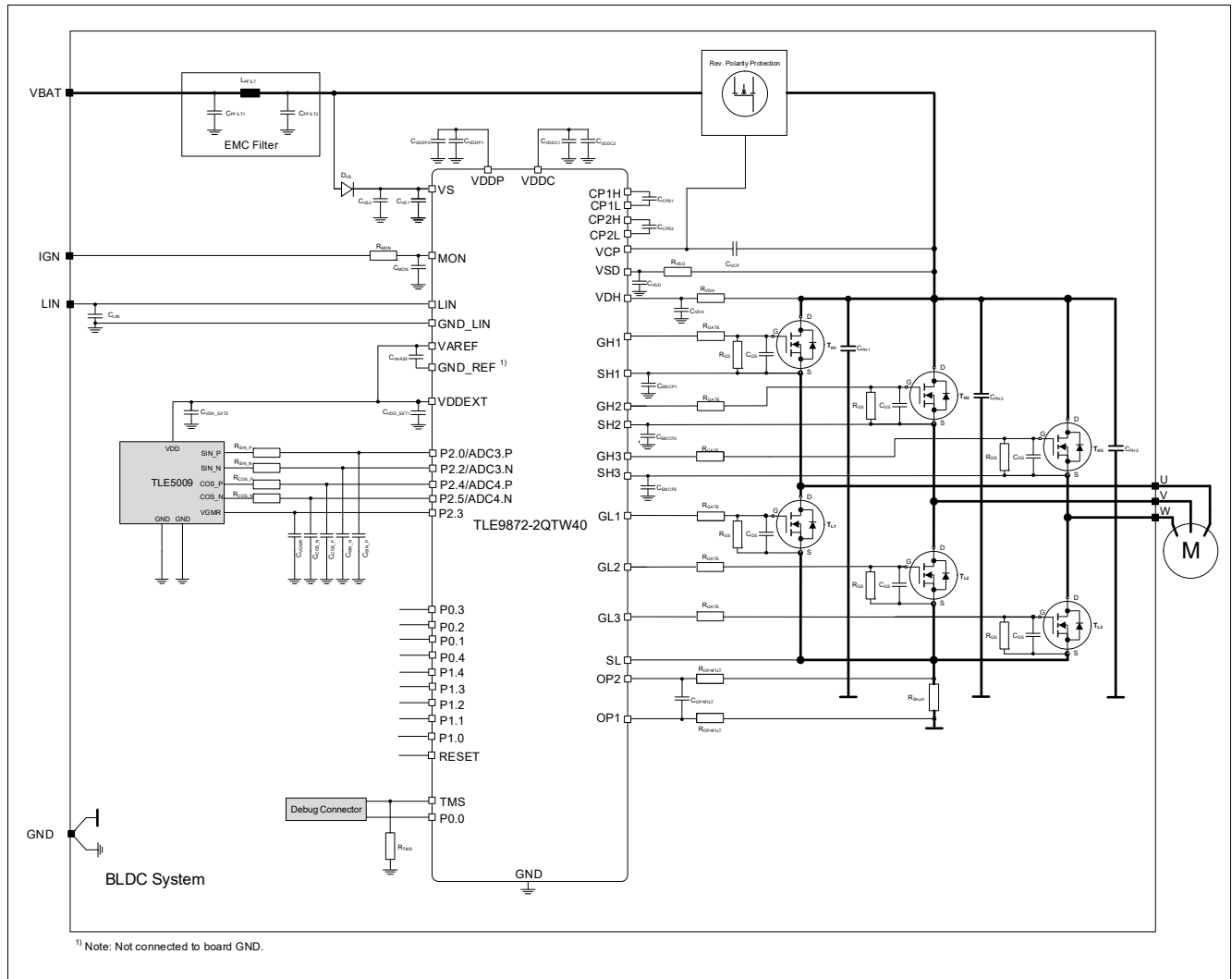

**Figure 3 Application schematic example for TLE987x-2QX**

**Table 3 External components (BOM)**

Symbol	Function	Component (typical)
$C_{VS1}$	Filter capacitor at VS pin (TLE987x supply)	$\geq 100 \text{ nF}$
$C_{VS2}$	Bulk capacitor at VS pin (TLE987x supply)	$> 2.2 \mu\text{F}$
$C_{VDDP}$	Output capacitor at VDDP pin (voltage regulator)	$470 \text{ nF} + 100 \text{ nF}$
$C_{VDD\_EXT}$	Output capacitor at VDD_EXT pin (voltage regulator)	$100 \text{ nF}$
$C_{VDDC}$	Output capacitor at VDDC pin (voltage regulator)	$470 \text{ nF} + 100 \text{ nF}$
$C_{VAREF}$	Filter capacitor at VAREF pin (analog reference)	$100 \text{ nF}$
$C_{LIN}$	Filter capacitor at LIN pin	$220 \text{ pF}$
$C_{VSD}$	Filter capacitor at VSD pin (charge pump supply)	$1 \mu\text{F}$
$C_{CPS1}$	Charge pump capacitor (first stage flying capacitor)	$220 \text{ nF}$
$C_{CPS2}$	Charge pump capacitor (second stage flying capacitor)	$220 \text{ nF}$
$C_{VCP}$	Charge pump capacitor (output bulk capacitor)	$470 \text{ nF}$
$C_{MON}$	Filter capacitor at MON pin (high-voltage monitor input)	$10 \text{ nF}$

**Table 3 External components (BOM)**

<b>Symbol</b>	<b>Function</b>	<b>Component (typical)</b>
$C_{VDH}$	Filter capacitor at VDH pin (drain high-side MOSFET driver)	3.3 nF
$C_{PH1}$	Filter capacitor at drain high-side FET (phase U)	220 $\mu$ F
$C_{PH2}$	Filter capacitor at drain high-side FET (phase V)	220 $\mu$ F
$C_{PH3}$	Filter capacitor at drain high-side FET (phase W)	220 $\mu$ F
$C_{OPAFILT}$	Filter capacitor at OP1 and OP2 pins (CSA inputs)	application related
$C_{EMCP1}$	Filter capacitor at SH1 pin (source high-side FET 1)	1 nF
$C_{EMCP2}$	Filter capacitor at SH2 pin (source high-side FET 2)	1 nF
$C_{EMCP3}$	Filter capacitor at SH3 pin (source high-side FET 3)	1 nF
$C_{PFILT1}, C_{PFILT2}$	Filter capacitors of the input $\pi$ filter	application related
$D_{VS}$	Reverse-polarity protection diode	application related
$L_{PFILT}$	Filter inductor of the input $\pi$ filter	application related
$R_{MON}$	Filter resistor at MON pin	3.9 k $\Omega$
$R_{VSD}$	Filter resistor at VSD pin	2 $\Omega$
$R_{VDH}$	Filter resistor at VDH pin	1 k $\Omega$
$R_{GATE}$	FET Gate resistor	2 $\Omega$
$R_{OPAFILT}$	Filter resistor at OP1 and OP2 pins (CSA inputs)	application related
$R_{Shunt}$	Shunt resistor	application related
$R_{GS}$	FET gate-source resistor	application related
$C_{GS}$	FET gate-source resistor	application related
$R_{VDDPU}$	Pull-up resistor for Hall sensor	application related
$R_{ADC}$	Filter resistor at ADC1 input	application related
$C_{ADC}$	Filter capacitor at ADC1 input	application related
$R_{TMS}$	Pull-down resistor at TMS pin (test mode select)	optional
$R_{SIN\_P} / R_{SIN\_N}$	Filter resistors at ADC3 input pins (Sigma-Delta version)	10 k $\Omega$
$R_{COS\_P} / R_{COS\_N}$	Filter resistors at ADC4 input pins (Sigma-Delta version)	10 k $\Omega$
$C_{SIN\_P} / C_{SIN\_N}$	Filter capacitors at ADC3 input pins (Sigma-Delta version)	68 nF
$C_{COS\_P} / C_{COS\_N}$	Filter capacitors at ADC4 input pins (Sigma-Delta version)	68 nF
$C_{VGMR}$	Filter capacitor at GPIO input pin (GMR bridge voltage)	4.7 nF


## Power Supply Generation Unit (PGU)

## 2 Power Supply Generation Unit (PGU)

The Power Management Unit (PMU) generates all required voltage supplies for the embedded MCU (VDDC, VDDP) as well as for the external supply (VDDEXT).

### 2.1 Block diagram

**Figure 4** shows the structure of the PMU, where the Power Supply Generation Unit (PGU) includes the voltage regulators for the pad supply (VDDP), the core supply (VDDC) and in cascade the voltage regulator to supply external circuits (VDDEXT).

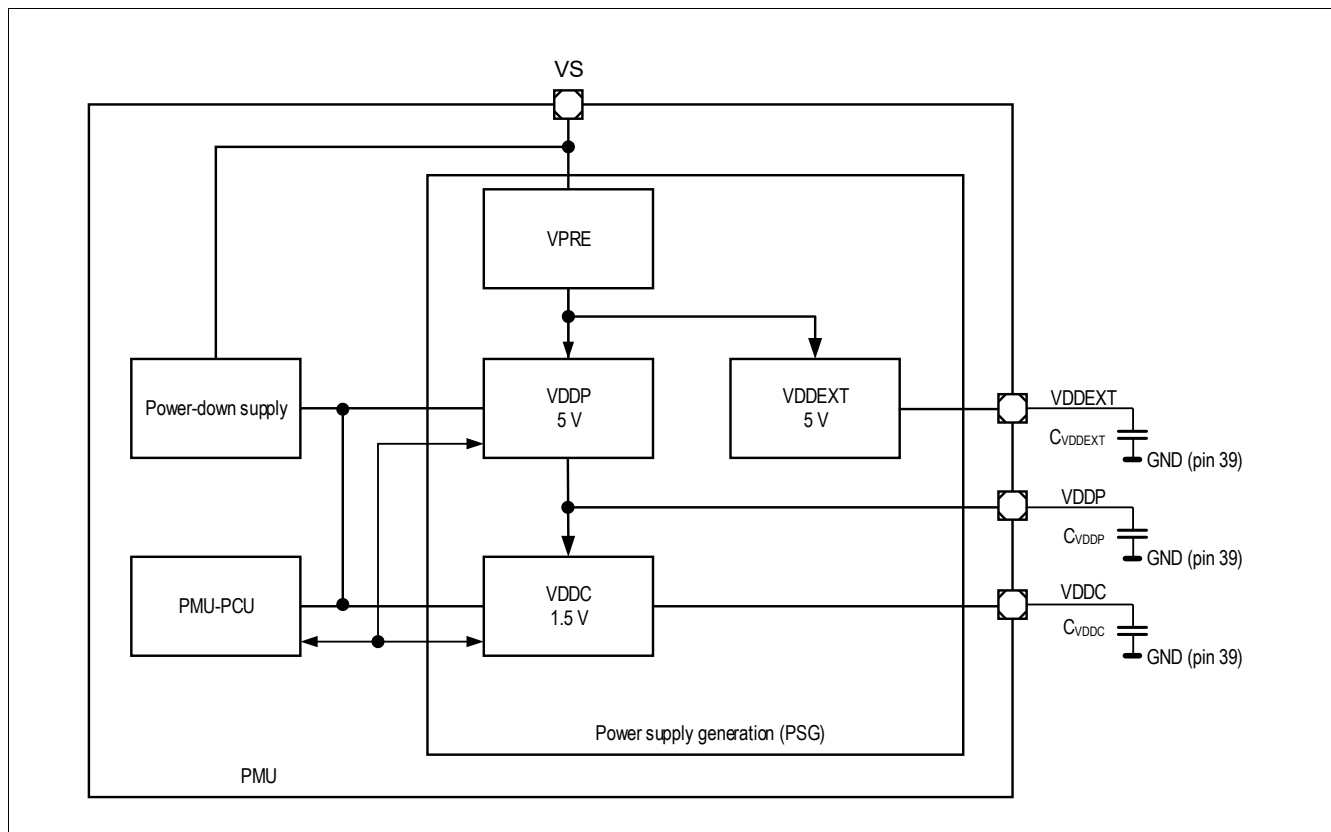

**Figure 4** PMU block diagram including the PGU (called PSG in the figure)


The submodules of the PMU are:

- **Power-down supply:** independent analog supply voltage generation for the Power Control Unit logic, for the VDDP regulator, and for the VDDC regulator.
- **VPRE:** analog supply voltage preregulator. This regulator reduces the power dissipation for the following regulator stages.
- **VDDP:** 5-V digital voltage regulator for internal modules and all GPIOs.
- **VDDC:** 1.5-V digital voltage regulator for internal microcontroller modules and core logic.
- **VDDEXT:** 5-V digital voltage regulator for external circuits.
- **PMU-PCU:** Power Control Unit responsible supervising and controlling the 5-V regulator and the 1.5-V regulator.

## 2.2 Input voltage VS, preregulator VPRE and reference voltage VAREF

The VS input is the supply voltage of the VPRE preregulator and the power-down supply. VS is derived from the battery voltage (VBAT) and, if necessary, it must be protected against reverse battery connections using a diode ( $D_{VS}$ ) in series to VBAT. The Infineon Application Note “[Reverse Polarity Protection for Embedded Power ICs](#)” provides a detailed description of the complete circuit for reverse battery protection.

The  $C_{VS1}$  and  $C_{VS2}$  capacitors, placed before the VS pin, respectively act as a filter and a bulk capacitor for the TLE987x/6x power supply.

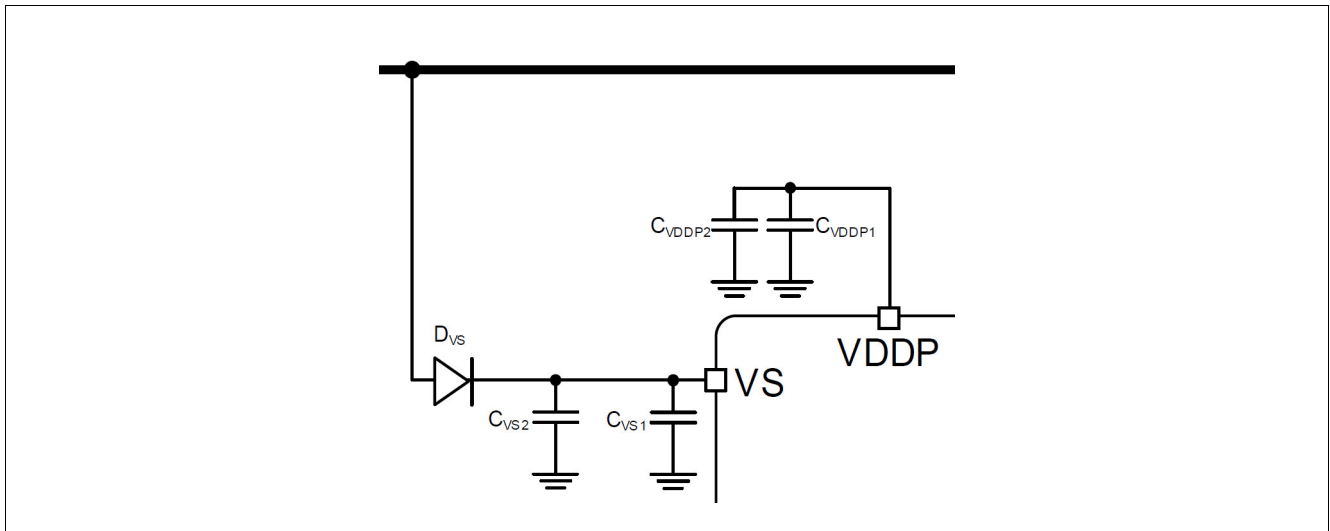

**Figure 5 Components before the VS pin**

If data should be saved in the flash memory at power down, the selection of  $C_{VS2}$  should be done in order to ensure that operations, modifying the content of the flash are never interrupted (for example, in case of power loss). Assuming that at power loss detection all the peripherals are disabled, power is still consumed by the MCU and flash erase or write operations. The size of  $C_{VS2}$  can be calculated using the equation:

(2.1)

$$C_{VS2} \geq \frac{I \times t}{\Delta V}$$

where:

- $I$  is the current consumption at power down
- $t$  is the time for which the MCU should stay active after power down
- $\Delta V$  is the difference between the voltage at the time when the loss of power is detected and the reset voltage of the MCU

As reported in the TLE987x/6x product datasheets, the supply voltage in Active mode with reduced functionality (full MCU and flash operation) has a minimum value of 3 V. For example, assuming 10 mA as the current consumption during power down, 20 ms as the time needed to save the flash content, and 3 V as  $\Delta V$ , then  $C_{VS2}$  must be at least 67  $\mu\text{F}$ .

**Table 4** shows the recommended components to connect before the VS pin.

**Power Supply Generation Unit (PGU)**

**Table 4**      **Component selection for the VS pin**

Symbol	Function	Recommended component
$D_{VS}$	Diode for reverse battery protection	<b>PN or Schottky diode</b> Voltage and current ratings defined according to the application
$C_{VS1}$	Filter capacitor	Ceramic capacitor <b>Min. value 100 nF</b> Voltage rating and dielectric type defined according to the application
$C_{VS2}$	Bulk capacitor	Electrolytic capacitor <b>Min. value 2.2 <math>\mu</math>F</b> Value, voltage rating, and temperature defined according to the application

The voltage preregulator **VPRE** generates an internal voltage of about 7 V from the VS input. The output voltage of VPRE is used as input for the internal voltage regulators, and it is not accessible externally.

The  $I_{PRE}$  current is shared between the VDDP and VDDEXT voltage regulators. The table summarizes the maximum currents allowed for each voltage regulator.

Linear regulator	Maximum current
VPRE	$I_{PRE} = 110 \text{ mA}$ $I_{PRE} = I_{DDP} + I_{DDEXT}$
VDDP	$I_{DDP} = 90 \text{ mA}$ $I_{DDEXT} = 20 \text{ mA}$
VDDEXT	$I_{DDEXT} = 40 \text{ mA}$ $I_{DDP} = 70 \text{ mA}$
VDDC	$I_{DDC} = 40 \text{ mA}$

The voltage VAREF is derived from VPRE and it can be used as 5 V reference voltage for the internal AD converters. The value of the capacitor  $C_{VAREF}$  is in the range of 100 nF up to 1  $\mu$ F.

**Power Supply Generation Unit (PGU)**

### 2.3 VDDP: voltage regulator 5.0 V

This module represents the 5 V voltage regulator, which provides the pad supply for the parallel port pins and other 5-V analog functions (for example, the LIN transceiver).

**Notes**

1. The output capacitor  $C_{VDDP}$  is necessary for the stability of the output voltage.
2. The values of the  $C_{VDDP}$  capacitors are specified in the table below.
3. One single ceramic capacitor can be used, as long as the value is within the recommended range.
4. The  $C_{VDDP}$  capacitor should be placed as close as possible to the VDDP pin in the layout.
5. For EMC reasons, a ferrite bead can be placed between the VDDP pin and the  $C_{VDDP}$  capacitor.

**Table 5 Capacitor selection for VDDP**

Symbol	Function	Recommended component
$C_{VDDP}$	Output capacitor at VDDP	Ceramic capacitor <b>Min. value: 470 nF + 1 <math>\mu</math>F (1.47 <math>\mu</math>F)</b> <b>Max. value: 2.2 <math>\mu</math>F + 2.2 <math>\mu</math>F (4.4 <math>\mu</math>F)</b> Voltage rating: 10 V or higher Size and dielectric type defined according to the application

### 2.4 VDDC: voltage regulator 1.5 V

The 1.5-V voltage regulator provides the power supply for the microcontroller core, the digital peripherals, and other internal analog 1.5-V functions (for example, ADC2) of the chip.

**Notes**

1. The output capacitor  $C_{VDDC}$  is necessary for the stability of the output voltage.
2. The values of the  $C_{VDDC}$  capacitors are specified in the table below.
3. One single ceramic capacitor can be used, as long as the value is within the recommended range.
4. The  $C_{VDDC}$  capacitor should be placed as close as possible to the VDDC pin in the layout.
5. It is NOT possible to place a ferrite bead between the VDDC pin and the  $C_{VDDC}$  capacitor.
6. For EMI reasons the ground of the VDDC and the ground of the TLE987x can be separated by placing a ferrite bead between the two ground points.

**Table 6 Capacitor selection for VDDC**

Symbol	Function	Recommended component
$C_{VDDC}$	Output capacitor at VDDC	Ceramic capacitor <b>Min. value: 100 nF + 330 nF (430 nF)</b> <b>Max. value: 1 <math>\mu</math>F + 1 <math>\mu</math>F (2 <math>\mu</math>F)</b> Voltage rating: 4 V or higher Size and dielectric type defined according to the application

**Power Supply Generation Unit (PGU)**

## **2.5 VDDEXT: voltage regulator 5.0 V**

The 5-V voltage regulator supplies power to external circuits. It can be used, for example, to supply an external sensor, LEDs, or potentiometers. VDDEXT can be used as the reference for the SDADC (ADC3/4), if available in the product variant.

### **Notes**

1. The output capacitor  $C_{VDDEXT}$  is necessary for the stability of the output voltage.
2. The values of the  $C_{VDDEXT}$  capacitors are specified in the table below.
3. One single ceramic capacitor can be used, as long as the value is within the recommended limits.
4. The  $C_{VDDEXT}$  capacitor should be placed as close as possible to the VDDC pin in the layout.
5. In case VDDEXT is not used and disabled, the output capacitor  $C_{VDDEXT}$  is not needed. The pin VDDEXT can be left open.

**Table 7 Capacitor selection for VDDEXT**

<b>Symbol</b>	<b>Function</b>	<b>Recommended component</b>
$C_{VDDEXT}$	Output capacitor at VDDEXT	Ceramic capacitor <b>Min. value: 100 nF + 1 <math>\mu</math>F (1.1 <math>\mu</math>F)</b> <b>Max. value: 2.2 <math>\mu</math>F + 2.2 <math>\mu</math>F (4.4 <math>\mu</math>F)</b> Voltage rating: 10 V or higher Dielectric type: defined according to the application

## Clock Generation Unit (CGU)


### 3 Clock Generation Unit (CGU)

The Clock Generation Unit (CGU) enables flexible clock generation. The frequency can be modified to optimize the ratio of performance to power-consumption. The system clock  $f_{\text{SYS}}$  can be generated from one of the following sources:

- Phase-locked loop (PLL) output  $f_{\text{PLL}}$
- External clock from external crystal oscillator  $f_{\text{OSC}}$
- External clock from external clock input  $f_{\text{OSC}}$
- Low-precision clock  $f_{\text{LP\_CLK}}$

#### 3.1 Block diagram

The CGU consists of a high-precision oscillator circuit (OSC\_HP), a PLL module with an internal oscillator (OSC\_PLL), and a configurable Clock Control Unit (CCU). The CGU can convert a low-frequency input or external clock signal to a high-frequency internal clock.

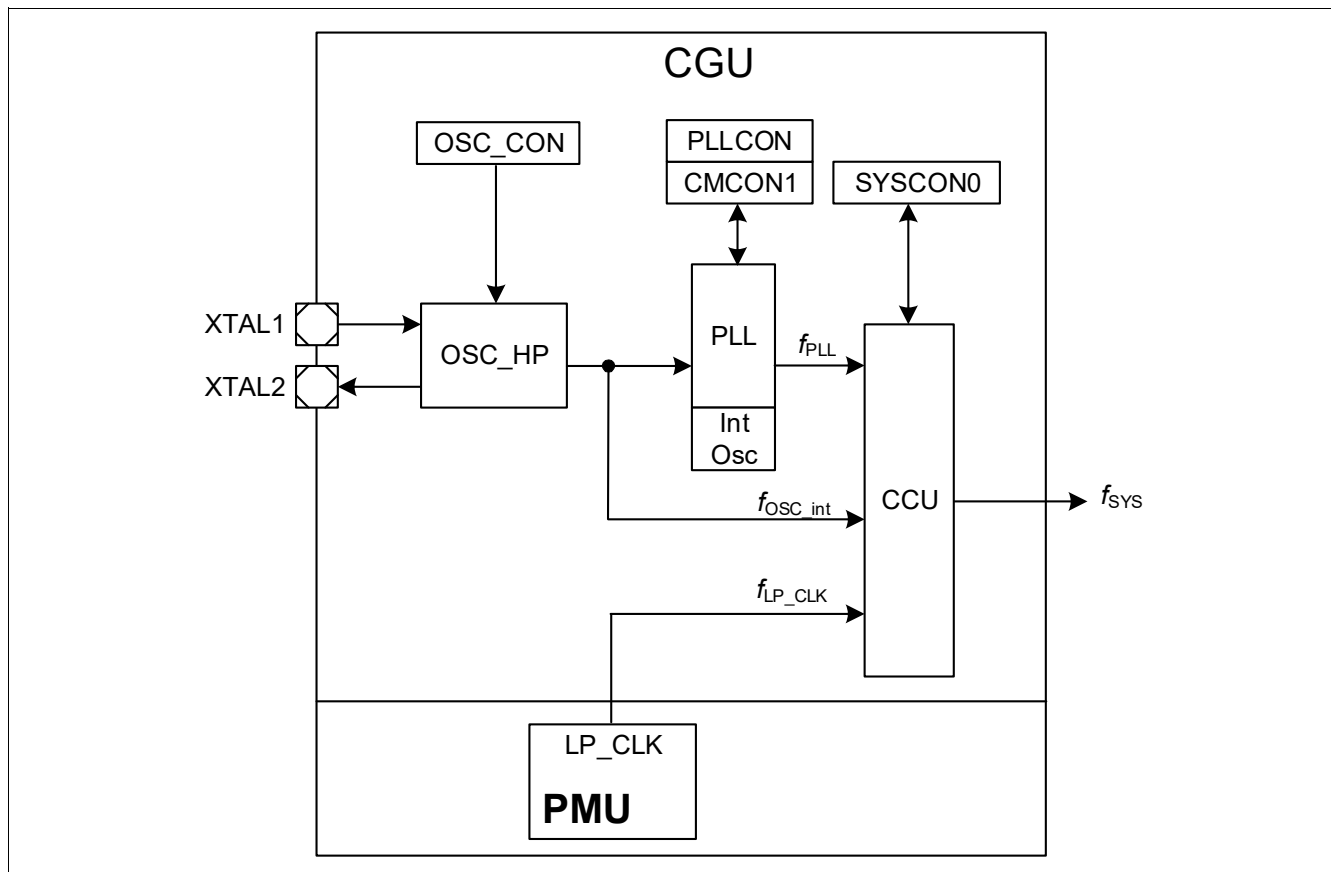

**Figure 6 CGU block diagram**

The submodules of the CGU are:

- **High-precision oscillator circuit:** designed to work with either an external crystal oscillator or an external stable clock source, it consists of an inverting amplifier with XTAL1 as the input and XTAL2 as the output.
- **PLL module:** this module generates the clock  $f_{\text{PLL}}$  in different modes:
  - Prescaler mode (VCO Bypass mode)
  - Normal mode
  - Freerunning mode

The reference frequency  $f_{\text{R}}$  can be selected to be taken either from the internal oscillator  $f_{\text{INT}}$  or from an

## Clock Generation Unit (CGU)

external clock source  $f_{\text{OSC\_INT}}$ .


The PLL uses up to three dividers to manipulate the reference frequency in a configurable way. Each of the three dividers can be bypassed corresponding to the PLL operating mode.

- **CCU:** The Clock Control Unit enables the selection of the source for  $f_{\text{SYS}}$ .

### 3.2 External Input Clock mode

The External Input Clock mode is used to directly supply the device with an externally generated clock signal in the range from 4 MHz to 16 MHz. In this mode, the high-precision oscillator circuit is bypassed and the external clock signal is fed directly into the PLL module. The input frequency has to be 4 MHz or higher, if the prescaler mode is used.


The external clock input has to be connected to XTAL1, while XTAL2 is left open (not connected). The negative terminal of the external clock input has to be connected to the analog GND (pin 39).

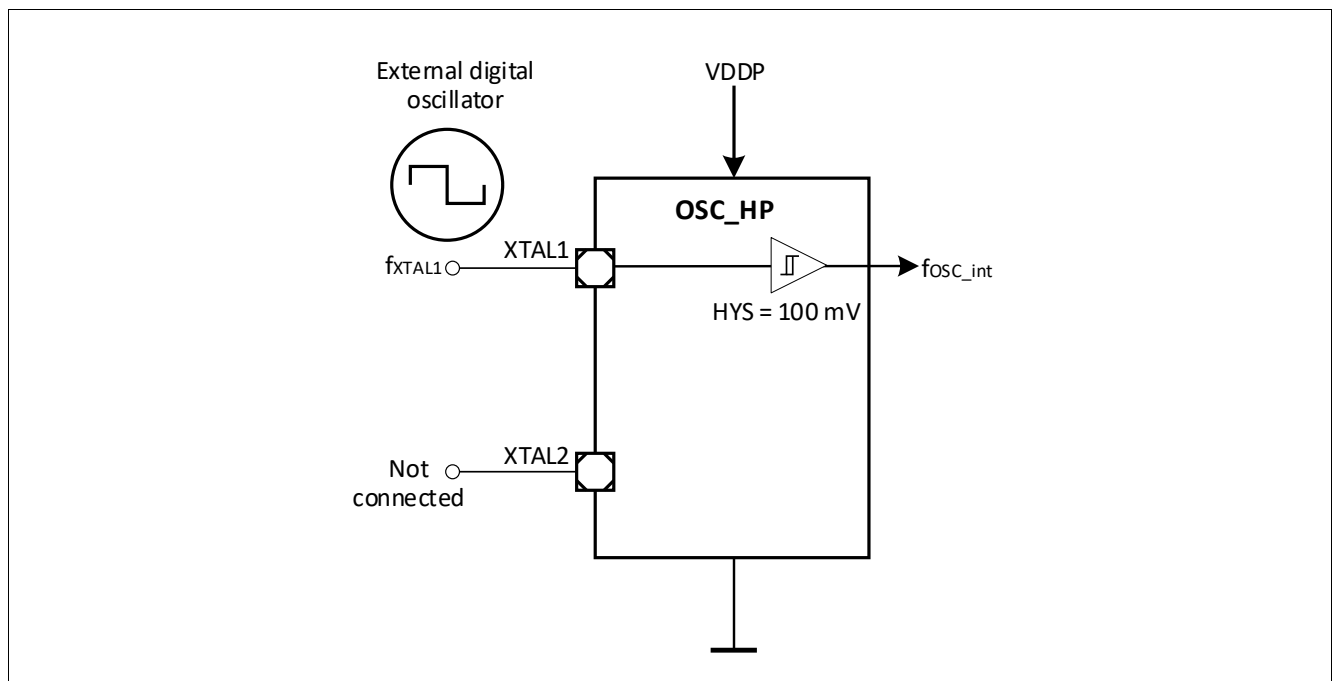

**Figure 7 External Input Clock mode**

### 3.3 External Crystal mode

The External Crystal mode is used to supply the device with an external crystal in the range from 4 MHz to 16 MHz. An external oscillator circuitry has to be placed, consisting of two load capacitors connected to XTAL1/GND and XTAL2/GND and an optional series damping resistor at XTAL2. The GND pin is in this case the analog GND (pin 39).

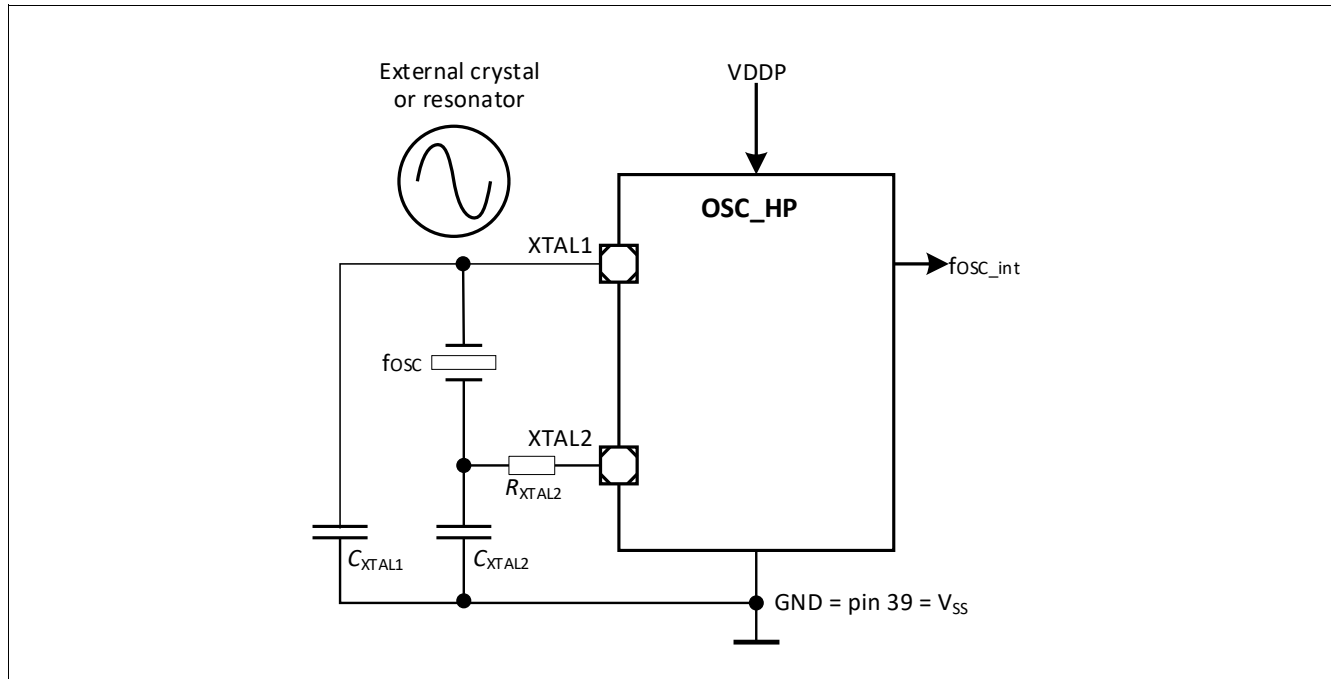

**Figure 8 External Crystal mode**

The values and the corresponding operating ranges depend on the chosen crystal and have to be determined and optimized in correlation with the crystal vendor, using the negative resistance method, which is the most common test for start-up and reliability of the oscillator. This method is about the insertion of a test resistor in series with the quartz crystal and the monitoring of the drive current. Typically, this test does not result in one set of circuitry values which is the 'right one', but it indicates a recommended range. Depending on further system requirements such as XTAL1 amplitude specification or oscillator frequency, the final circuitry values of the oscillator are then selected.

More information about the test method can be found in the Infineon Application Note "[Crystal Oscillator Basics AP56002](#)".

Symbol	Function	Recommended component
$C_{XTAL1}$ , $C_{XTAL2}$	Load capacitors for external crystal oscillator forming an LC tank circuit which determines the oscillator frequency	$\geq 10$ V ceramic capacitor X7R/X8R (low ESR, 0805 package)
$R_{XTAL2}$	Serial damping resistor	0-280 $\Omega$

The oscillator can operate for a specified set of crystals with known ESR and parasitic capacitances  $C_{i0}$  and  $C_o$  up to a specific value.

Choosing different crystals requires detailed consideration of parasitics, external circuitry, frequency range, and quality of the intended crystal. Its proper operation has to be verified by testing.


## Clock Generation Unit (CGU)

**Table 8 Recommendation for oscillator load capacitors**

$f_{osc}$	4 MHz	8 MHz	12 MHz	16 MHz
$ESR_{typ} / \Omega$	120	90	80	70
$C_{IO} / pF$	3.5	3.5	3.5	3.5
$C_O / pF$	3	3	3	3
$C_{XTAL1} = C_{XTAL2} / pF$	33	18	12	12

### 3.4 Layout recommendations

**Figure 9** shows a layout example for an SMD quartz crystal to be used with the TLE987x/6x.

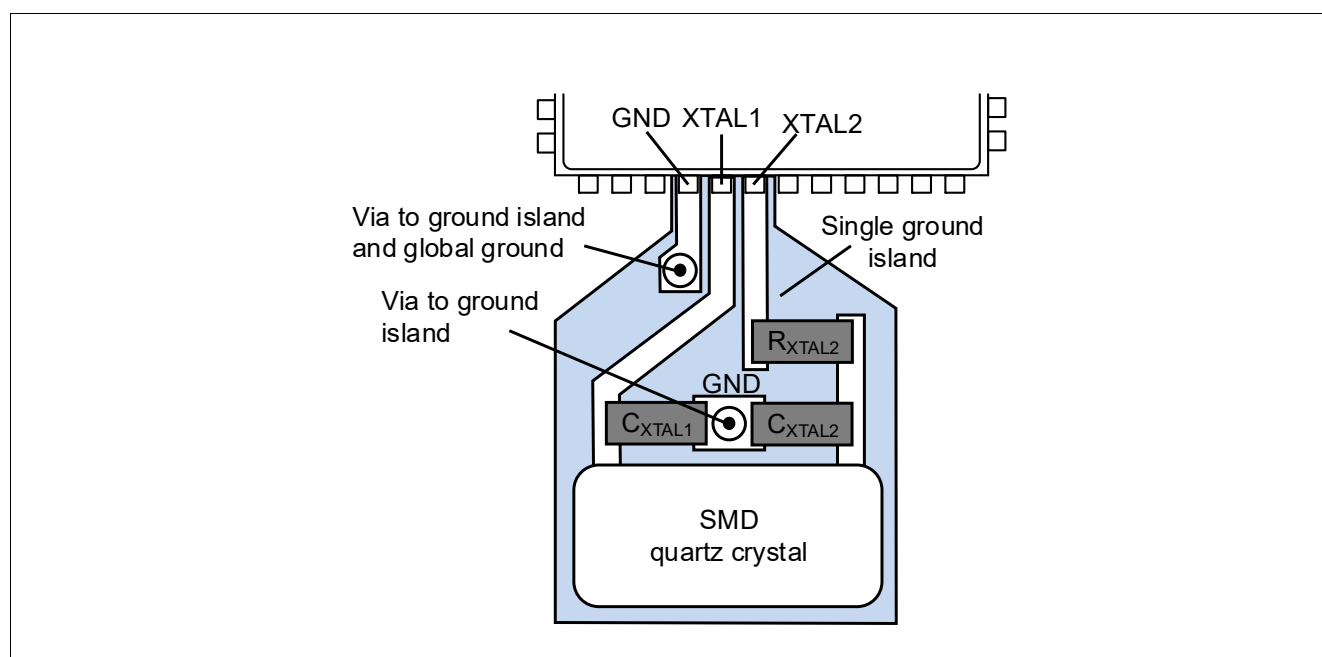


**Figure 9 CGU layout recommendation**

## LIN transceiver

### 4 LIN transceiver

The LIN module is a transceiver for the Local Interconnect Network (LIN), compliant to the LIN2.2 standard, backward compatible to LIN1.3, LIN2.0 and LIN2.1. It operates as a bus driver between the protocol controller and the physical network. The LIN bus is a single-wire, bidirectional bus, which is typically used for in-vehicle networks, using data rates between 2.4 kBaud and 20 kBaud. Additionally, data rates up to 115.2 kBaud are supported.

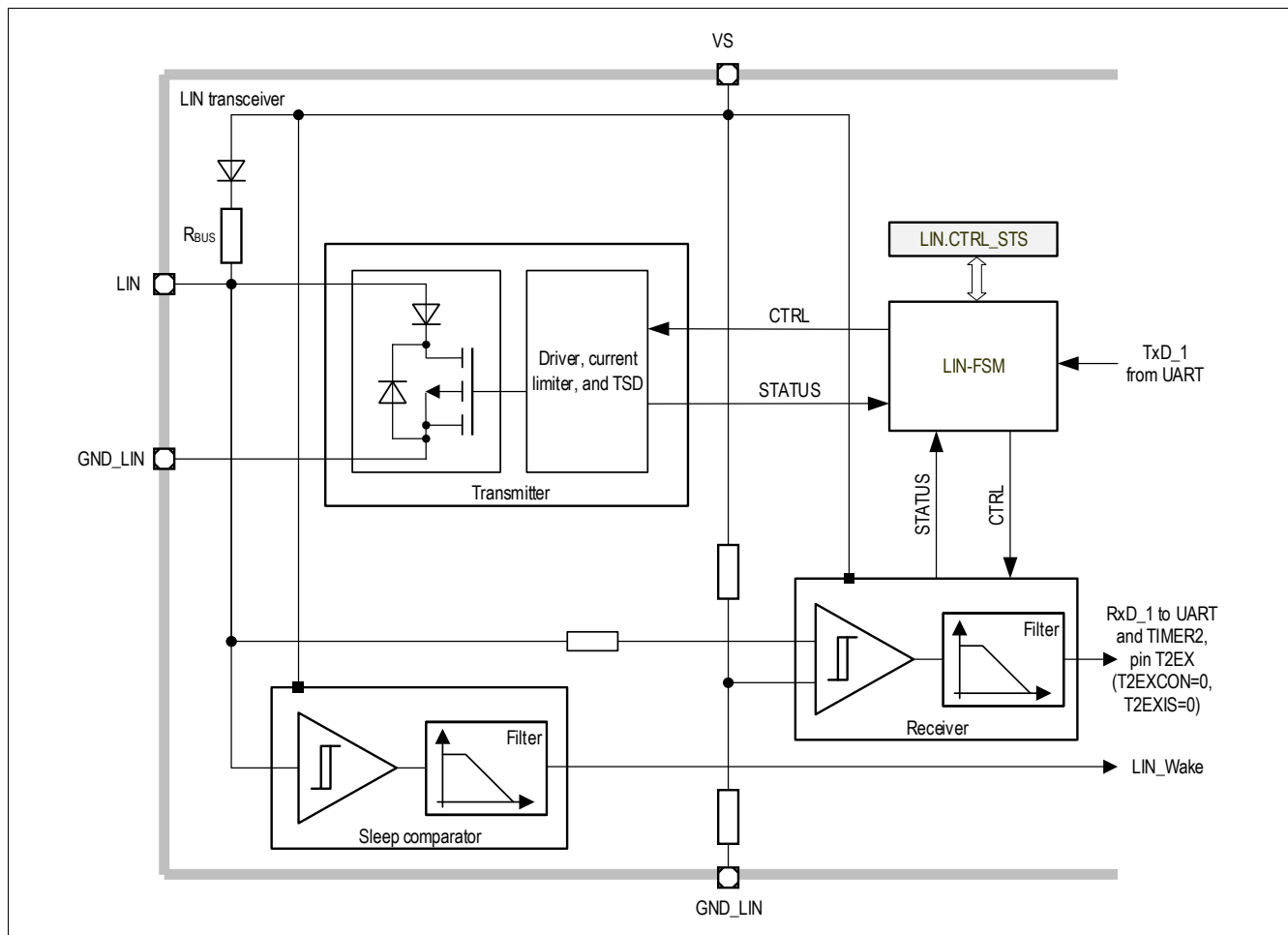

**Figure 10 LIN transceiver Block Diagram**

It is recommended to put a 220 pF capacitor between the LIN input and GND\_LIN pins. This complies with the LIN specification 2.2.

The GND\_LIN pin has to be connected to a global ground net outside the chip.

In order to avoid interferences with the SoC's core voltage, it is recommended to connect GND\_LIN to the same ground net of the power MOSFETs – called power GND.

To reduce digital ground bounce transmitted via LIN, GND\_LIN should not be connected directly to the GND of the TLE987x/6x. It is better to have a slight decoupling by using few millimeters of trace.

The LIN transceiver can be used also with PWM control. In this case, a pull-up resistor between the LIN input and the battery input voltage should be placed. The value of the pull-up resistor is  $\geq 1 \text{ k}\Omega$ .

In case additional filtering is needed because of EMC issues, common mode chokes before the LIN pin are not recommended. A ferrite bead placed at GND\_LIN is preferred.

## High-voltage monitor input

### 5 High-voltage monitor input

This module monitors external voltage to detect levels above or below a specified threshold, or it can be used in Low-Power mode to detect a wake-up event at the high-voltage MON pin.

#### 5.1 Block diagram

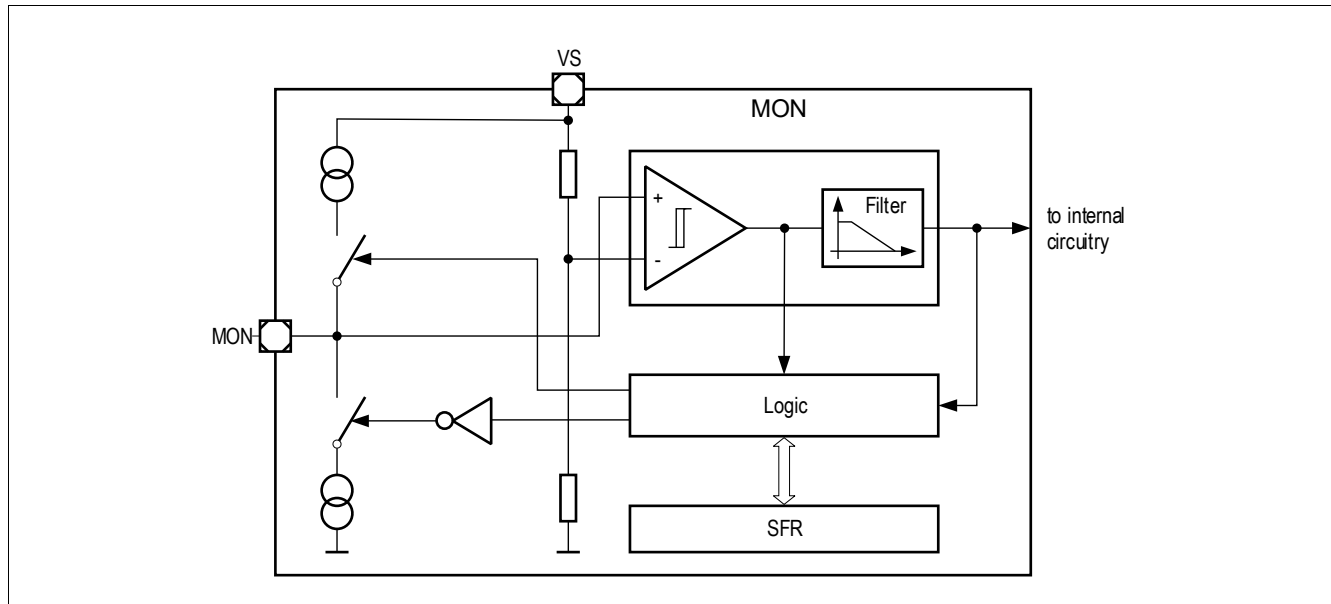


Figure 11 Monitor input block diagram

#### 5.2 Application hints

The functional description of the high-voltage monitor input is included in chapter 26 of the TLE987x and TLE986x User Manuals.

A dedicated R-C filter ( $R_{MON}$  and  $C_{MON}$ ) must be placed before the MON pin (Figure 2), in order to protect it against reverse polarity connection and voltage transients (ISO pulses), which could violate the absolute maximum ratings of the MON pin. In fact, in a typical use-case the MON pin could be directly connected to the car battery in order to sense the supply voltage, especially during power-down.

Table 9 shows the recommended  $R_{MON}$  and  $C_{MON}$  values. The GND to be used for  $C_{MON}$  is the analog or digital GND. Since the R-C time constant affects the voltage slope on the MON pin, the  $R_{MON}$  and  $C_{MON}$  values should be selected according to the application requirements. Due to potential high peak power during transient tests, the recommended package for  $R_{MON}$  is 1206 SMD.

Table 9 Component selection for the MON pin


Symbol	Function	Recommended component
$R_{MON}$	Filter resistor	<b>Min. value 1 kΩ</b> $R_{MON}$ value and size selected according to the application, package 1206 SMD recommended
$C_{MON}$	Filter capacitor	Ceramic capacitor <b>Min. value 10 nF, typical voltage rating 50 V</b> $C_{MON}$ value, voltage rating, size, and dielectric type selected according to the application

## 6 Bridge driver (excluding charge pump)

The bridge driver is intended to drive external normal-level MOSFETs in bridge configuration. This chapter provides details about external components, which are needed depending on application requirements. Detailed information about the bridge driver functioning and configuration is available in the Infineon Application Note “[TLE986x/TLE987x Bridge Driver](#)”.

### 6.1 Application diagram

The following application diagram shows the gate drivers for one half-bridge with the (partially optional) external components, which are described in this chapter.

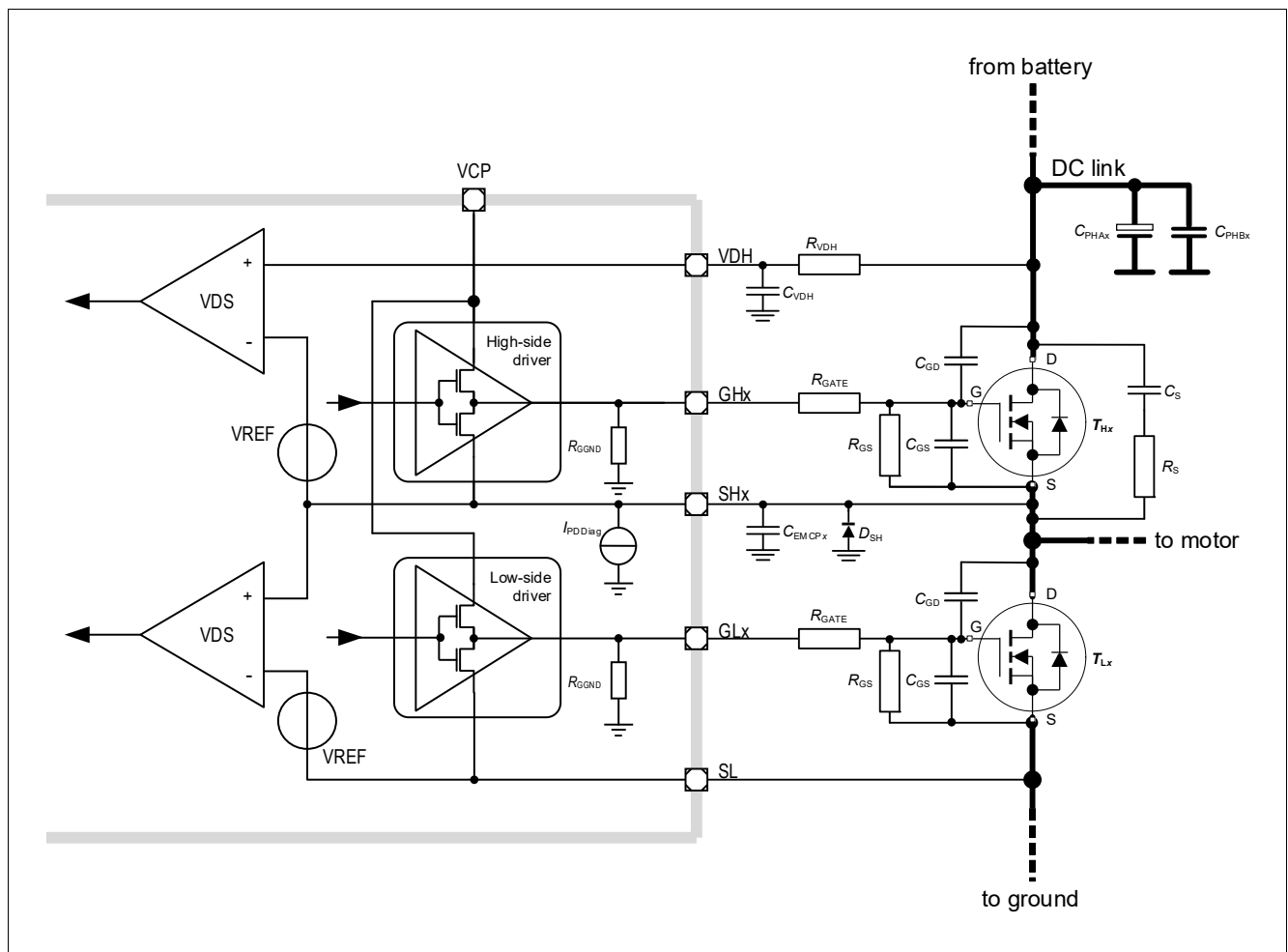

**Figure 12 Gate drivers for one half-bridge with external components**

## 6.2 External components

### 6.2.1 Overview

Component	Short description	Recommended value
$R_{\text{GATE}}$	<b>Gate resistor (optional)</b> : suppresses potential oscillations between PCB line inductances and MOSFET capacitances	2 $\Omega$ ... 10 $\Omega$
$R_{\text{GS}}$	<b>Gate-to-source resistor</b> : terminates the MOSFET gate	100 k $\Omega$
$C_{\text{GS}}$	<b>Gate-to-source capacitor (optional)</b> : linearizes the intrinsic MOSFET gate-to-source capacitor	it depends on MOSFET
$C_{\text{GD}}$	<b>Gate-to-drain capacitor (optional)</b> : linearizes the intrinsic MOSFET gate-to-drain capacitor	
$C_{\text{PHAx}}$	<b>DC link capacitors: A</b> buffers DC link voltage	it depends on application requirements
$C_{\text{PHBx}}$	<b>DC link capacitors: B</b> suppresses double-digit MHz oscillations	
$R_{\text{S}}, C_{\text{S}}$	<b>Snubber (optional)</b> : reduces voltage peaks and ringing at motor pin	
$C_{\text{EMCPx}}$	<b>EMC filter capacitor at the SHx pin</b> : suppresses fast transients at SHx	1 nF
$R_{\text{VDH}}, C_{\text{VDH}}$	<b>Low-pass filter at the VDH pin</b> : suppresses high-frequency components of DC link voltage	1 k $\Omega$ , 1 nF ... 3.3 nF
$D_{\text{SH}}$	<b>Protection diode at the SHx pin (optional)</b> : limits SHx undershoot voltages	–

### 6.2.2 Details

#### 6.2.2.1 Gate resistor

The optional gate resistor  $R_{\text{GATE}}$  suppresses potential oscillations between PCB line inductances and MOSFET capacitances, which build up an LC oscillator that can be stimulated by fast transients during MOSFET switching. The value of  $R_{\text{GATE}}$  depends on the PCB layout conditions, MOSFET parasitics, and switching speed, but should be as small as possible, preferably in the range from 2  $\Omega$  to 10  $\Omega$ .

#### 6.2.2.2 Gate-to-source resistor

The gate-to-source resistor  $R_{\text{GS}}$  terminates the gate of the external MOSFET to its source. It should be placed as close as possible to the MOSFET to keep it turned off, for example, in the case of electromagnetic interference (EMI) or broken PCB lines. The recommended value is 100 k $\Omega$ .

**Bridge driver (excluding charge pump)**

### 6.2.2.3 Gate-to-source capacitor

The optional gate-to-source capacitor  $C_{GS}$  linearizes the intrinsic MOSFET gate-to-source capacitance and reduces the tolerance of the total gate-to-source capacitance seen by the gate driver. The value of  $C_{GS}$  should be large enough to dominate the intrinsic MOSFET gate-to-source capacitance  $C_{GS\_int}$ . The recommendation is:  $C_{GS} \geq 2 \times C_{GS\_int}$ .

#### Notes

1. The maximum gate charge  $Q_{tot\_max}$  per MOSFET including the external gate capacitors must not exceed 100 nC.
2.  $C_{GS\_int}$  is usually not directly given in MOSFET datasheets, but it can be estimated from parameters like  $C_{iss}$  or  $Q_{gs}$ .

### 6.2.2.4 Gate-to-drain capacitor

The optional gate-to-drain capacitor  $C_{GD}$  linearizes the intrinsic MOSFET gate-to-drain capacitor and reduces the tolerance of the total gate-to-drain capacitance seen by the gate driver. The placement of  $C_{GD}$  is recommended, if it is important for the application to have a well-controlled linear slew rate at the SHx pin:  $\Delta V_{SHx} / \Delta t = I_{GATE} / C_{GD}$ .

#### Notes

1. The maximum gate charge  $Q_{tot\_max}$  per MOSFET including the external gate capacitors must not exceed 100 nC.
2. In order to avoid unintended switch-on of the MOSFET during fast transients, the following condition must be met:  $C_{GD} / C_{GS} \leq 1 / 10$ .

### 6.2.2.5 DC link capacitors

The DC link capacitors  $C_{PHAx}$  and  $C_{PHBx}$  serve two purposes:

1.  $C_{PHAx}$  works as a buffer capacitor.
2.  $C_{PHBx}$  suppresses double-digit MHz oscillations on the DC link voltage.

The total value of all DC link capacitors  $C_{PH\_tot} = \sum (C_{PHAx} + C_{PHBx})$  depends on the acceptable DC link voltage ripple caused by PMW operation and on additional application-specific requirements, like having motors operating in generator mode or the need to buffer the motor energy in the case of an emergency shutdown of the MOSFETs.

**Note:**  $C_{PH\_tot}$  must be large enough to always keep all connected input pins (for example, VDH, VSD) within their absolute maximum ratings.

As a starting point for the value of  $C_{PH\_tot}$ , a rule of thumb is 230  $\mu F$  per 10 A of motor current. The bigger part of the capacitance is covered by electrolytic capacitors  $C_{PHAx}$  and the rest by ceramic capacitors  $C_{PHBx}$ . It is recommended to choose capacitors with low ESR and low self-inductance and to place them close to their respective high-side MOSFETs, in order to minimize series resistances and inductances in the high-current path.

**Bridge driver (excluding charge pump)**

### **6.2.2.6 Snubber**

The optional snubber  $R_S$  and  $C_S$  reduces voltage peaks and ringing at the motor pin, which can be caused by PCB parasitics like series inductances. The values for  $R_S$  and  $C_S$  depend on the half-bridge power ratings and on the parasitics of the selected MOSFET.

Starting values for  $R_S$  and  $C_S$  can be derived from the following constraints:

- $R_S \leq V_{\text{DCLink}} / I_{\text{motor}}$  in order to keep the voltage across  $R_S$  always smaller than the DC link voltage
- $C_S \geq 2 \times C_{\text{OSS}}$ , where  $C_{\text{OSS}}$  is the output capacitance of the MOSFET

#### **Notes**

1. For  $R_S$ , a resistor with very low self-inductance should be chosen. The resistor power class can be derived from the maximum energy stored in  $C_S$ .
2. For  $C_S$ , a capacitor with high peak-current capability should be chosen.

### **6.2.2.7 EMC filter capacitor at the SHx pin**

The EMC filter capacitor  $C_{\text{EMCPx}}$  at the SHx pin suppresses fast transients coming from the motor pin. The recommended value is 1 nF. This capacitor should be placed as close as possible to the SHx pin.

### **6.2.2.8 Low-pass filter at the VDH pin**

The low-pass filter  $R_{\text{VDH}}$  and  $C_{\text{VDH}}$  at the VDH pin suppresses high-frequency components on the DC link voltage. The VDH input serves as the reference voltage of the high-side drain-source comparators and should be stable right after each MOSFET switching event. Therefore, a time constant in the range of a low single-digit  $\mu\text{s}$  value should be targeted, for example:  $R_{\text{VDH}} = 1 \text{ k}\Omega$  and  $C_{\text{VDH}} = 1 \text{ nF}$ .

*Note:  $R_{\text{VDH}}$  performs an additional protection role by limiting the current out of the VDH pin in the case of a reverse-polarity event or other undershoots of the DC link voltage.*

### **6.2.2.9 Protection diode at the SHx pin**

The optional protection diode at the SHx pin limits SHx undershoot voltages. This diode is only recommended if undershoots below the absolute maximum ratings may be expected due to unknown application conditions.

## Charge pump


### 7 Charge pump

The charge pump is intended to supply the bridge driver integrated in the TLE987x/6x, as well as the Back-EMF comparators. The purpose of this chapter is to provide a design method for the external capacitors, depending on the application requirements.

#### 7.1 Application diagram

The following application diagram shows the charge pump and its external components, which are the flying capacitors CCPS1 / CCPS2 and the output capacitor CVCP. The input voltage of the charge pump is VSD, while the output voltage is VCP.

$V_M$  is the motor voltage after the MOSFET for reverse polarity protection. An RC network can be optionally placed between  $V_M$  and VSD.  $C_{VSDM}$  is acting as filter capacitor, while  $R_{VSD}$  limits the current flowing into VSD during voltage transients. The recommended values for  $C_{VSDM}$  and  $R_{VSD}$  are 1  $\mu$ F and 2  $\Omega$ .

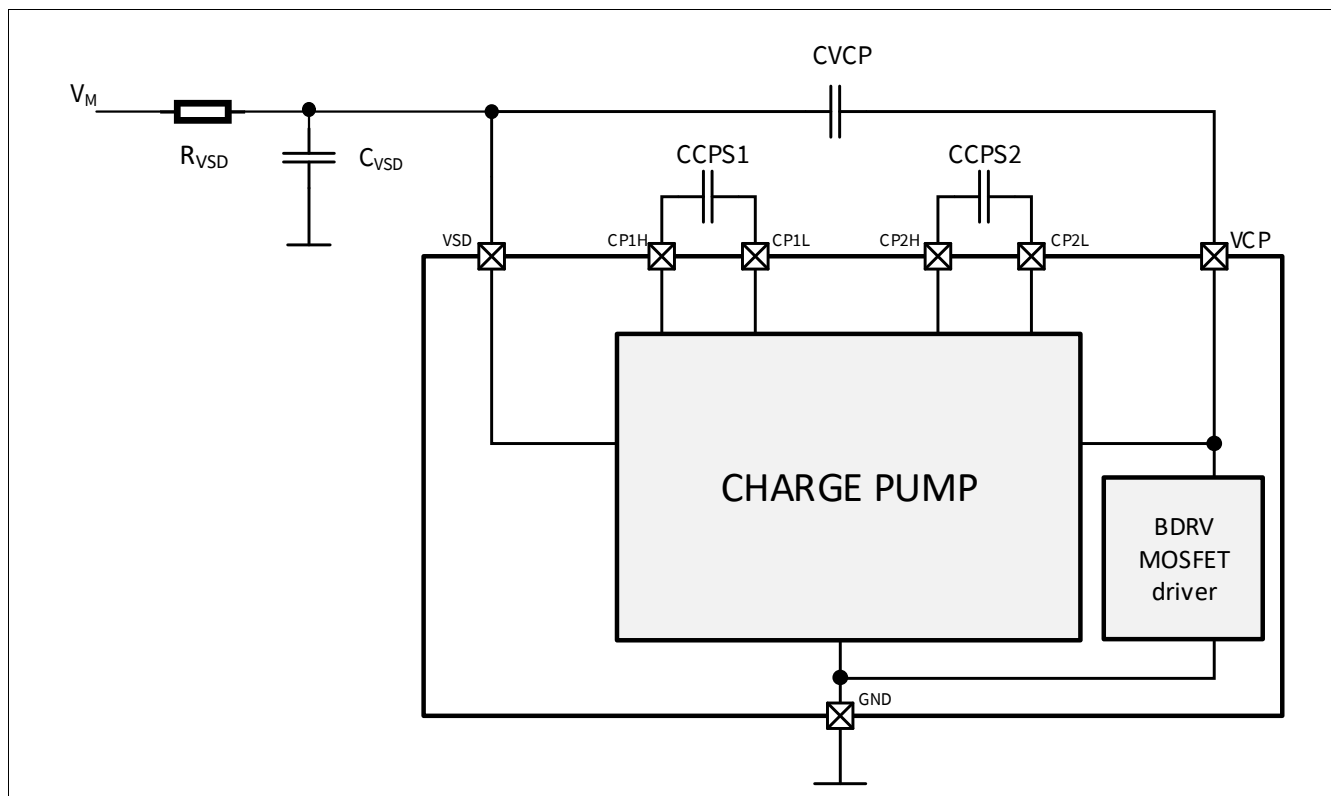

**Figure 13** Charge pump application diagram

#### 7.2 Charge pump: how it works

The voltage VCP is generated by a 2-stage charge pump, as a multiplying effect of the input voltage VSD using two flying capacitors CCPS1 and CCPS2: ideally, each stage of the charge pump can provide a voltage increase equal to the input voltage. The output capacitor CVCP acts as bulk for the voltage VCP. A detailed description of the behavior of an n-stage charge pump is available in the following literature:

- “On-Chip High-Voltage Generation in Integrated Circuits Using an Improved Multiplier Technique”  
by J.F. Dickson
- “Theoretical and Experimental Analysis of Dickson Charge Pump Output Resistance”  
by A. Cabrini, L. Gobbi, and G. Torelli

## Charge pump

The switches of the charge pump are driven by an internal clock (CLK) with a frequency equal to  $f_{SW}$ , derived from the TLE987x/6x system clock. The following pattern applies (**Figure 14**):


- **Clock set to low:** the capacitor CCPS1 is charged by VSD, while the energy of CCPS2 is transferred to the output, boosting the voltage VCP of the capacitor CVCP. Considering  $V_{DROP1}$  as the voltage drop of the switches of the first stage and ignoring the load current, the average voltage VCPS1 can be expressed as:

$$VCPS1 = 2 VSD - V_{DROP1}$$

- **Clock set to high:** the energy is transferred from CCPS1 to CCPS2, while the output voltage VCP is buffered by the bulk capacitor CVCP. Considering  $V_{DROP2}$  as the voltage drop of the switches of the first and second stage and ignoring the load current, the average voltages VCPS2 and VCP can be expressed as:

$$VCPS2 = 3 VSD - V_{DROP2} \quad ; \quad VCP = 3 VSD - V_{DROP}$$

where  $V_{DROP}$  is the total voltage drop of the switches of the charge pump.

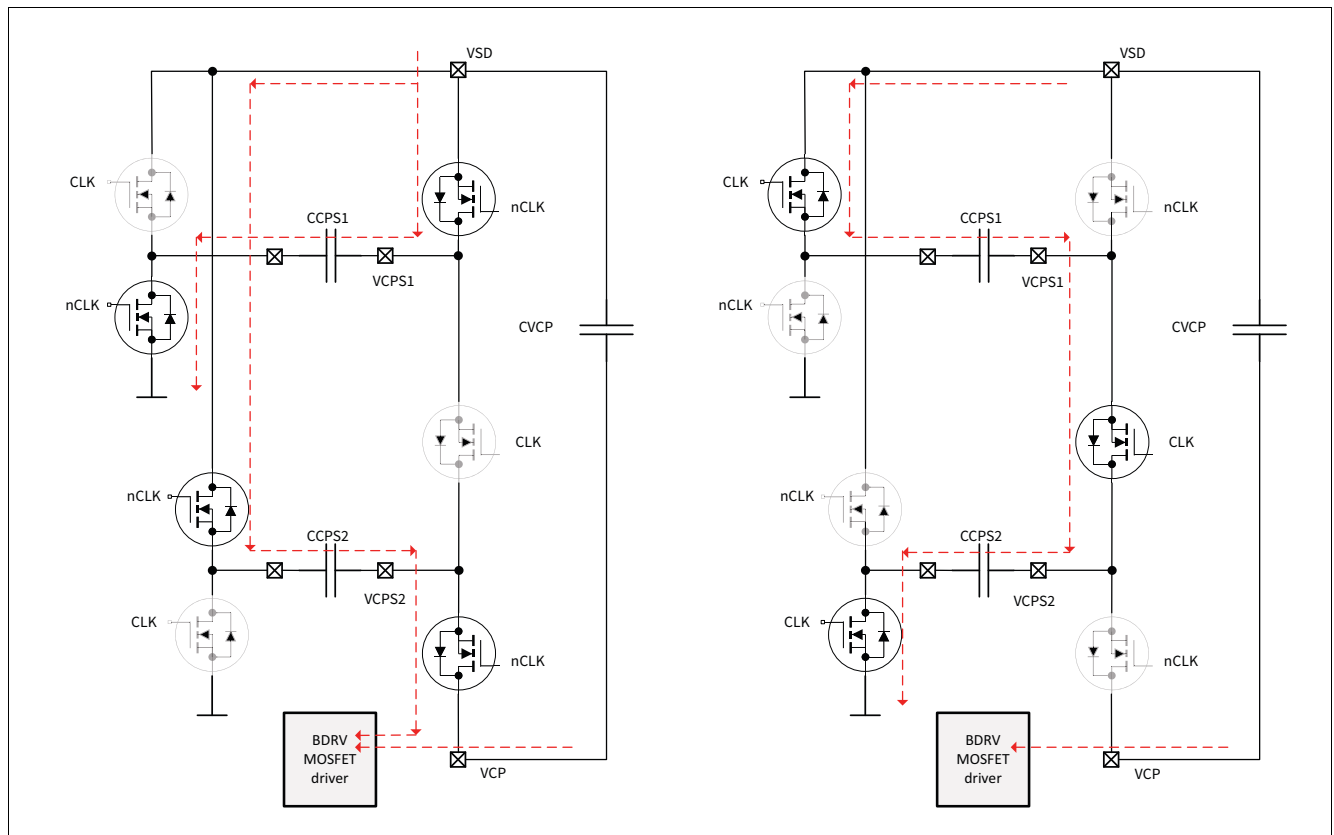

**Figure 14 Basic scheme of the charge pump (left: clock set to low; right: clock set to high)**

## Charge pump

Including now the load current in the calculation, the output voltage VCP can be expressed as:

(7.1)

$$V_{CP} = 3 V_{SD} - V_{DROP} - R_{OUT\_AVG} \times I_{CP}$$

where:

- $I_{CP}$  is the average output current, as sum of the bias current of the bridge driver and the total current needed to drive the MOSFETs gates;
- $R_{OUT\_AVG}$  is the average output resistance of the charge pump, which can be expressed as:

(7.2)

$$R_{OUT\_AVG} \approx \frac{2}{f_{SW} \times CCPS} + \frac{3}{4 \times f_{SW} \times CVCP}$$

where  $f_{SW}$  is the switching frequency of the charge pump, and CCPS1 and CCPS2 are both equal to CCPS. Considering:


$$V_{DROP} = I_{CP} \times R_{EQ}$$

the [Equation \(7.1\)](#) can be rearranged as follows:

(7.3)

$$V_{CP} = 3 \times V_{SD} - I_{CP} (R_{EQ} + R_{OUT\_AVG})$$

where  $R_{EQ}$  is an average resistance, which takes into account of the total voltage drop  $V_{DROP}$  as soon as it varies with the output current. A value of  $R_{EQ}$  fitting to the TLE987x/6x charge pump is about 100 Ω. [Figure 15](#) shows the equivalent circuit as expressed by the [Equation \(7.3\)](#).

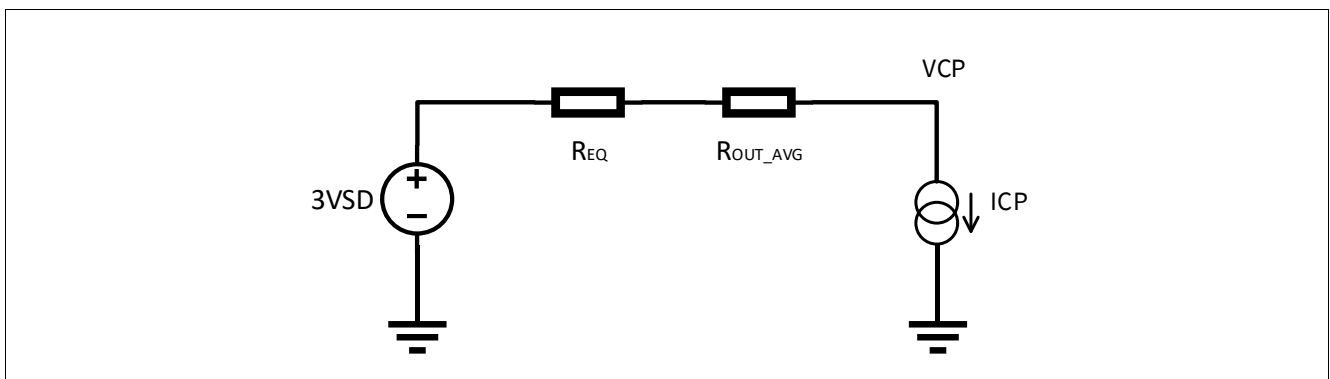

**Figure 15** Charge pump equivalent circuit

## Charge pump

Considering the wide range of the input voltage VSD, the charge pump of the TLE987x limits the output voltage VCP according to the following relations:

$$V_{CP} - V_{SD} \cong \begin{cases} 14 \text{ V} & \text{if } V_{CP} - V_{SD} \geq 14 \text{ V} \\ V_{CP} - V_{SD} & \text{if } V_{CP} - V_{SD} < 14 \text{ V} \end{cases}$$

Important to note is that the above equations are aiming to provide an equivalent model of the charge pump considering average values of the electrical parameters, not RMS (root medium square) values. **For this reason, they should not be used straightforward to calculate the power dissipation of the charge pump itself.**

### 7.2.1 ICP load current calculation

The load current ICP of the charge pump is the sum of the currents supplied to each gate, and the bias current of the bridge driver. In [Figure 16](#) the gate charge and discharge current paths are shown. Referring to this figure, the following equations can be derived:

(7.4)

$$I_{CP} = N_G \times (I_{CP_M} + I_{BIAS})$$

(7.5)

$$I_{CP_M} = N_M \times f_{PWM} \times Q_M$$

(7.6)


$$Q_M = Q_{MOSFET} + CGS_{ext} \times V_{GS} + CGD_{ext} \times V_{GD}$$

where:

- $N_G$  is the number of half-bridge drivers active in one PWM switching period. This value depends on the PWM switching scheme and the control technique used in the application. Considering a 3-phase motor,  $N_G$  is equal to 1 with block commutation, while  $N_G$  is equal to 3 with FOC (Field Oriented Control).
- $I_{CP_M}$  is the current of each half-bridge gate driver.
- $I_{BIAS}$  is the bias current of each single half-bridge driver. A typical for  $I_{BIAS}$  value is about 2 mA.
- $N_M$  is the number of MOSFETs turned on in one PWM switching period. This value depends on the PWM switching scheme and the control technique used in the application. For block commutation and FOC  $N_M$  is equal to 2.
- $f_{PWM}$  is the PWM switching frequency.

## Charge pump


- $Q_M$  is the total charge transferred to the High-Side (HS) and/or Low-Side (LS) gate, including the charge of external capacitors.
- $Q_{MOSFET}$  is the gate charge of the HS (and/or LS) gate present at a certain VGS.
- $CGS_{ext}$  is the value of the external gate to source capacitance.
- $VGS$  is the gate to source voltage.
- $CGD_{ext}$  is the value of the external gate to drain capacitance.
- $VGD$  is the gate to drain voltage.

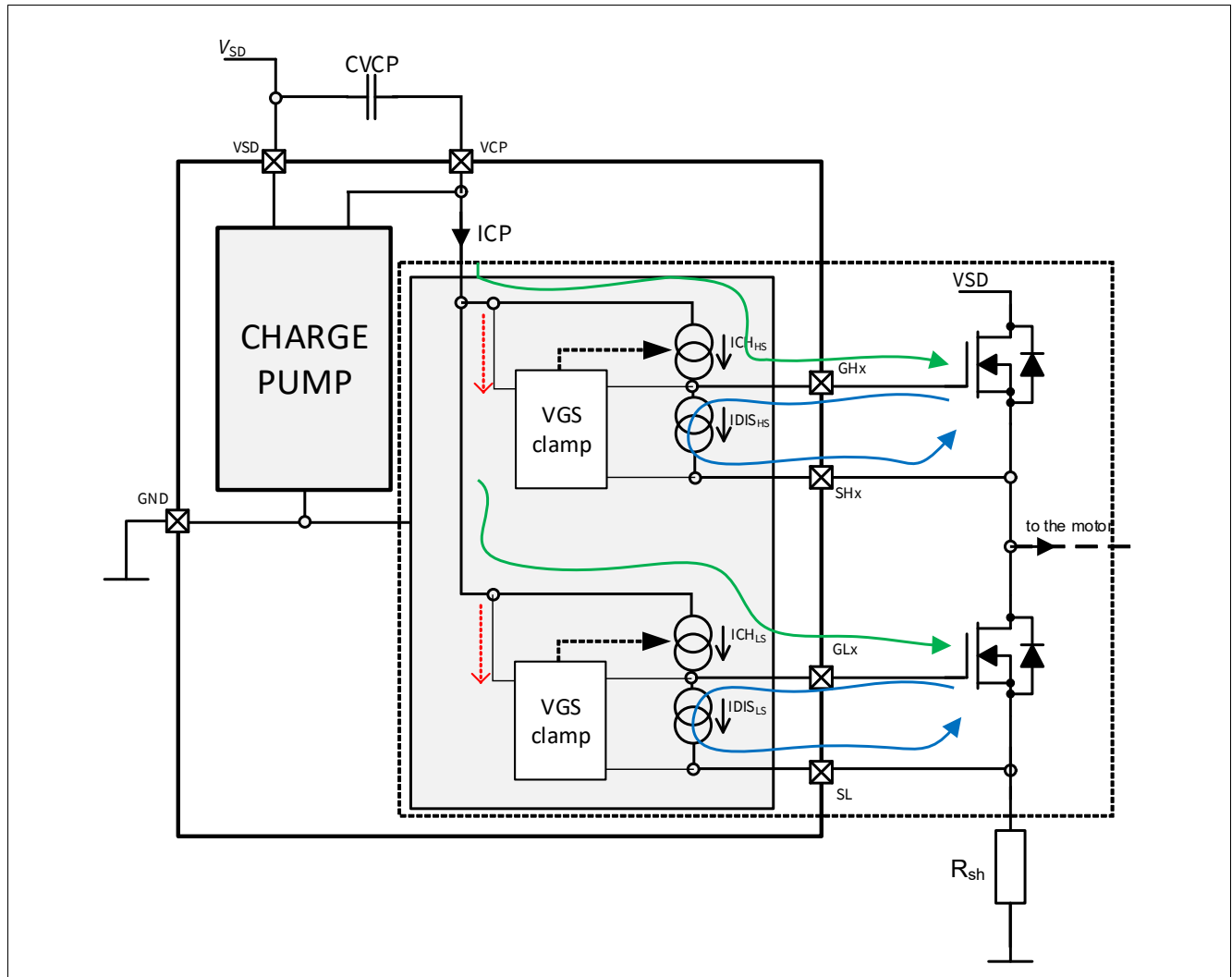

**Figure 16** Schematic representation of the High-side and Low-side MOSFET gate charge (green) and discharge (blue) currents paths (left). Bias current in red. Each gate driver block is repeated 3× in the TLE987x, while 2× in the TLE986x.

## Charge pump

The gate charge  $Q_{\text{MOSFET}}$  can be determined from the characteristics of the MOSFET. A typical gate charge graph of an automotive Infineon MOSFET ([IAUA120N04S5N014](#)) is shown in the [Figure 17](#).

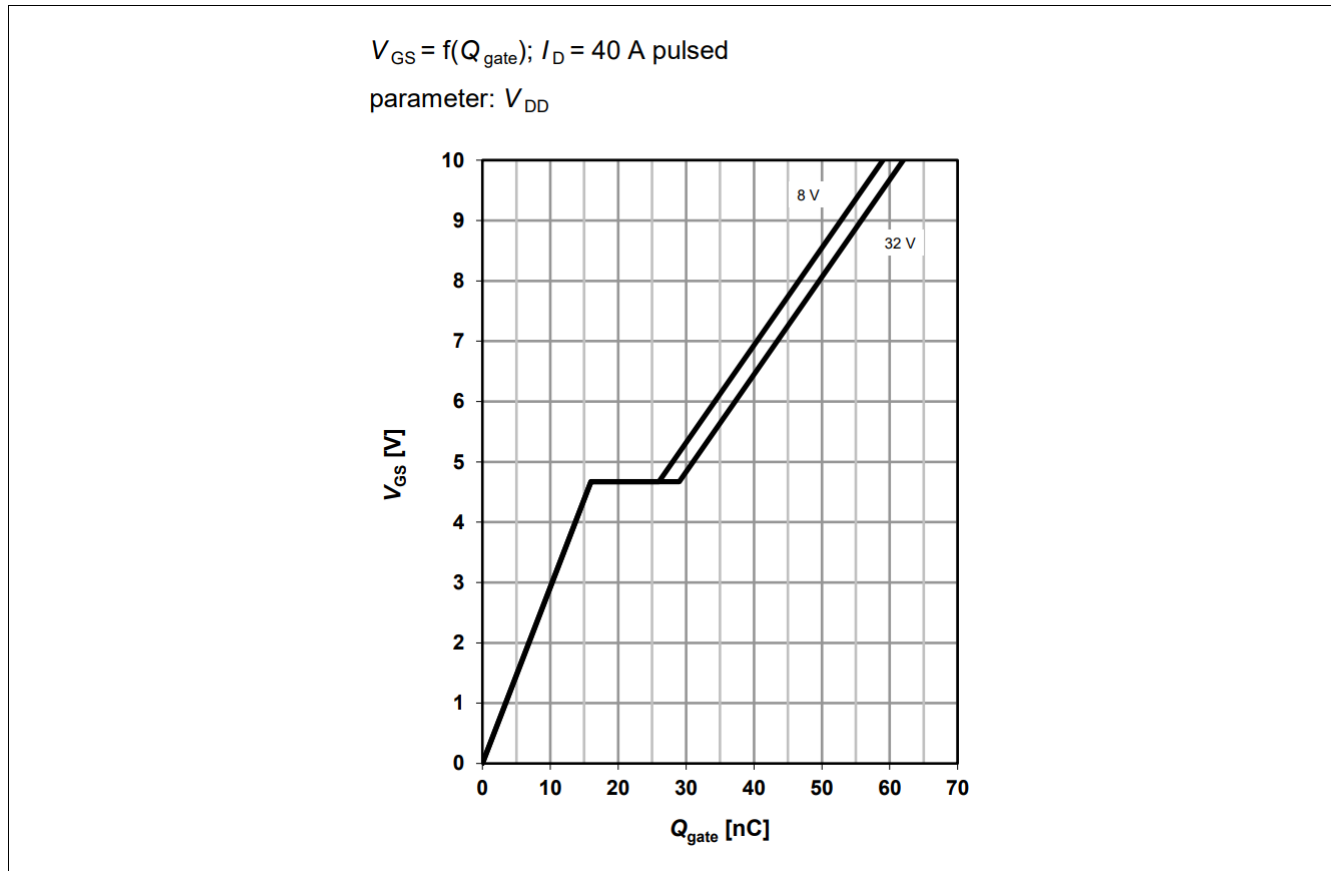

**Figure 17 Gate charge of the IAUA120N04S5N014**

In the bridge driver implementation of the TLE987x/6x, the HS and LS gate source voltages  $V_{\text{GS}}$  are limited by an internal clamping. In [Figure 18](#) a simplified schematic of the bridge driver is illustrated. It can be assumed that the MOSFETs ON-resistances and the current sensing resistor  $R_{\text{sh}}$  are in the order of magnitude of  $[\text{m}\Omega]$ . As a consequence the following approximations can be made:

- When **HSx** is **ON** and **LSx** is **OFF**  $\rightarrow V_{\text{PHx}} \cong V_{\text{SD}}$
- When **LSx** is **ON** and **HSx** is **OFF**  $\rightarrow V_{\text{PHx}} \cong V_{\text{SL}} \cong \text{GND}$


Taking this into account, the typical average  $V_{\text{GS}_{\text{HS}}}$  (for the HS) and  $V_{\text{GS}_{\text{LS}}}$  (for the LS) voltages can be estimated as:

(7.7)

$$V_{\text{GS}_{\text{HS}}} \cong \begin{cases} 12.5 \text{ V} & \text{if } V_{\text{CP}} - V_{\text{SD}} \geq 14 \text{ V} \\ V_{\text{CP}} - V_{\text{SD}} - 1.5 \text{ V} & \text{if } V_{\text{CP}} - V_{\text{SD}} < 14 \text{ V} \end{cases}$$

$$V_{\text{GS}_{\text{LS}}} \cong \begin{cases} 12.5 \text{ V} & \text{if } V_{\text{CP}} \geq 14 \text{ V} \\ V_{\text{CP}} - 1.5 \text{ V} & \text{if } V_{\text{CP}} < 14 \text{ V} \end{cases}$$

## Charge pump

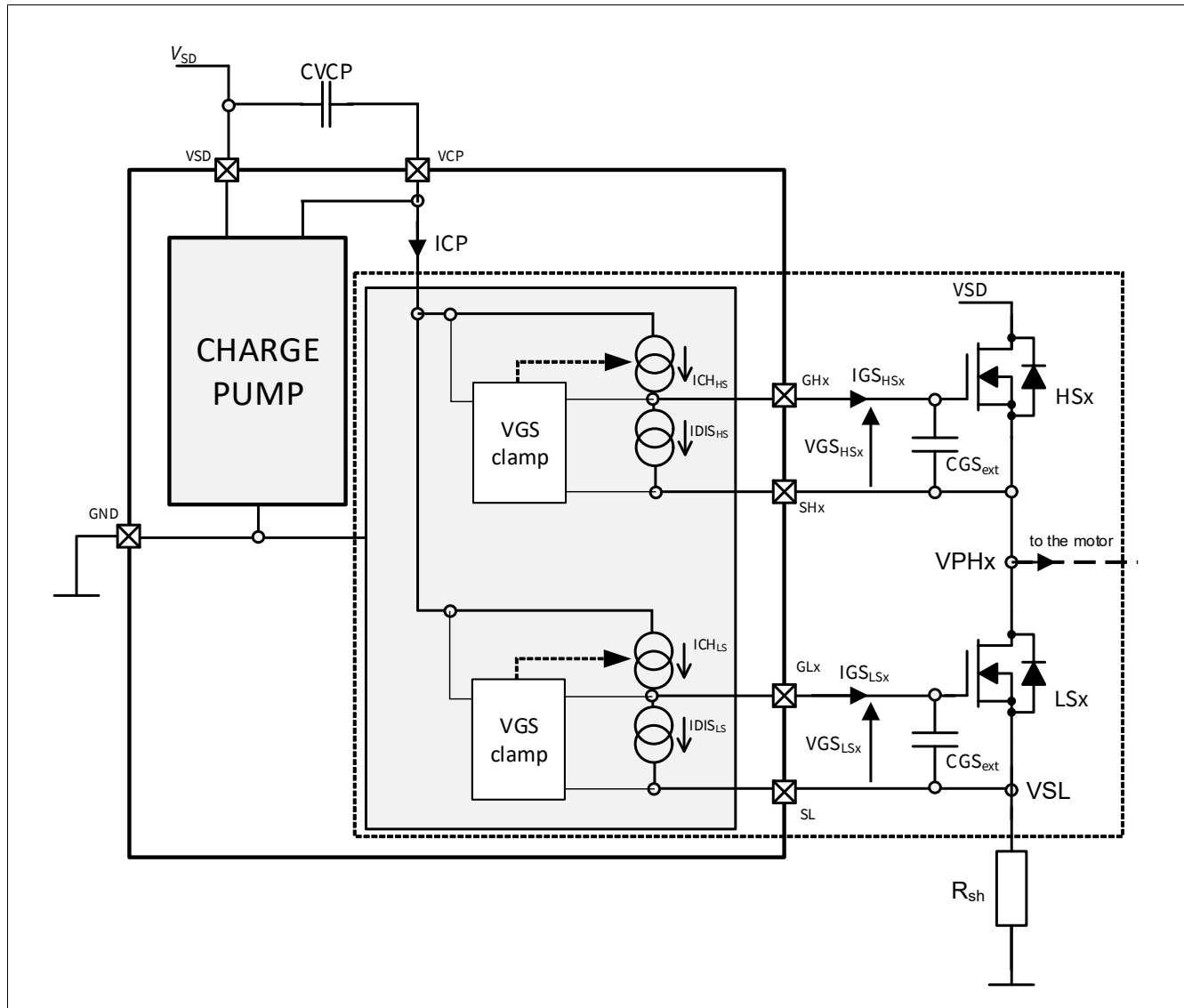

**Figure 18** Simplified BDRV block diagram with highlight on gate-source voltage clamping. Each gate driver block is repeated 3× in the TLE987x, while 2× in the TLE986x.

A calculation example is provided here below, where no capacitors are connected to the MOSFETs gates and FOC control with a 3-phase motor is used. For sake of simplicity, we can assume VGS to have the same value for HS and LS, as well as to be independent from ICP.

- Assumptions:

$$N_M = 2 \quad ; \quad f_{PWM} = 20 \text{ kHz} \quad ; \quad Q_{MOSFET} \cong 60 \text{ nC} \quad ; \quad V_{GS} = 12.5 \text{ V}$$

## Charge pump

- Considering VGS equal to 12.5 V, the gate charge should be consequently increased, since the 60 nC are estimated for VGS = 10 V.

$$Q_{\text{MOSFET}} \cong 60 \text{ nC} \times \frac{12.5 \text{ V}}{10 \text{ V}} = 75 \text{ nC}$$

- The current for each gate driver is equal to:

$$ICP_M = N_M \times f_{\text{PWM}} \times Q_{\text{MOSFET}} \cong 3 \text{ mA}$$

- The total ICP current is:

$$ICP = 3 \times (ICP_M + I_{\text{BIAS}}) \cong 15 \text{ mA}$$

Another calculation example is provided here below, where a capacitor is placed between gate and source, and no capacitor between gate and drain is connected. The control scheme is always FOC. For sake of simplicity, we can assume VGS and VGD to have the same value for HS and LS, as well as to be independent from ICP.

- Assumptions:

$$\begin{aligned} N_M &= 2 & ; & & f_{\text{PWM}} &= 20 \text{ kHz} & ; & & Q_{\text{MOSFET}} &= 60 \text{ nC} \\ VGS &= VGD = 12.5 \text{ V} & ; & & CGS_{\text{ext}} &= 1 \text{ nF} \end{aligned}$$

- The charge for each gate is then:

$$Q_M = 60 \text{ nC} \times \frac{12.5 \text{ V}}{10 \text{ V}} + 12.5 \text{ V} \times 1 \text{ nF} \cong 88 \text{ nC}$$

- The current for each gate driver is equal to:

$$ICP_M = N_M \times f_{\text{PWM}} \times Q_M \cong 3.5 \text{ mA}$$

- The total ICP current is:

$$ICP = 3 \times (ICP_M + I_{\text{BIAS}}) \cong 16.5 \text{ mA}$$

## Charge pump

### 7.3 Charge pump external capacitors design

The flying capacitors CCPS1 and CCPS2 boost the input voltage VSD to generate the output voltage VCP, while the output capacitor CVCP is acting as bulk capacitor. The selection of the values and type should consider the following requirements:

- **VCP voltage in steady state:** as shown in the [Equation \(7.1\)](#), the output voltage depends also on the value of the charge pump capacitors.
- **Voltage ripple:** the ripple of the flying capacitors can be expressed as:

(7.8)

$$V_{\text{ripple}} = \frac{I_{CP}}{f_{SW} \times C}$$

where C is the value of the capacitor. The voltage ripple of the output capacitor CVCP is equal to the one of the flying capacitors, but divided by 2.

- **Dynamic response:** the higher the value of the capacitors, the slower will be the start-up time and the response to load changes. In a typical TLE987x/6x application, this requirement is not critical.
- **Losses due to ESR** (Equivalent Series Resistance): the higher the value of the capacitors, the higher will be the ESR and so the losses. Using ceramic capacitors, the losses can be considered as not relevant in this application.
- **DC bias voltage:** ceramic capacitors exhibit lower capacitance values, when the applied voltage increases. According to the point of load and the desired capacitance value, the voltage rating should be adequately selected. For a typical application, 50 V capacitors are recommended.

Here a method is presented to select the charge pump capacitors:

1. Define the type of MOSFETs of the application.
2. Define the switching frequency  $f_{PWM}$  of the bridge driver.
3. Calculate the load current ICP, as described in the [Equation \(7.4\)](#).
4. Calculate the preliminary values of CCPS and CVCP using the [Equation \(7.8\)](#). As a rule, we can consider a maximum ripple of 0.5 V for the flying capacitors CCPS and 0.25 V for CVCP. Moreover, at least 50% higher capacitance should be taken into account of the DC bias.
5. Calculate  $R_{OUT\_AVG}$  using the [Equation \(7.2\)](#).
6. Calculate  $V_{DROD}$  using the [Equation \(7.3\)](#).
7. Calculate VCP voltage using the [Equation \(7.3\)](#).
8. Calculate the voltage VCP vs. VSD using the [Equation \(7.7\)](#), checking that the gates are driven with a sufficient voltage in the input voltage range VSD, as required by the application.

The recommended values are 220 nF for the flying capacitors (CCPS1 / CCPS2), and 470 nF for the output capacitor (CVCP). These values allow to have a VCP voltage sufficiently high within the nominal working conditions of the charge pump, as well as a low voltage ripple in the load current range.

## Charge pump

### 7.3.1 Calculation example

A calculation example is provided here below.

1. Identify the MOSFETs, for example: **IAUA120N04S5N014**.
2. Define the switching frequency:

$$f_{PWM} = 20 \text{ kHz}$$

3. Calculate ICP, considering  $V_{GS} = 12.5 \text{ V}$ ,  $N_M = 2$ , and no external capacitors connected to the gates:

$$ICP \cong 15 \text{ mA}$$

4. Calculate preliminary values for CCPS and CVCP, considering a charge pump frequency of 250 kHz and a voltage ripple of 0.4 V and 0.1 V for CCPS and CVCP respectively.

$$CCPS = 150 \text{ nF} \rightarrow +50\% \rightarrow 220 \text{ nF}$$

$$CVCP = 300 \text{ nF} \rightarrow +50\% \rightarrow 470 \text{ nF}$$

5. Calculate  $R_{OUT\_AVG}$ :

$$R_{OUT\_AVG} = 43 \text{ } \Omega$$

$$ICP \times R_{OUT\_AVG} \cong 0.65 \text{ V}$$

6. Calculate the voltage drop:

$$V_{DROP} = ICP \times R_{EQ} \cong 1.5 \text{ V}$$

7. Calculate VCP vs. VSD:

$$VCP - VSD \cong 2 \times VSD - 2.2 \text{ V}$$

8. Considering 8 V – 18 V as VSD voltage range, calculate the voltages VCP vs. VSD,  $V_{GS_{HS}}$  and  $V_{GS_{LS}}$ :

	VCP-VSD	VGS <sub>HS</sub>	VGS <sub>LS</sub>
<b>VSD = 18 V</b>	14 V	12.5 V	12.5 V
<b>12 V</b>	14 V	12.5 V	12.5 V
<b>10 V</b>	14 V	12.5 V	12.5 V
<b>8 V</b>	13.8 V	12.3 V	12.5 V

From the table, the minimum VGS voltage is equal to 12.3 V, so the MOSFETs can be correctly driven in every condition.

## Current Sense Amplifier

### 8 Current Sense Amplifier

The Current Sense Amplifier (CSA) is an analog circuit capable for amplifying a differential input voltage by a programmable gain  $G$ .

Despite being actually a voltage amplifier, it is specifically designed for shunt current measurements. For this purpose, the pins OP2 and OP1 are connected to the terminals of a suitably designed shunt resistor, through which the current to be measured flows, and a filter network.

#### 8.1 Block diagram

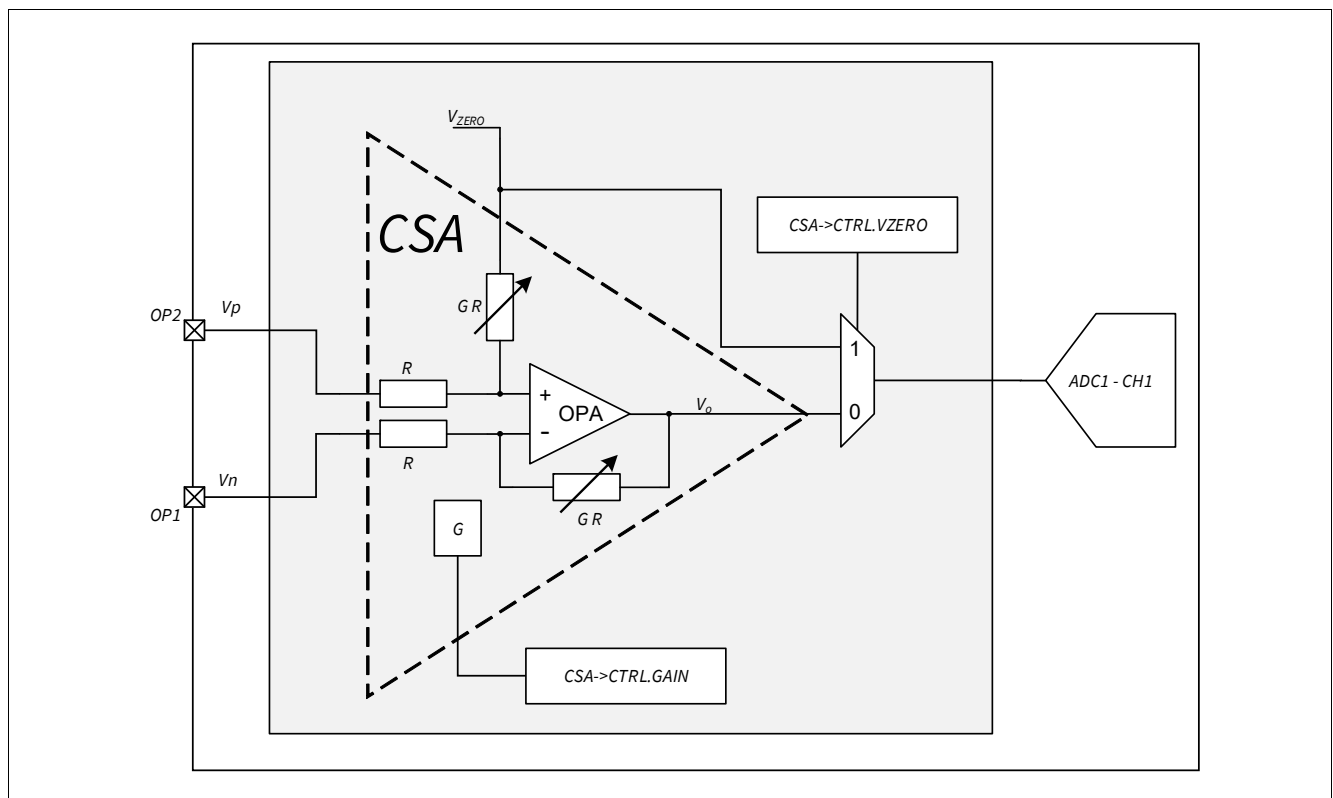


Figure 19 CSA block diagram and application schematic for shunt current measurement

## 8.2 Functional description

**Figure 19** shows the block diagram of the CSA together with the registers and logic related to its setup. The amplifier is built around an OPA configured as a differential amplifier with an output voltage offset. The amplifier's output is permanent connected to the ADC1 channel 1, which means it is loaded by a fixed impedance. It is an integrated closed loop amplifier and it can be used only as such. What follows will describe the entire CSA configuration and behavior.

### 8.2.1 DC characteristics

The **differential input voltage** is defined as:

(8.1)

$$V_{id} = OP2 - OP1 = V_p - V_n$$

The **ideal DC transfer characteristics** can be calculated as:

(8.2)

$$\begin{aligned} V_o &= V_{ZERO} + G V_{id} \\ V_{ZERO} &= 0.4 V_{AREF} \\ V_{id} = 0 &\rightarrow V_o = V_{ZERO} \end{aligned}$$

where  $V_{ZERO}$  is the **output voltage offset** and  $V_{AREF}$  is the reference voltage of ADC. If, for example,  $V_{AREF}$  is generated by the internal reference voltage generator, its nominal value is 5 V. As a consequence  $V_{ZERO} = 2$  V, which allows the ADC1 channel 1 to measure positive and negative values of  $V_{id}$ .

The **linear output voltage range** of the amplifier is (see P\_13.1.4 of the datasheet):

(8.3)

$$\min, \max\{V_o\} = V_{OUT} = V_{ZERO} \pm 1.5 V$$

With the use of the internal  $V_{AREF}$  generator,  $V_o$  can assume any value between 0.5 V and 3.5 V.

The  $V_o$  range limits the **differential linear input range**, which also depends on the gain setting according to (see P\_13.1.1 of the datasheet):

(8.4)

$$\min, \max\{V_{id}\} = V_{IX} = \pm 1.5 V / G$$

Outside these ranges, the CSA characteristics are not linear and therefore undefined.

## Current Sense Amplifier

Because it is not an ideal circuit, the OPA exhibits **an input offset**  $V_{OS}$ . Because of this, the output voltage can be expressed by:

(8.5)

$$V_o = V_{ZERO} + G (V_{id} \pm V_{OS})$$

$$V_{id} = 0 \rightarrow V_o = V_{ZERO} \pm G V_{OS} = V_{ZERO} \pm V_{OOS}$$

This implies that the direct measurement of  $V_{ZERO}$  by means of CSA->CTRL.VZERO = 1 will differ from the value of  $V_o$  with  $V_{id} = 0$  with CSA->CTRL.VZERO = 0. This difference equals to the **output offset**  $V_{OOS}$  (see parameter P\_13.1.17). These measurements can be used to calculate this difference in the application software and to compensate the offset.

The **common mode input voltage** is defined as:

(8.6)

$$V_{icm} = \frac{OP2 + OP1}{2} = \frac{V_p + V_n}{2}$$

Considering also the contribution of  $V_{icm}$  and **the common mode rejection ratio** DC\_CMRR (see parameter P\_13.1.8 for grade 1 in conjunction with P\_13.1.27 for grade 0 devices), the **DC characteristics** can be expressed as:


(8.7)

$$V_o = V_{ZERO} \pm V_{OOS} + G (V_{id} + V_{icm} / CMRR_{lin})$$

$$CMRR_{lin} = 10^{\frac{DC\_CMRR}{20}}$$

**Figure 20** shows a graphical representation of the **differential DC characteristics** and the input/output range.

## Current Sense Amplifier

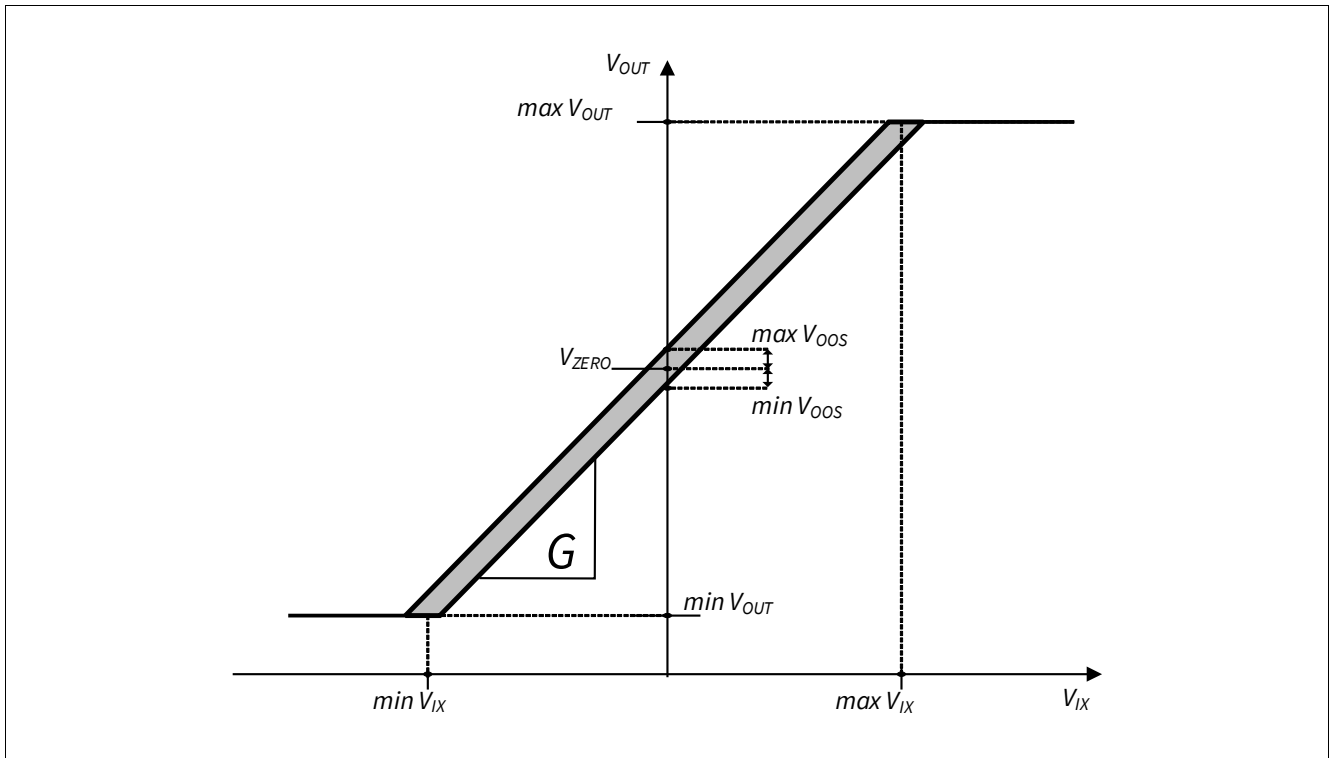

**Figure 20** Differential DC characteristics

### 8.2.2 AC characteristics

The CSA can be modeled as a three-ports network with two input ports and one output port, as shown in [Figure 21](#). The two input ports represent OP2 and OP1, while the output port represents  $V_{OUT}$ . Voltages for all three ports refer to the ground potential GND.

By considering the specific characteristics of the CSA, the three-port network can be expressed as:

(8.8)

$$\begin{cases} v_o = A_d v_{id} + A_{cm} v_{icm} \\ v_p = Z_{pp} i_p + Z_{pn} i_n \\ v_n = Z_{np} i_p + Z_{nn} i_n \end{cases}$$

where:

(8.9)


$$\begin{cases} v_{id} = v_p - v_n \\ v_{icm} = \frac{v_p + v_n}{2} \end{cases}$$

## Current Sense Amplifier

The first equation in [Equation \(8.8\)](#) represents the output behavior, while the other two represent the input behavior of the CSA. The nominal value of the input impedances can be expressed as:

(8.10)

$$\begin{aligned} Z_{pp} &= \left. \frac{v_p}{i_p} \right|_{i_n=0} = (G+1)R & Z_{pn} &= \left. \frac{v_p}{i_n} \right|_{i_p=0} = 0 \\ Z_{np} &= \left. \frac{v_n}{i_p} \right|_{i_n=0} = GR & Z_{nn} &= \left. \frac{v_n}{i_n} \right|_{i_p=0} = R \end{aligned}$$

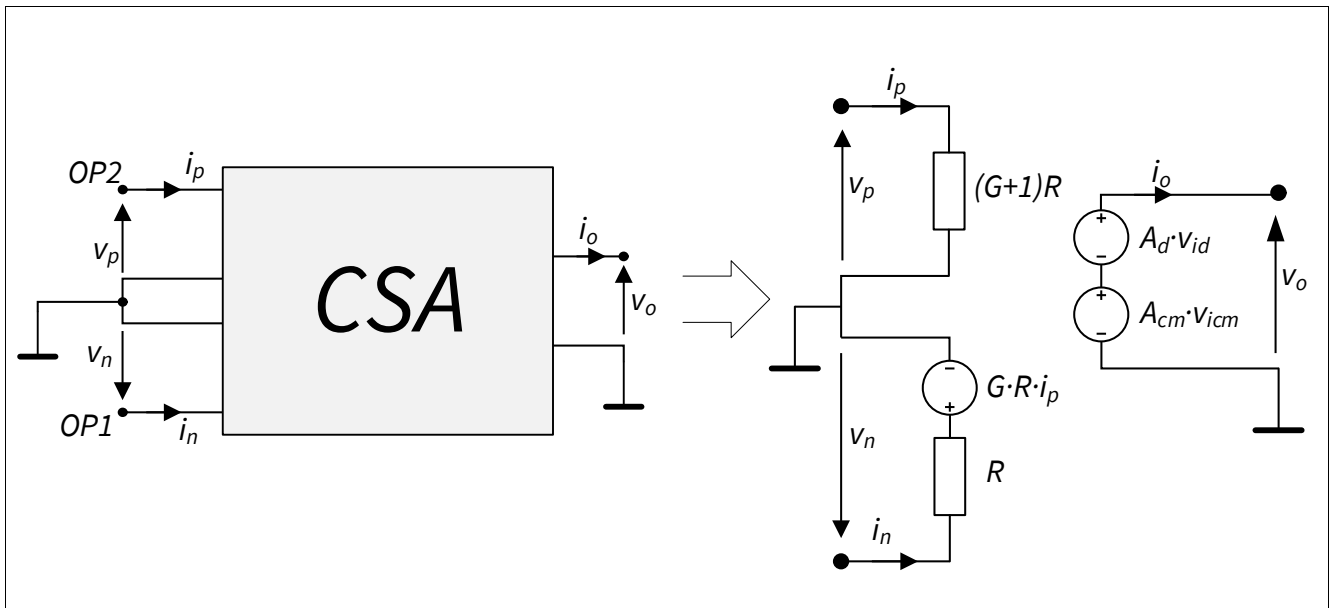

**Figure 21** CSA AC simplified three-ports model

**Figure 21** shows a schematic representation of the input equations and its impedances. This representation together with the equations are necessary to design the external current-sensing and filtering network.

The resistors  $R$  have nominal values of 1.25 k $\Omega$  (see P\_13.1.25 of the datasheet), and  $G$  changes according the programmed gain.

The closed-loop nature of the CSA ensures the stability is guaranteed in any application condition. The **open-loop transfer function** of the CSA together with its **gain and phase margins** are designed and fixed for each  $G$  gain configuration. Therefore, only the **closed-loop** transfer functions are described here.

The **DC common mode gain** can be derived from the CMRR as:

(8.11)

$$A_{cm} = \frac{A_d}{CMRR}$$

## Current Sense Amplifier

The typical **AC differential gain transfer function** is shown in **Figure 22** and defined as:


(8.12)

$$A_d(s) = \frac{v_o(s)}{v_{id}(s)}$$

A simplified analytical expression for each transfer function can be used in order to identify the typical frequency and time-domain parameters. A dominant-pole approximation of  $A_d(s)$  is:

(8.13)

$$A_d(s) = \frac{v_o(s)}{v_{id}(s)} \approx \frac{G}{\left(\frac{s}{\omega_p} + 1\right)^4}$$

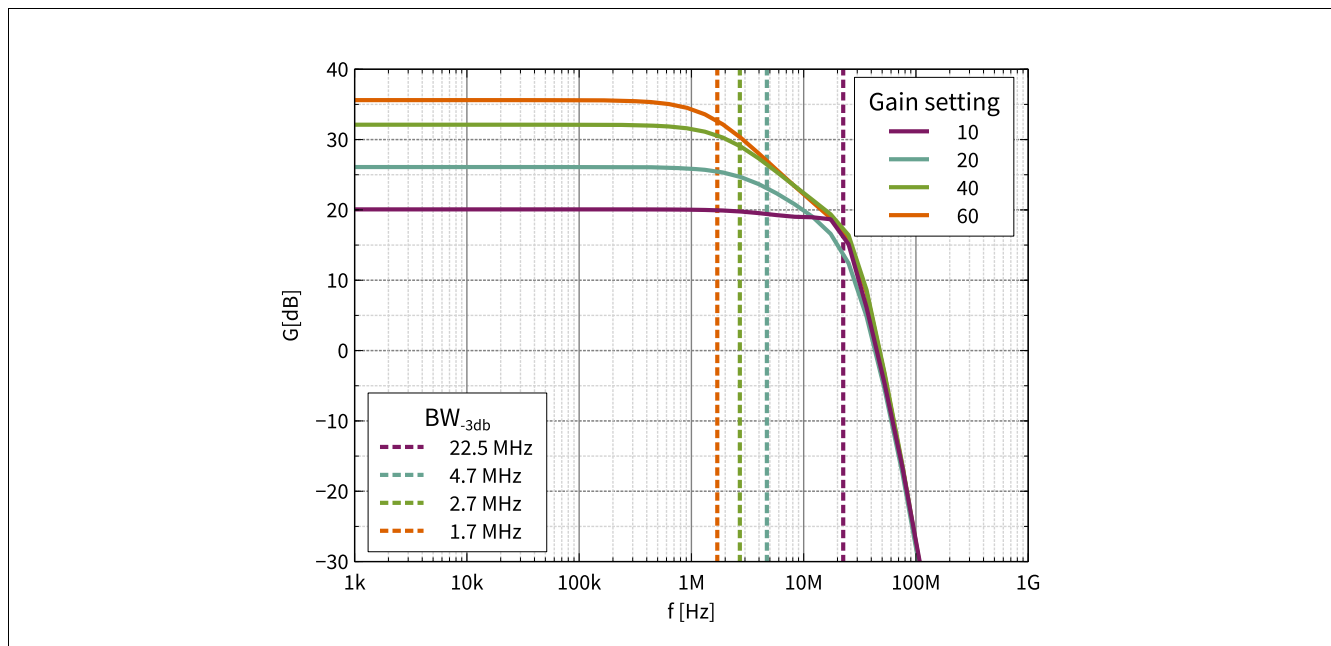

**Figure 22 AC differential gain transfer function**

The typical values of  $\omega_p$  for each gain setting are shown in **Table 10**. Being a 4<sup>th</sup>-order transfer function, its step response in the time domain has a quite complex analytical expression. However, we can still define the time constant  $\tau_p$  and its relation to the settling time  $T_s$ :

(8.14)

$$\tau_p = \frac{1}{\omega_p} \quad T_s \approx 9 \tau_p$$

The **settling time**  $T_s$  is defined as the time between the instant when the step is applied at  $V_{id}$  and the instant in which  $V_o$  remains confined within  $\pm 2\%$  of its final value. **Table 10** shows the values of the estimated typical  $T_s$  and  $\tau_p$  for each gain setting.

**Table 10** Typical values for gain settings


Gain [V/V]	10	20	40	60
$\omega_p$ [Mrad/s]	50	27	17	12
$\tau_p$ [ns]	20	37	57	84
Settling time [ns]	185	330	520	760

### 8.3 Application hints

The CSA is designed to measure the differential voltage across a shunt resistor through which the current to be measured flows. A typical circuit implementation of the sensing network is shown in [Figure 23](#).

Because of the parasitic inductance introduced by the shunt resistor and the PCB traces, the signal across the shunt resistor presents spikes and ringings. This effect must be compensated by a filtering network as shown in [Figure 23](#).

[Chapter 8.3.1](#) and [Chapter 8.3.2](#) describe a procedure for designing the shunt resistor and the filter network.

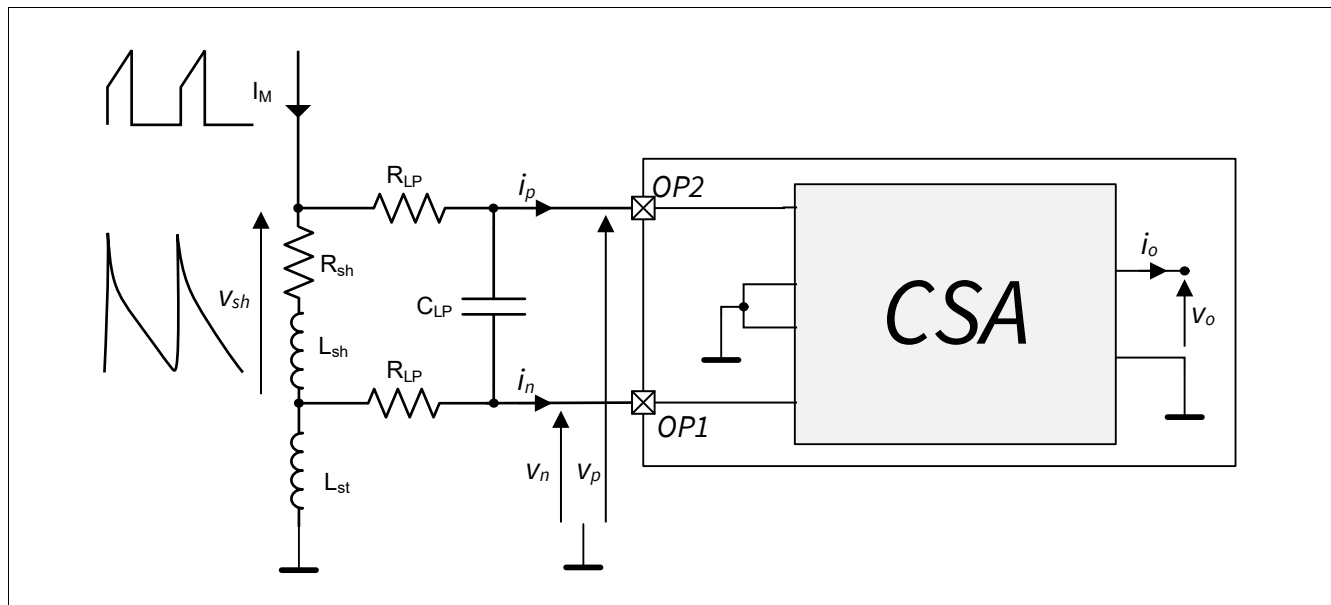

**Figure 23** Typical circuit implementation

#### 8.3.1 Shunt resistor selection

In a typical application, the input pins OP2 and OP1 are connected to an external shunt resistor so that:

(8.15)

$$V_{id} = R_{sh} I_M$$

$$V_o = V_{ZERO} + G R_{sh} I_M$$

where  $I_M$  is the current to measure, and  $R_{sh}$  is the nominal resistance of the shunt resistor. This equation represents the ideal DC behavior of the CSA, so it is only valid once all the dynamics of the system are eliminated. However, it is still a valid design equation for the choice of  $R_{sh}$  and  $G$ .

## Current Sense Amplifier

Indeed, because of the limited output voltage range of the CSA, one has to consider the behavior under maximum current:

(8.16)

$$V_o^{\max} = V_{\text{ZERO}} + 1.5 \text{ V} > V_{\text{ZERO}} + G R_{\text{sh}} I_M^{\max}$$

This leads to the **1<sup>st</sup> design equation**:

(8.17)

$$R_{\text{sh}} < R_{\text{sh}}^{\max} = \frac{1.5 \text{ V}}{G I_M^{\max}}$$

*Note: This equation should be used so that  $R_{\text{sh}}$  is as close as possible to its maximum limit in order to take the greatest advantage of the  $V_o$  range.*

Since the output voltage is eventually measured by the ADC1 channel 1, one has to consider the relation between the current resolution  $\Delta I_M$  and the ADC1 resolution  $\Delta V_o$ :

(8.18)

$$\Delta V_o = \frac{V_{\text{AREF}}}{2^{10} - 1} < G R_{\text{sh}} \Delta I_M^{\min}$$

Using the internal reference leads to  $\Delta V_o \approx 4.5 \text{ mV}$ . From this condition, the **2<sup>nd</sup> design equation** derives:

(8.19)

$$R_{\text{sh}} > R_{\text{sh}}^{\min} = \frac{\Delta V_o}{G \Delta I_M^{\min}}$$

*Note: This equation should be used so that  $R_{\text{sh}}$  is as far as possible to its minimum limit.*

Another effect to consider is the power dissipation of the shunt resistor:

(8.20)

$$P_{D_{\text{sh}}} = R_{\text{sh}} I_{M_{\text{RMS}}}^2$$

## Current Sense Amplifier

In order to limit the power dissipation to a certain value  $P_{Dsh}^{max}$ , the **3<sup>rd</sup> design equation** should be applied:

(8.21)

$$R_{sh} < R_{sh}^D = \frac{P_{Dsh}^{max}}{I_{M_{RMS}}^2}$$

The following **considerations** are also relevant when selecting a shunt resistor:

1. The higher the gain, the lower the bandwidth, as seen in **Figure 22**.
2. The values of commercial current sensing resistors are discrete and limited.
3. More shunt resistors in parallel are possible to increase the total maximum power dissipation.

### Design example: Selecting a shunt resistor

- $I_M(t)$  is a square-wave current with:
  - $I_M^{max} = 10 \text{ A}$
  - $I_M^{min} = 0 \text{ A}$
  - Duty cycle = 80%
- $V_{AREF} = 5 \text{ V}$  (internal)
- $\Delta I_M^{min} = 100 \text{ mA}$
- $P_{Dsh}^{max} = 1 \text{ W}$

To find the suboptimal shunt resistance, the best approach is to consider the three design equations for each gain setting  $G = \{10, 20, 40, 60\}$ :

1. From the 1<sup>st</sup> design equation (**Equation (8.17)**):

(8.22)

$$R_{sh} < R_{sh}^{max} = \frac{1.5 \text{ V}}{G \cdot 10 \text{ A}} = \{15; 7.5; 3.75; 2.5\} \text{ m}\Omega$$

2. From the 2<sup>nd</sup> design equation (**Equation (8.19)**):

(8.23)

$$R_{sh} > R_{sh}^{min} = \frac{4.5 \text{ mV}}{G \cdot 100 \text{ mA}} = \{4.5; 2.25; 1.225; 0.75\} \text{ m}\Omega$$

3. From the 3<sup>rd</sup> design equation (**Equation (8.21)**):

(8.24)

$$R_{sh} < R_{sh}^D = \frac{1 \text{ W}}{80 \text{ A}^2} = 12.5 \text{ m}\Omega$$

## Current Sense Amplifier

**Figure 24** shows a graphical representation of the design equations above. It shows that any gain setting can fit the case, given that  $R_{sh}$  falls in the selection area.


On the base of this analysis and considerations **1.** and **2.**, a suboptimal choice for this use case would be a 7-mΩ resistor with a gain setting  $G = 20$ . This will lead to the following actual values:

(8.25)

$$V_o^{\max} = 2 + 20 \cdot 7 \text{ m}\Omega \cdot 10 \text{ A} = 3.4 \text{ V}$$

$$\Delta I_M = \frac{4.5 \text{ mV}}{20 \cdot 7 \text{ m}\Omega} \approx 32.2 \text{ mA}$$

$$P_{D_{sh}} = 7 \text{ m}\Omega \cdot 80 \text{ A}^2 = 560 \text{ mW}$$

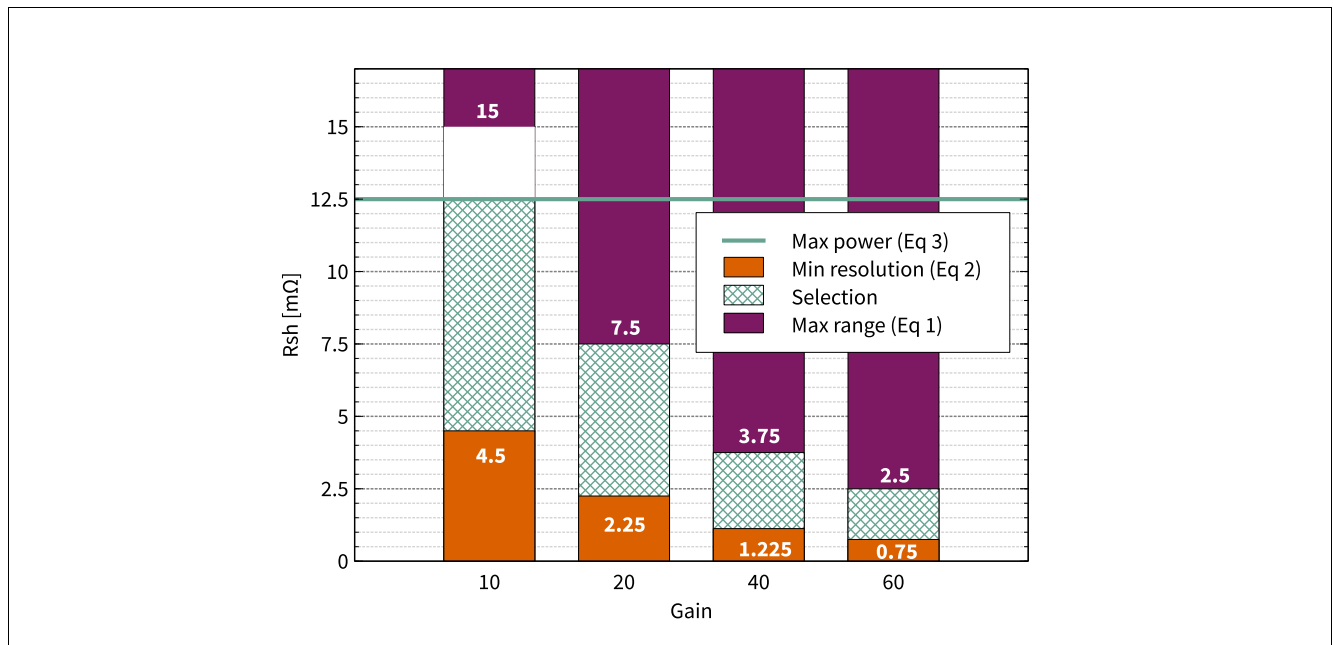

**Figure 24** Graphical representation of the design example values

## Current Sense Amplifier

### 8.3.2 Filter network selection

The goal of the filter network design is to shape the dynamics of the CSA input voltage so that it is the best representation of the measured current. In practice, the design goal is to choose the values of the low pass filter components  $R_{LP}$  and  $C_{LP}$  that damp the ringings caused by the parasitic inductance  $L_{sh}$ .

$V_o$  as function of  $I_M$  needs to be expressed. We could do this in the time domain, but the AC analysis in the frequency domain can simplify the design procedure. The total CSA gain transfer function can be defined as:

(8.26)

$$H(s) = \frac{v_o(s)}{i_M(s)}$$


Further  $H(s)$  can be broken down as a function of the CSA differential and common mode gains from the input pins OP2 and OP1 to the input of the ADC1:

(8.27)

$$H(s) = \frac{v_o(s)}{i_M(s)} = \frac{A_d(s)v_{id}(s) + A_{cm}(s)v_{icm}(s)}{i_M(s)} \approx \frac{v_{id}(s)}{i_M(s)} A_d(s)$$

*Note: The above simplification is possible because both the common-mode input signal and gain are negligible compared to the differential ones.*

In the frequency domain, the design goal mentioned above translates into obtaining a response as flat as possible, ideally a constant response across the whole frequency spectrum. As known  $A_d(s)$  has a flat gain, but within limited bandwidth (see [Figure 22](#) and [Table 10](#)), so the effect of the shunt and filter network has to preserve this level of fidelity.

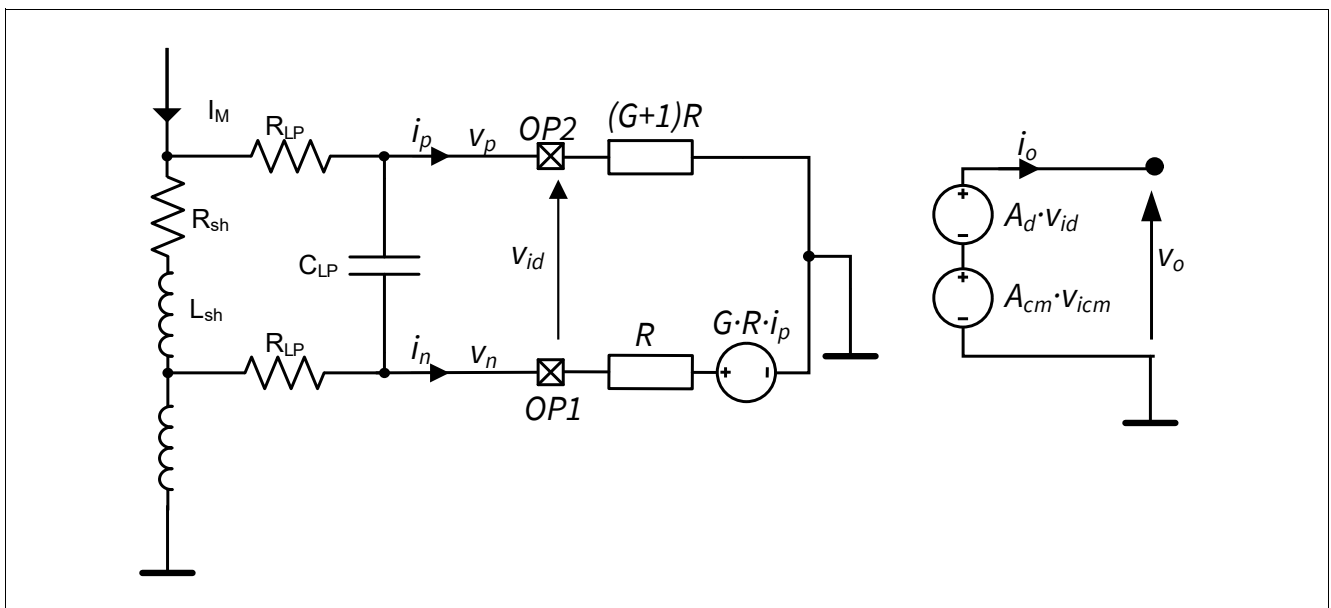

**Figure 25 CSA input filter and graphical representation of the CSA impedances**

## Current Sense Amplifier

In conclusion, the best dynamic performance obtainable (without introducing any additional reactive device) is the one of the CSA. This requires:

(8.28)

$$Z_T(s) = \frac{v_{id}(s)}{i_M(s)} = R_{sh}$$

This will be eventually the condition for calculating one of the design equations.

The analytical calculation of  $Z_T(s)$  from the schematic in **Figure 25** leads to:

(8.29)

$$Z_T(s) = \frac{v_{id}(s)}{i_M(s)} = R_{sh} \frac{F \left( 1 + \frac{s L_{sh}}{R_{sh}} \right)}{s^2 C_{LP} L_{sh} F + s \left( \frac{L_{sh}}{2 R} + C_{LP} (R_{sh} + 2 R_{LP}) \right) F + 1}$$

$$F = \frac{2 R}{2 R + R_{sh} + 2 R_{LP}}$$

For  $s = 0$ , that means in DC regime, the transimpedance can be expressed as:

(8.30)

$$Z_T(s)|_{s=0} = R_{sh} F$$

This means that the factor  $F$  introduces a DC error. This factor indeed represents the portion of the DC current  $I_M$  that flows through the low pass filter resistors  $R_{LP}$  and the input stage of the CSA (because of its non-infinite input resistance  $R$ ).

This error can be minimized by considering that  $R_{sh} \ll R$  and by imposing the **1<sup>st</sup> design equation**:

(8.31)

$$R_{LP} < \frac{R}{p}$$

This condition leads to a DC gain error of:

(8.32)

$$\text{Err}Z_T\% = \frac{R_{sh} - R_{sh} F}{R_{sh}} < \frac{1}{1 + p} \%$$

## Current Sense Amplifier

For example, for  $p = 100$  the error would be less than 1%. It is therefore good practice to choose a value of  $R_{LP}$  between  $1\ \Omega$  and  $15\ \Omega$ .

The following considerations can then be applied:

- If  $p = 100$  then  $F \approx 1$
- $R_{sh} \ll R_{LP}$
- $L_{sh}/2R \approx 0$

These assumptions will lead to a final simplified transfer function:

(8.33)

$$Z_T(s) = \frac{v_{id}(s)}{i_M(s)} \approx R_{sh} \frac{1 + \frac{s L_{sh}}{R_{sh}}}{s^2 C_{LP} L_{sh} + s C_{LP} 2R_{LP} + 1} = R_{sh} \frac{1 + \frac{s}{\omega_z}}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1}$$

The parasitic inductance introduces a 2<sup>nd</sup>-order dynamics and a zero in the filter transfer function. The zero will boost the transfer function, increasing the high frequency content of the step response. The poles instead, depending on the filter values, could:

- Introduce a resonance ( $Q > 1/\sqrt{2}$ ), which will result in a fast, but overshooting step response.
- Split, one in low frequency and one at high frequency ( $Q < 1/\sqrt{2}$ ) obtaining a slow, but smooth step response.

None of these effects is desirable because the goal is to obtain a flat response (at least within the bandwidth of the CSA). A third option would be to try to cancel the dynamic of the zero with one of the poles. Partial cancelation of the zero is indeed possible when:

(8.34)

$$C_{LP} = \frac{L_{sh}}{2 R_{LP} R_{sh}}$$

This is the **2<sup>nd</sup> design equation**. The pole/zero cancellation is never perfect in practice, because of the uncertainty and variation of the passives values. So, this method gives the suboptimal value of  $C_{LP}$  that maximizes the bandwidth of the filter.

This design equation has to be considered as a starting point recommendation for the customer's design. The designer shall make use of the analytical tools shown in this chapter to choose the  $C_{LP}$  value considering the design's specifications.

## Current Sense Amplifier

In **Figure 26** one can observe the effect of 4 different  $C_{LP}$  values on the normalized transfer functions and step responses:

(8.35)

$$\frac{H(s)}{G R_{sh}} \quad ; \quad \frac{Z_T(s)}{R_{sh}}$$

### 8.3.3 Conclusion

When all design equations are used to select the current sensing and filter network, the transfer function from measured current to output of the CSA can be simplified as:

(8.36)


$$H^{opt}(s) = \frac{v_o(s)}{i_M(s)} = Z_T^{opt}(s) A_d(s) \approx \frac{R_{sh}}{1 + s C_{LP} 2 R_{LP}} \frac{G}{\left(\frac{s}{\omega_p} + 1\right)^4}$$

This means that:

- The DC error introduced by the finite CSA input impedance  $R$  is minimized.
- The 2<sup>nd</sup>-order dynamics introduced by the sensing resistor parasitic inductance  $L_{sh}$  is tamed.

The speed of the signal is mainly affected by the CSA bandwidth. As shown in **Table 10**, the typical settling time depends on the gain setting  $G$ . **Figure 26** shows that the CSA bandwidth is capable to settle within 800 ns typically for the highest gain (lowest bandwidth) setup. In a motor control with 20 kHz PWM, 800 ns represents a duty cycle of 1.6%. So for applications where very high precision and fast response is needed by the current sensing, it is suggested to setup the CSA (and design the passives) for the lowest gain possible.

Current Sense Amplifier

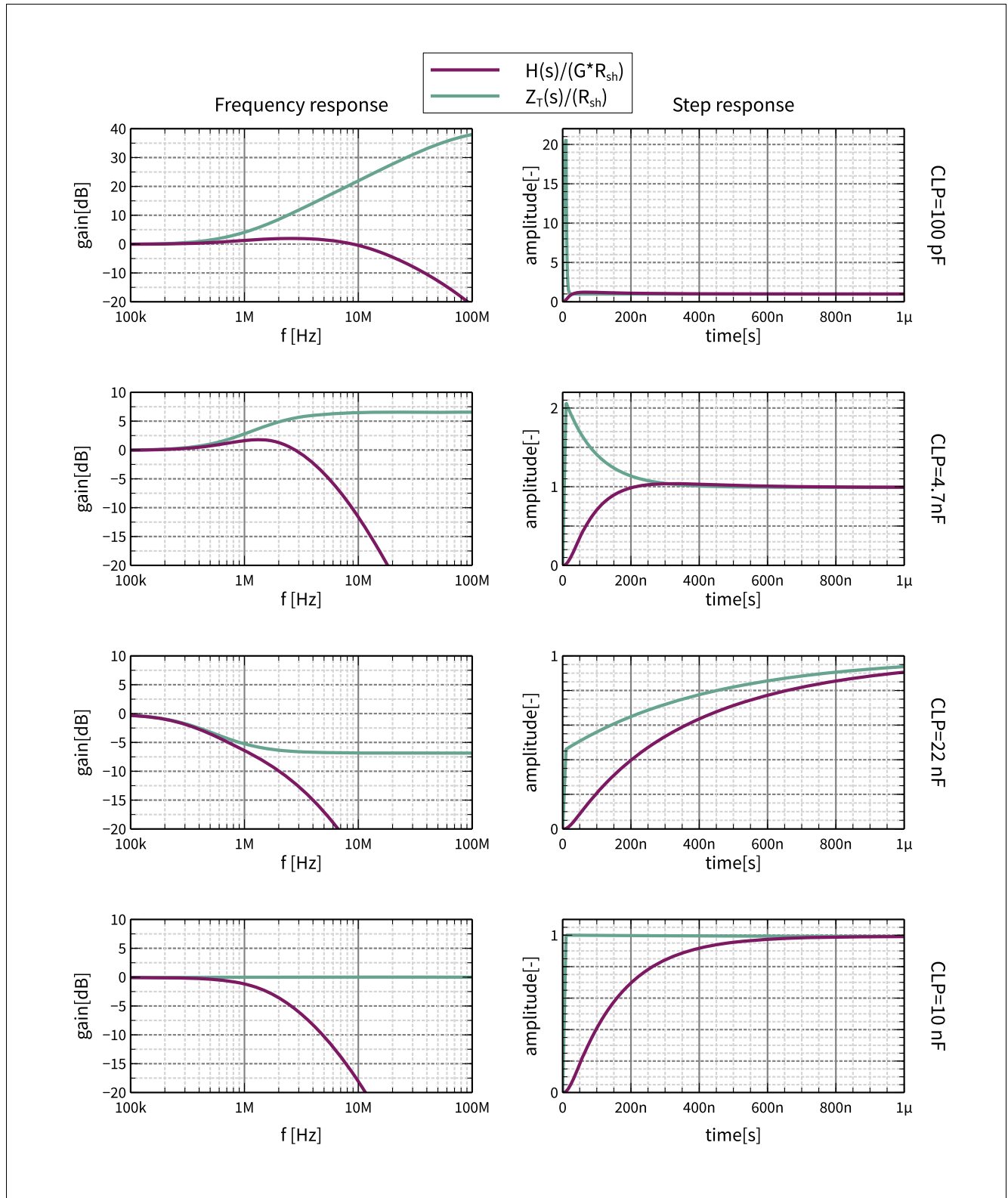

**Figure 26** Frequency and step response of the transfer functions  $Z_T(s)$  and  $H(s)$  with different values of  $C_{LP}$  and the following values:  $L_{sh} = 1 \text{ mH}$ ,  $R_{sh} = 5 \text{ m}\Omega$ ,  $R_{LP} = 10 \text{ }\Omega$ ,  $G = 60$ . The last value,  $10 \text{ nF}$ , is the suboptimal value that satisfies the 2<sup>nd</sup> design equation

## SWD (Serial Wire Debug) interface circuitry

### 9 SWD (Serial Wire Debug) interface circuitry

The SWD interface is used to download code to the embedded Power IC or to debug the chip. This chapter explains how to implement the circuitry around the chip to achieve a successful SWD connection.

#### 9.1 Description of the SWD interface

The SWD interface provides a debug port for severely pin limited packages, such as may be used for small package microcontrollers, but also for complex ASICs where limiting the pin count is critical and can be a critical factor for the device cost.

As SWD interface the TLE987x uses the pins TMS (data) and P0.0 (clock). In the evaluation boards, the signals are routed through a 5 × 2 pinheader (SWD connector). The following implementation explains the connection between Embedded Power IC and the SWD interface.


#### 9.2 Implementing an SWD interface connection to TLE987x/6x

The SWD interface can be directly connected to chips of the TLE987x/6x families. **Figure 27** shows the interconnections between the Embedded Power device and the SWD connector.

External pull-up or pull-down resistors are not needed because internal pull-down resistors are present.


The GND for the SWD connector is the digital GND of the TLE987x/6x (pin 19).

A ceramic capacitor from RESET pin to GND can be placed in order to improve immunity from transients. The recommended value of the capacitor is 1 nF. If this capacitor is used, a blanking time of 31  $\mu$ s in the Reset Blind Time Register (CNF\_RST\_TFB) has to be configured.

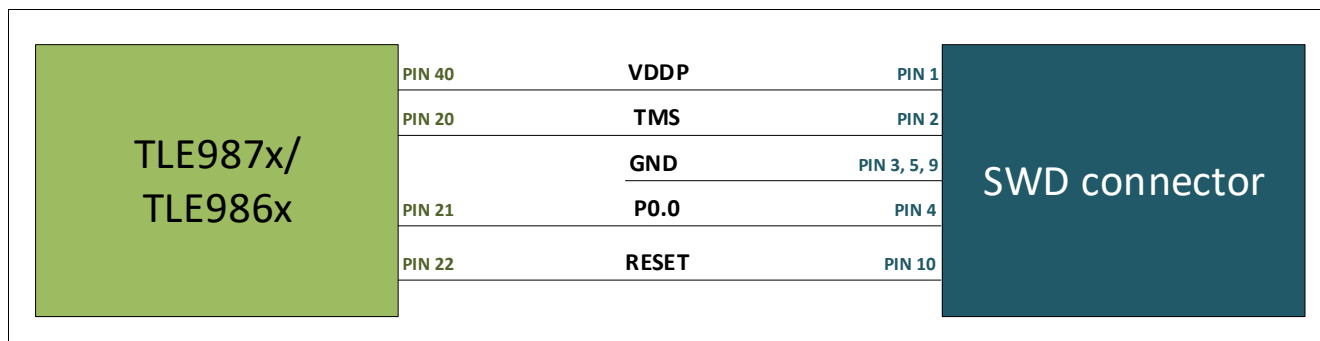

**Figure 27** SWD connection to the TLE987x and TLE986x device

On the SWD interface of the **TLE9879 EvalKit** and **TLE9869 EvalKit**, the pin 9 is used to deactivate the onboard debugging circuit. In a typical implementation, this pin is used as GND. The pinout is shown in **Figure 28**.

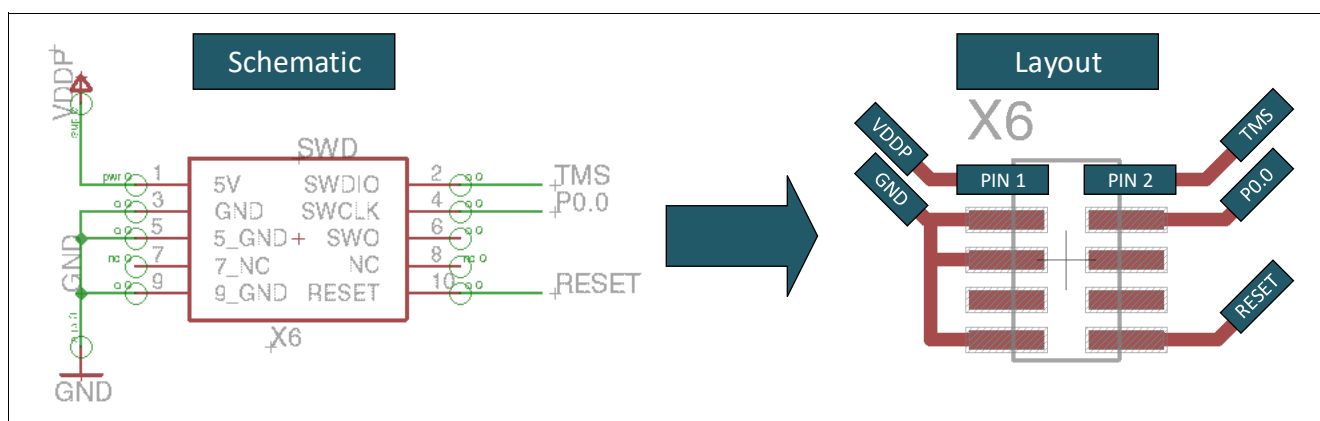

**Figure 28** SWD interface implementation for an application

## Unused pins

### 10 Unused pins

**Table 11** shows the recommendations for the TLE987x/6x pins, in case they are not used in the application. The GND digital pins are pin 19 and pin 28, while the GND analog is pin 39.

**Table 11 Connecting unused pins**

Type	Pin number	Recommendation 1 (if unused)	Recommendation 2 (if unused)
MON	14	GND analog/digital	open + configured internal PU/PD
GPIO	15, 16, 17, 18, 21, 23, 24, 25, 26, 27, 31, 32, 35	GND analog/digital	external PU/PD or open + configured internal PU/PD
TMS	20	open	
RESET	22	open	
P2.0 / XTAL1	29	GND analog/digital	
P2.2 / XTAL2	30	open	
VAREF	34	open (VAREF disabled)	
CSA	36, 37	open (CSA disabled)	
VDDEXT	45	open (VDDEXT disabled)	
LIN	48	open	

## 11 EMI recommendation

In this chapter general recommendations are provided regarding PCB layout, as well as some specific hints for microcontrollers and MOSFET bridge drivers.

### 11.1 Recommendations for optimized PCB layout

Electromagnetic interference (EMI) is mainly radiated by the PCB and the connected cables. In fact, cables are very efficient antennas, especially for common-mode currents. Loops on the PCB are regarded as good emitting antennas. Loops inside an IC are considered to be small compared to the external loops on PCB and cabling. EMI from the IC can be neglected in most cases.

#### 11.1.1 Placement of the connectors

Having connectors on both sides of the PCB might cause high emissions. A good PCB design should place all connectors on the same side.

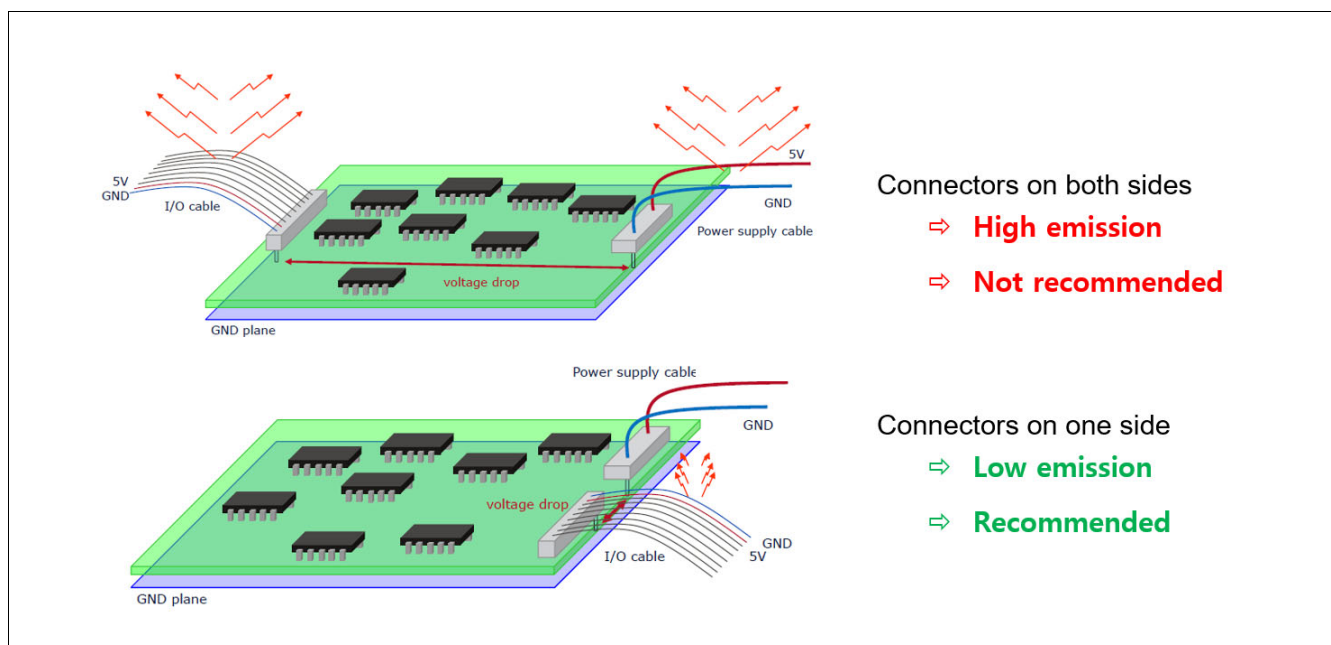


Figure 29 Placement of the connectors

#### 11.1.2 Floor-planning the PCB

For the placement of components, the following rules should be considered:

- All components from one group should be located together (power, digital, analog, supply, and so on).
- Connectors should all be placed on the same side.
- Susceptible parts should be placed away from noisy parts (power, digital, analog).
- Parts that generate noise should be close to a connector.
- Route all traces to the components in each zone as if this zone had its own ground plane.
- For simplicity and clarity reasons, number the components in each zone in the same way (for example, analog = 100, digital = 200, power = 300, and so on).

EMI recommendation

### 11.1.3 Routing the power supply traces

Wiring loops on the PCB should be as small as possible.

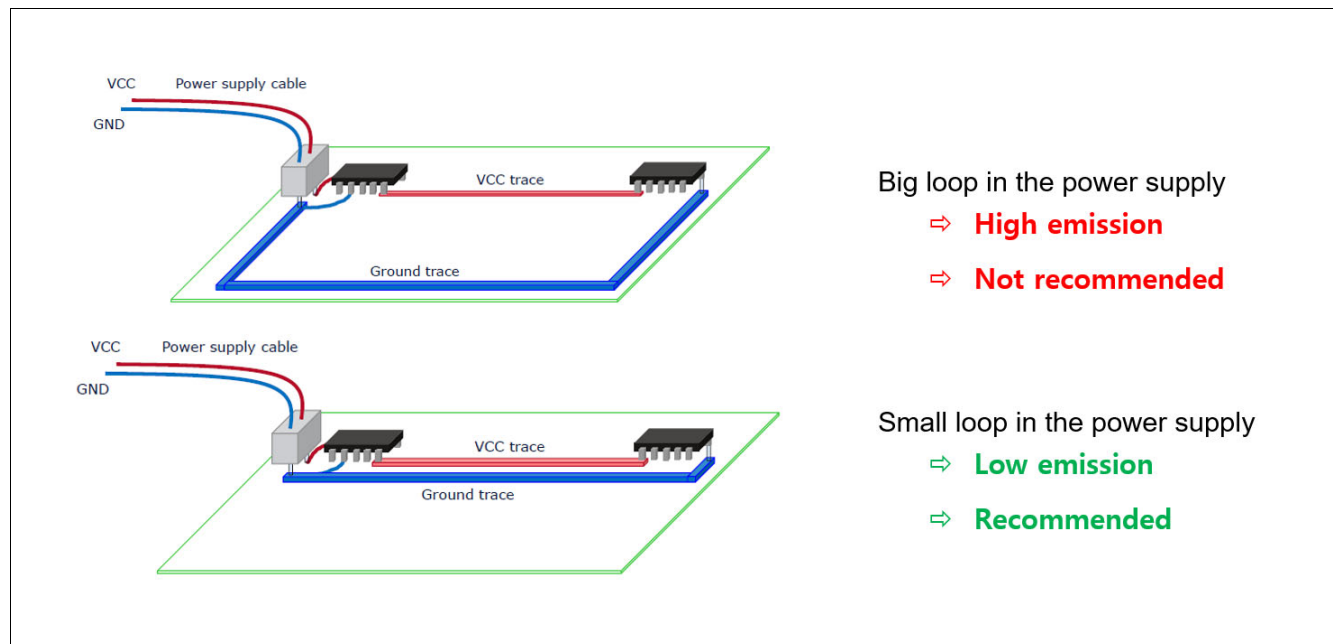
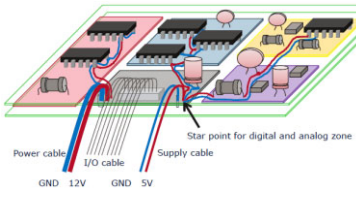
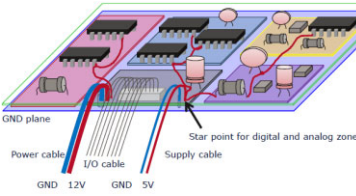
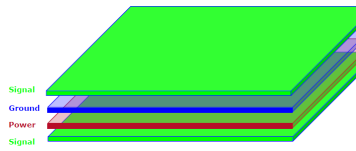
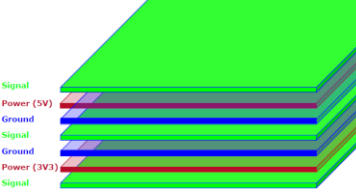


Figure 30 Routing the power supply traces

**EMI recommendation**

### 11.1.4 Number of PCB layers

**Table 12 Rules for different PCB types**

<p>Two layer PCB (no ground plane)</p>		<ul style="list-style-type: none"> <li>• Keep the loop areas that are formed by ground and power supply traces as small as possible.</li> <li>• Route power supply traces always together (parallel, next to each other) starting from once central star point and spreading into each individual zone.</li> <li>• Do not mix the supplies of different zones.</li> <li>• Fill free areas with ground.</li> </ul>
<p>Two layer PCB (solid ground plane)</p>		<ul style="list-style-type: none"> <li>• Use a solid ground plane.</li> <li>• Components of one zone should be supplied by only one supply from a central star point.</li> <li>• Do not mix the supplies of different zones.</li> <li>• Supply traces cannot have loops; use a tree structure instead.</li> </ul>
<p>Multilayer configuration (4 layers)</p>		<ul style="list-style-type: none"> <li>• Keep ground and power supply layers next to each other. This provides a good decoupling capacitor for free.</li> <li>• Avoid slots in ground and power supply planes (for example, by routing signal traces within these planes, vias in a row, through hole connectors).</li> </ul>
<p>Multilayer configuration (more than 4 layers)</p>		<ul style="list-style-type: none"> <li>• Route critical signals (for example, high-frequency signals, susceptible signals) in an inner signal layer that is embedded between two ground layers.</li> <li>• Give each power supply domain (for example, 5 V, 3.3 V, and so on) separate power and ground planes.</li> </ul>

## **12 Specific PCB design rules for microcontrollers with bridge drivers**

Some general recommendations are:

- Separate the IC supply (VS and VSD) from VDH, that is, separate voltage sense lines from power stages.
- For minimal power dissipation, the recommended package for serial resistor at MON is SMD1206.
- Placeholder for RC snubber circuit for all bridge MOSFETs should be considered for damping of circuit resonances during switching (if needed).
- For better filter performance and longer life, low-ESR electrolytic capacitors, rated for higher ripple current, should be used.
- When a shunt resistor is used, the maximum acceptable capacitance between VDH and SL is 30  $\mu\text{F}$ . Higher values would affect the current sensing too much.

**Specific PCB design rules for microcontrollers with bridge drivers**

## 12.1 Input filter

The input  $\pi$  filter is required for PWM applications. The component values depend on the switching frequency and motor current (**Figure 31**).

The best value of filter capacitor C13 is 1/10 of the input capacitor C15, in order to optimize the filter performance. If an electrolytic capacitor cannot be used for C13 due to reverse polarity requirements, a ceramic capacitor with a value  $>10 \mu\text{F}$  can be used. This capacitor (C17) can be also placed before the circuit for reverse battery protection.


The choice of the inductor L1 depends on the specific application, where typical parameters to consider are the input current, ambient temperature, space in the layout, EMC requirements.

The ground connection of C13 should be the common ground star point (use the ground plane).

In order to avoid RF disturbances entering the board from outside, the ceramic capacitor C14 should be placed as close as possible to the ECU connector.

C16 is optional and should be used for a floating motor cases, to force the common-mode current back to the source.


The input capacitor C15 is an alternative when there is not enough space for three single capacitors. A much better solution are three capacitors placed close to each phase to reduce the loop of the commutation circuit (C28, C48, C68). The C27 / C47 / C67 ceramic capacitors are filters for high frequency currents.

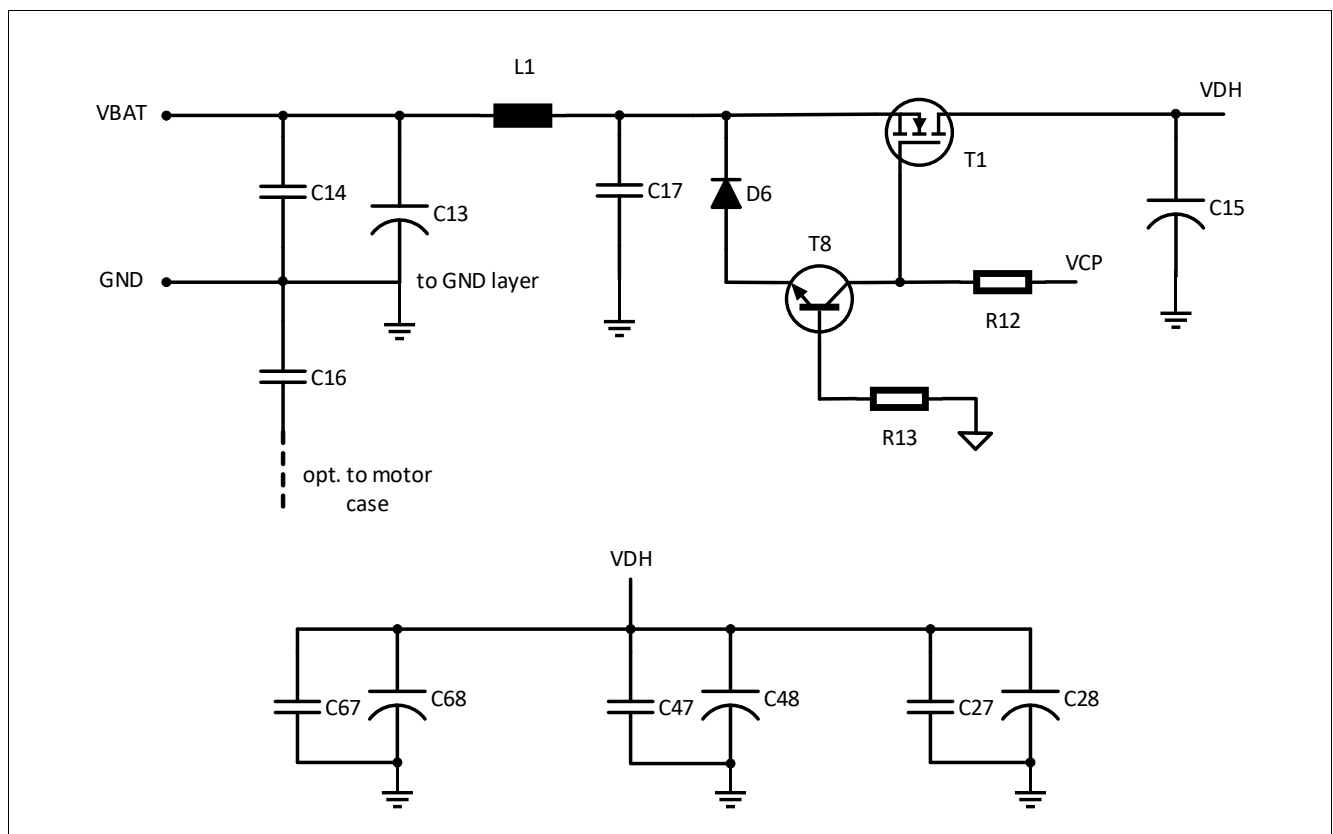

**Figure 31 Input  $\pi$  filter and input capacitor**

### 12.1.1 GND concept

Ground planes should be placed to keep the power MOSFETs' switching currents and the IC operating currents as much as possible separated. **Figure 32** shows these currents and the symbols used for their returning paths.

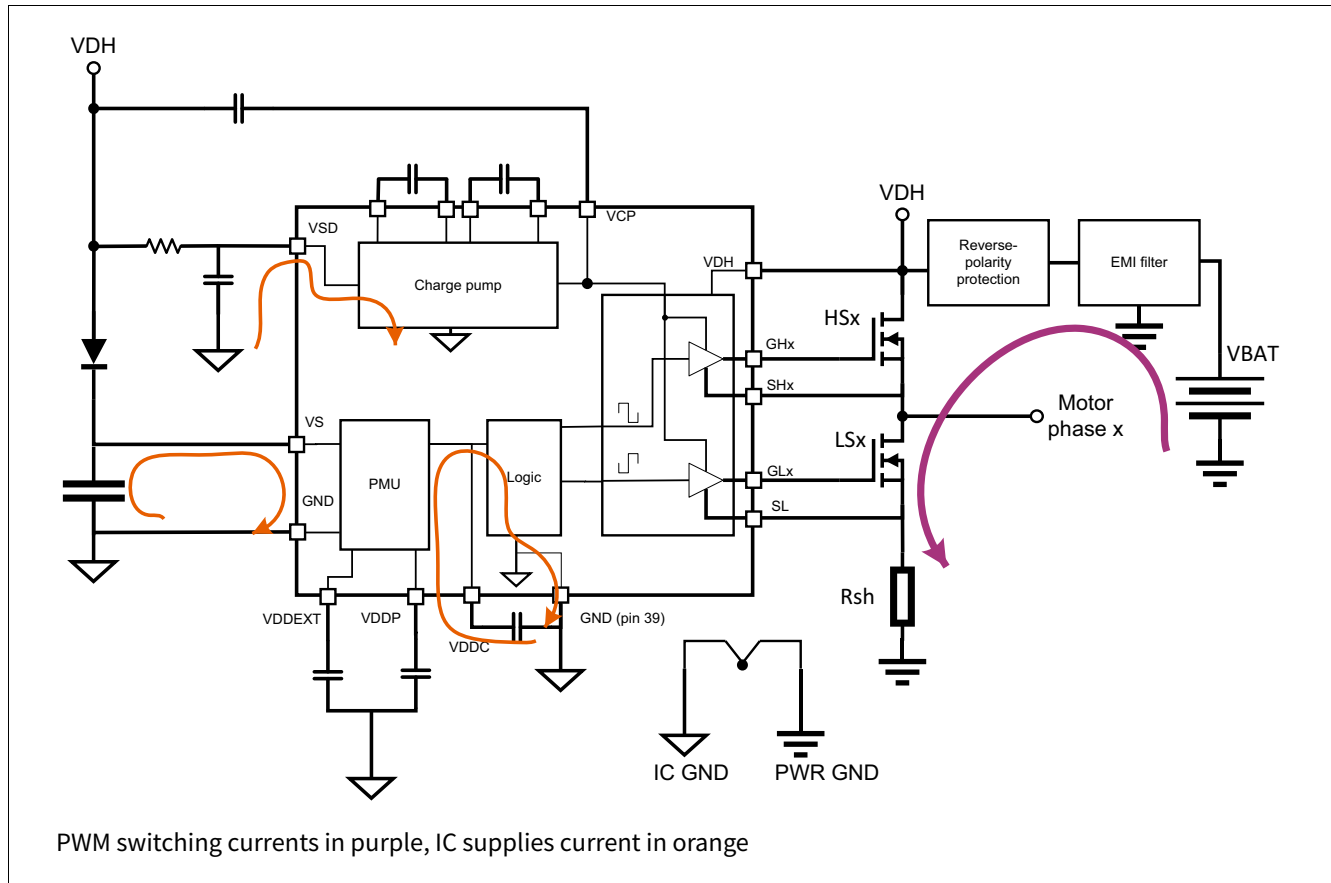

**Figure 32 GND concept and main current paths**

This solution has two beneficial effects:

- The three main GND pins (19, 28, 39) are not influenced by the PWM currents. Voltage differences in the internal ground connections of the analog and digital circuitry in the IC will be limited.
- High-frequency current interactions with the battery ground terminal will be limited.

A practical example is shown in **Figure 33**. The connection between the PWR GND (mid-top) and IC GND (mid-bottom) planes consists of a slim trace and a via. This connection ensures the IC's current supply, while rejecting high-frequency currents that could loop from the IC to the battery.

Consider these guidelines for the GND pin routing:

- Pin 39 should have the most solid connection to the IC GND plane. In the layout example this is accomplished by taking advantage of the exposed pad solid connection through multiple vias. When this is not feasible, connect the VDDC capacitor's GND pin to IC GND with as many vias as possible.
- Pin 19 and 28 can have a weaker connection to IC GND.

To minimize the stray inductance, the loop “input cap – bridge MOSFET – shunt resistor” should be as small as possible.

A typical conducted EMI spectrum of an application that follows these rules is shown in **Figure 34**. This measurement has been performed on the layout example with the motor-running functions turned off to highlight the spectral contribution of the AC currents generated by the IC.

Specific PCB design rules for microcontrollers with bridge drivers



Figure 33 Example PCB layers


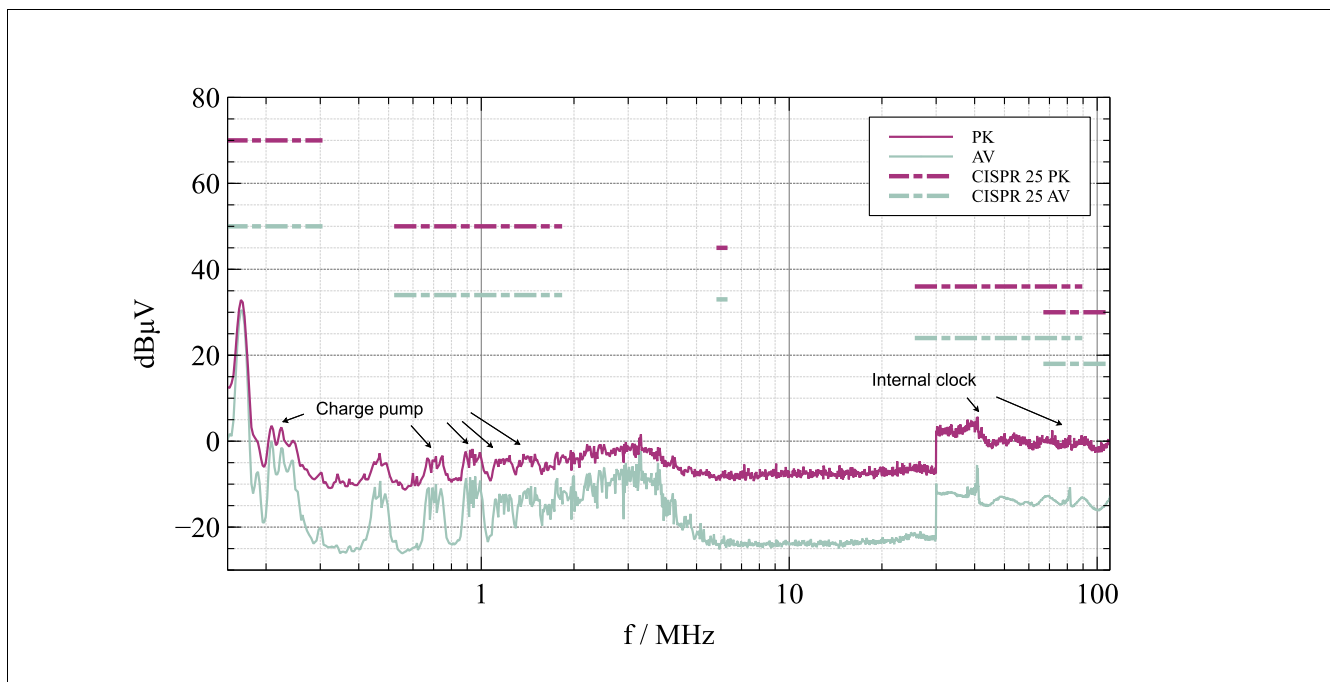


Figure 34 Conducted EMI measurement spectrum related to the layout example

**Specific PCB design rules for microcontrollers with bridge drivers**

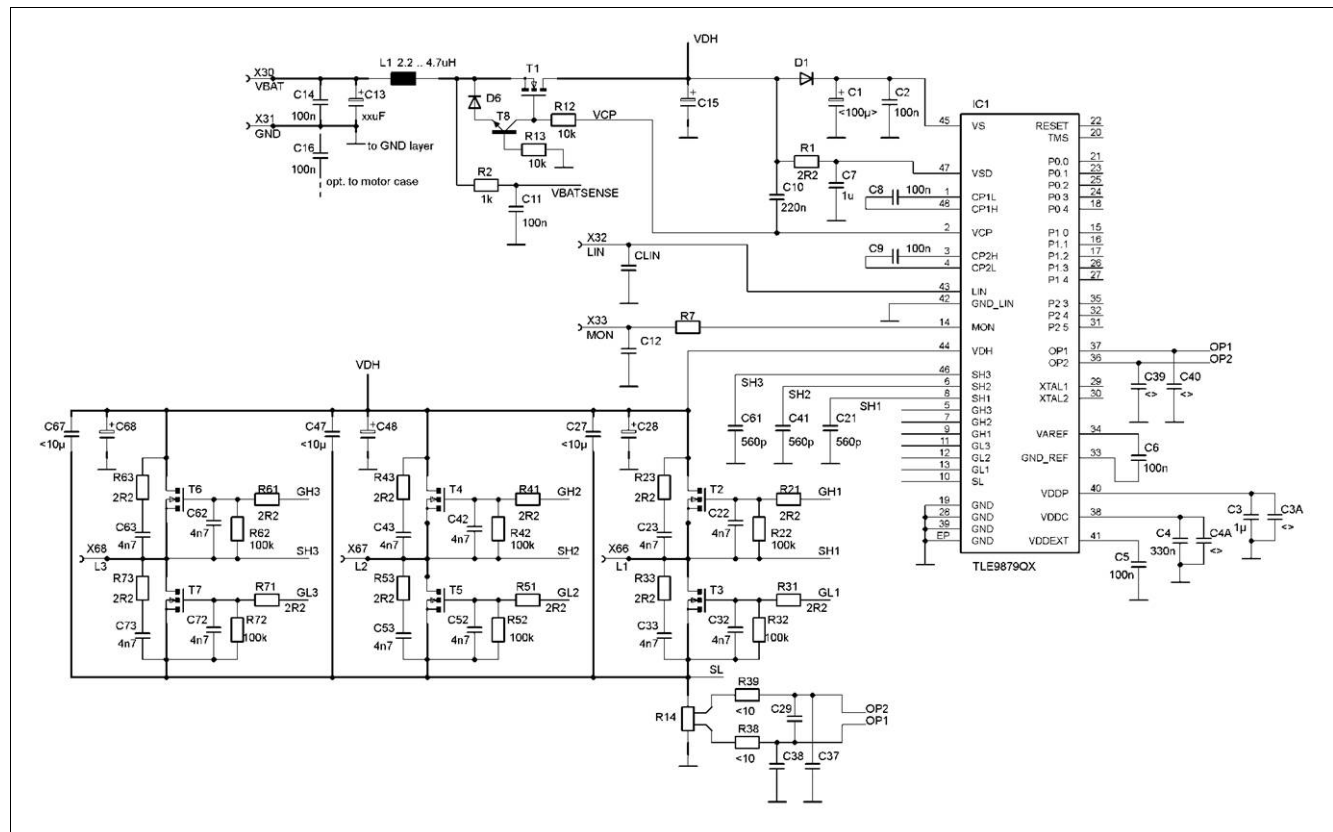

**Figure 35** Ground concept and bypass capacitors

**Specific PCB design rules for microcontrollers with bridge drivers**


## 12.2 Bypass capacitors

**Figure 35** shows the main bypass capacitors used in a typical application. Some comments and recommendations:

- Unless differently specified, all bypass capacitors, acting as input filter of a pin of the IC, should be placed as close as possible to the pin itself.
- To minimize RF disturbances, all components around the shunt resistor should be placed as close as possible to the resistor itself.
- C37 and C38 are optional and they create an additional RC filter to GND. Their selection should be done in relation with C29, since they influence the dynamic of the signal at the input of the CSA.
- C39 and C40 are placeholders for additional capacitors at OPx. They are required if the distance to the shunt resistor is higher than ~5 cm, in order to suppress RF disturbances on this node coupled into the trace behind the  $R_{\text{shunt}}$  filter.
- C6 should only connect VAREF and GND\_REF, no external GND connection.

## 12.3 Layout recommendation for a 3-phase motor bridge

**Figure 36** shows the commutation circuit of one bridge leg. This bridge leg can be a part of a 2-phase or 3-phase bridge.

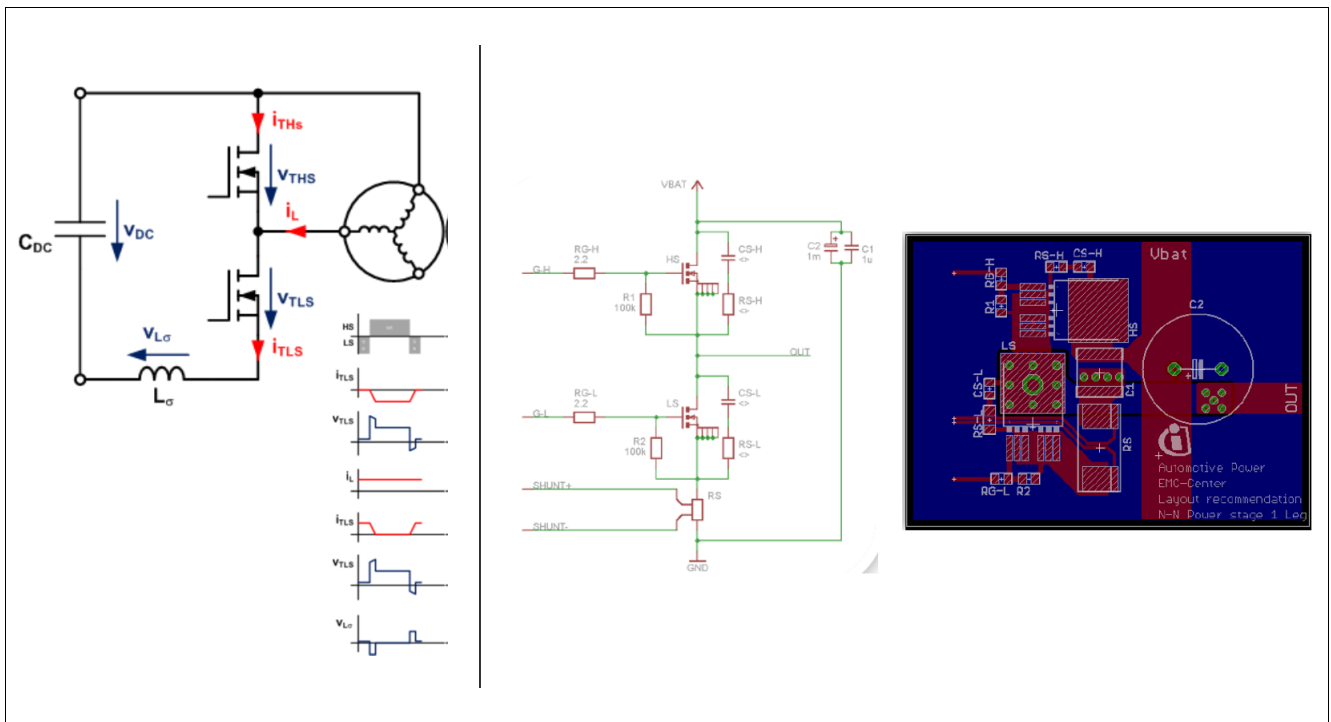


**Figure 36 Layout – one bridge leg with two N-MOSFETs (as part of a 2-phase or 3-phase motor bridge)**

During a switch from the low-side to the high-side, the current is commutating from LS switch to HS switch. The ideal commutation circuit is a loop consisting of  $C_{DC}$ ,  $T_{HS}$ ,  $T_{LS}$ . The inductive part of the real circuit is considered in the stray inductance  $L_{\sigma}$ . Overvoltages are induced over  $L_{\sigma}$  during switching. These overvoltages are coupled directly to Out and to Vs and also cause radiated emissions. The size of the commutation circuit has to be as small as possible.

**Figure 36** shows an example for a low-impedance layout of one motor bridge leg. The capacitors C2, CS-H, and CS-L are placed as close as possible to the device pins.

**Figure 37** shows a recommendation for the commutation circuit of a 3-phase motor bridge.

**Specific PCB design rules for microcontrollers with bridge drivers**

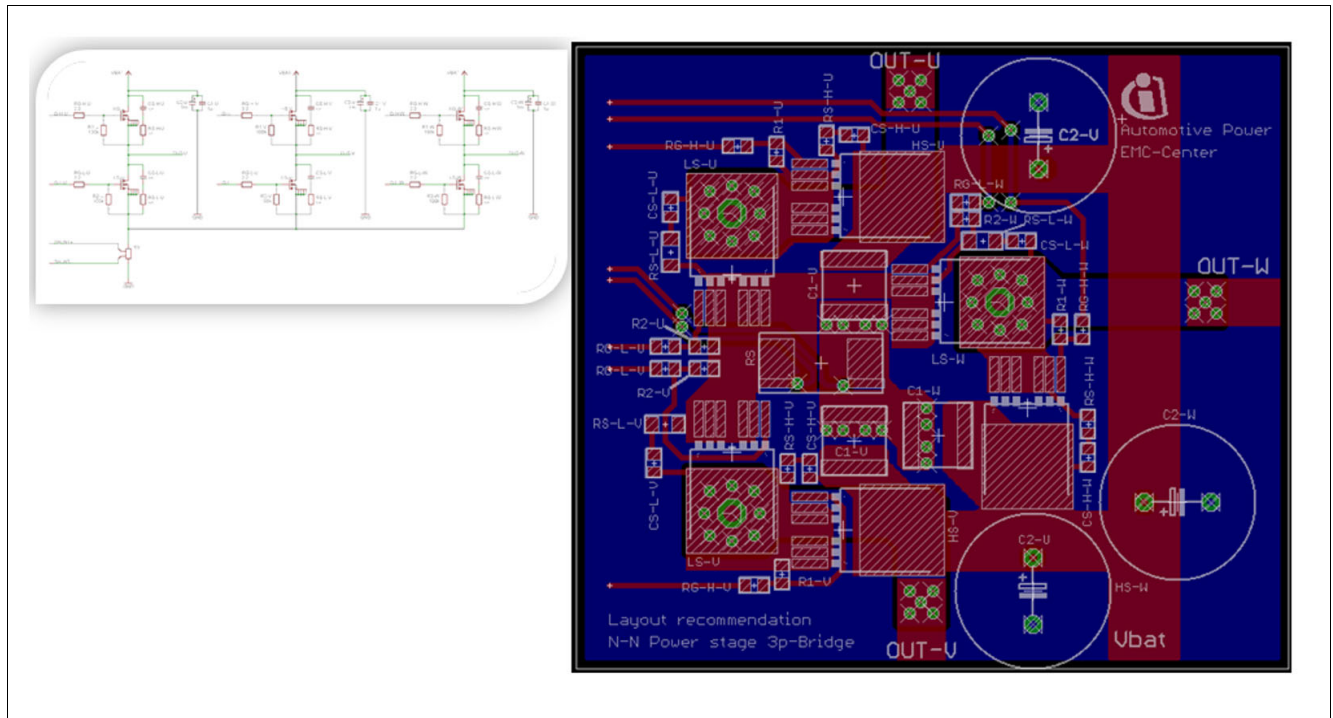


**Figure 37** Layout recommendation – 3-phase motor bridge

Specific PCB design rules for microcontrollers with bridge drivers

## 12.4 Layout recommendation for a current sense shunt

The layout affects the current sensing of the shunt. A low inductive shunt is no guarantee for a low noise measurement signal. The quality of the signal depends on the layout with trace parasitics:

- Use a four-wire sense approach with symmetric sense lines.
- Avoid inductive coupling into the sense wires.
- Take care of capacitive currents on the leads in presence of high  $\Delta V/\Delta t$  (common mode noise).

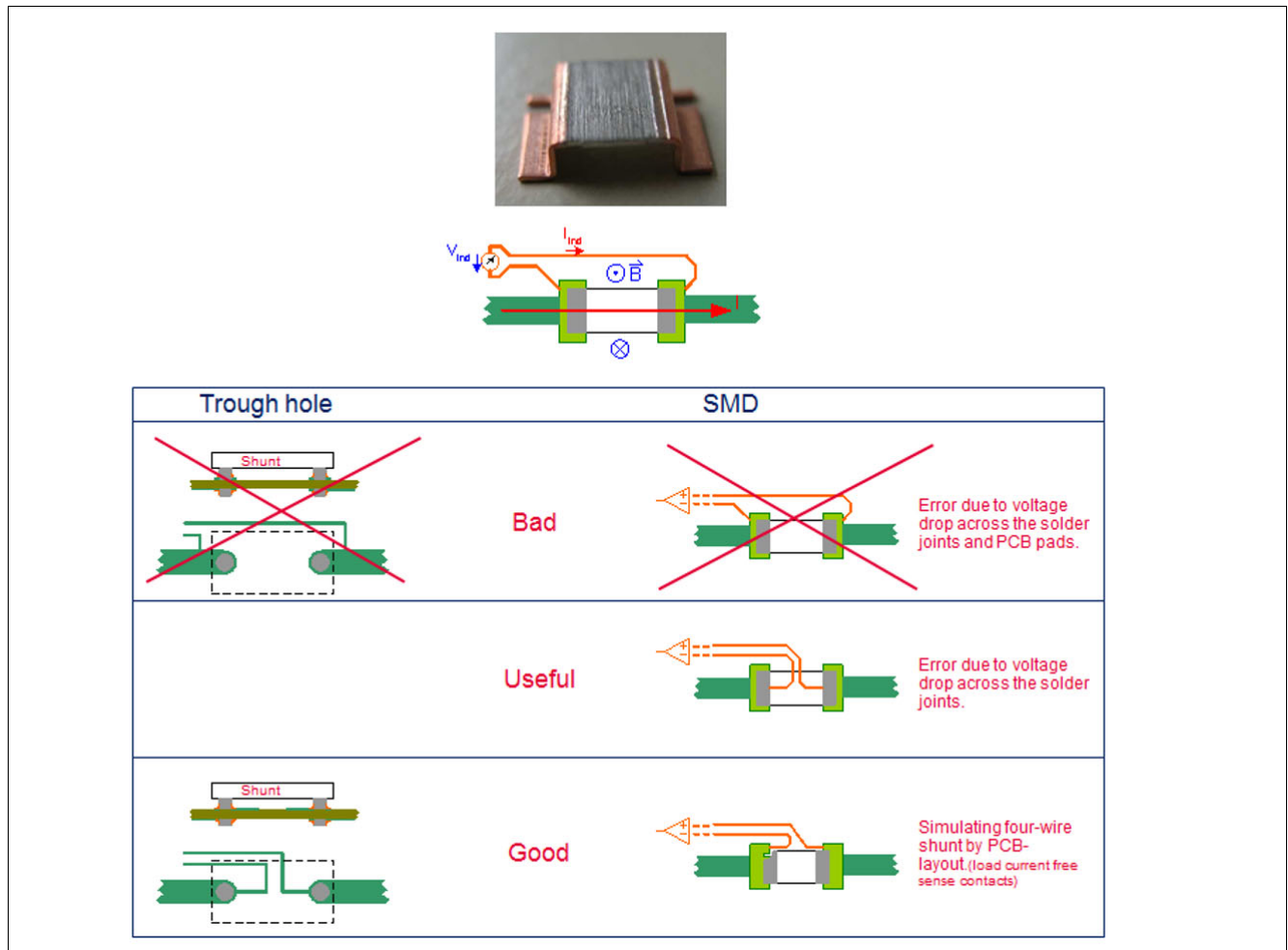

**Figure 38** Layout recommendation – current sense shunt  
No magnetic current sensing, pseudo-four-wire technique

## Revision history

Revision	Date	Changes
1.0	2020-10-30	Initial creation.

**Trademarks**

All referenced product or service names and trademarks are the property of their respective owners.

**Edition 2020-10-30**

**Published by**

**Infineon Technologies AG**

**81726 Munich, Germany**

**© 2020 Infineon Technologies AG.**

**All Rights Reserved.**

**Do you have a question about any aspect of this document?**

**Email: [erratum@infineon.com](mailto:erratum@infineon.com)**

**Document reference**

**Z8F80032532**

**IMPORTANT NOTICE**

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office ([www.infineon.com](http://www.infineon.com)).

**WARNINGS**

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.

# Mouser Electronics

Authorized Distributor

Click to View Pricing, Inventory, Delivery & Lifecycle Information:

Infineon:

[TLE98722QTW40XUMA1](#)