

User guide to BGT24LTR11N16

XENSIV™ 24 GHz radar sensor

About this document

Scope and purpose

This user guide describes the key features of Infineon's XENSIV™ BGT24LTR11N16 24 GHz MMIC, and helps the user quickly get started with the sensor evaluation board. It provides:

- Description of all the different building blocks of the MMIC.
- Operation of the different blocks.
- Measurement data showing behavior over temperature.
- VCO control using different methodologies – PTAT, PLL, and a software-based open loop.

Intended audience

This document serves as a primer for firmware or software engineers who want to get started with hardware design for Infineon's XENSIV™ 24 GHz radar sensors.

Table of contents

About this document.....	1
Table of contents.....	2
1 Introduction	3
2 Building blocks	4
2.1 Transmitter	4
2.2 Receiver	5
2.3 Voltage controller oscillator (VCO)	7
2.4 Proportional to absolute temperature (PTAT) voltage source	8
2.5 Frequency divider.....	9
3 Evaluation board.....	10
3.1 Schematic diagram	10
3.2 Matching structures	11
3.3 Layout	12
3.4 Layout version improving TX to RX isolation	12
4 VCO control	14
4.1 VCO control using PTAT	14
4.2 VCO control using a PLL	16
4.3 VCO control using a software based open-loop concept	17
4.3.1 Hardware setup.....	17
4.3.2 Concept	18
4.3.3 Operation	20
References.....	21
Revision history.....	22
Disclaimer.....	23

2 Building blocks

2.1 Transmitter

BGT24LTR11 has a single-ended transmitter output TX (pin 11) with a typical output power of 6 dBm. The transmitter's output may be enabled and disabled by applying appropriate voltages to TX_ON (pin 5) as shown in Table 1.

Disabling the TX output will not save power, as the output will be switched to an internal load while the rest of the chip is still running. This is necessary in case one wants to implement a software-controlled oscillator, as explained in section 4.

Table 1 Enabling/disabling TX output

Enable TX	Disable TX
Voltage at TX_ON > 2 V	Voltage at TX_ON < 0.8 V

 


Figure 2 TX output power vs. VCO frequency and temperature

 


Figure 3 TX output power with VTUNE connected to V_PTAT vs. temperature

2.2 Receiver

The receiver consists of an LNA followed by a quadrature direct-conversion mixer. Its input (RX, pin 3) is single ended. The voltage conversion gain is typically 20 dB with a single side-band noise figure of 10 dB.

 


Figure 4 Conversion gain vs. RX frequency and temperature

 


Figure 5 Noise figure vs. RX frequency and temperature

 


Figure 6 Conversion gain vs. temperature and RX frequency

 


Figure 7 Noise figure vs. temperature and RX frequency

2.3 Voltage controller oscillator (VCO)

 


Figure 8 VCO frequency vs. tuning voltage and temperature

 


Figure 9 VCO frequency vs. temperature, VCO controlled by PTAT voltage source. Measured at random sample.

2.4 Proportional to absolute temperature (PTAT) voltage source

The PTAT voltage source generates a voltage V_{PTAT} at the V_PTAT pin (pin 15) which is proportional to the temperature of the chip. It is powered separate from VCC via the VCC_PTAT pin (pin 16).

The PTAT voltage source generates a tuning voltage for the VCO in Doppler mode, see section [4.1](#).

 


Figure 10 Voltage generated by PTAT voltage source vs. temperature for a random device.

2.5 Frequency divider

BGT24LTR11's frequency divider has two divider ratios, divide by 16 and divide by 8182 which result in output frequencies of 1.5 GHz and 3 MHz respectively.

Table 2 **Setting the divider ratio**

Divider ratio	Voltage at VCC_PTAT (pin 16)
16	< 0.8 V
8192	3.3 V

Setting the divider to a 3 MHz output will cause the PTAT to consume current. This ratio is usually used only in case of a software controlled VCO. In this use case, the V_{PTAT} is also required to check the validity of the used look-up table (LUT), as explained in section [4.3](#).

3 Evaluation board

3.1 Schematic diagram

 


Figure 11 Schematic diagram of the BGT24LTR11 EVAL board

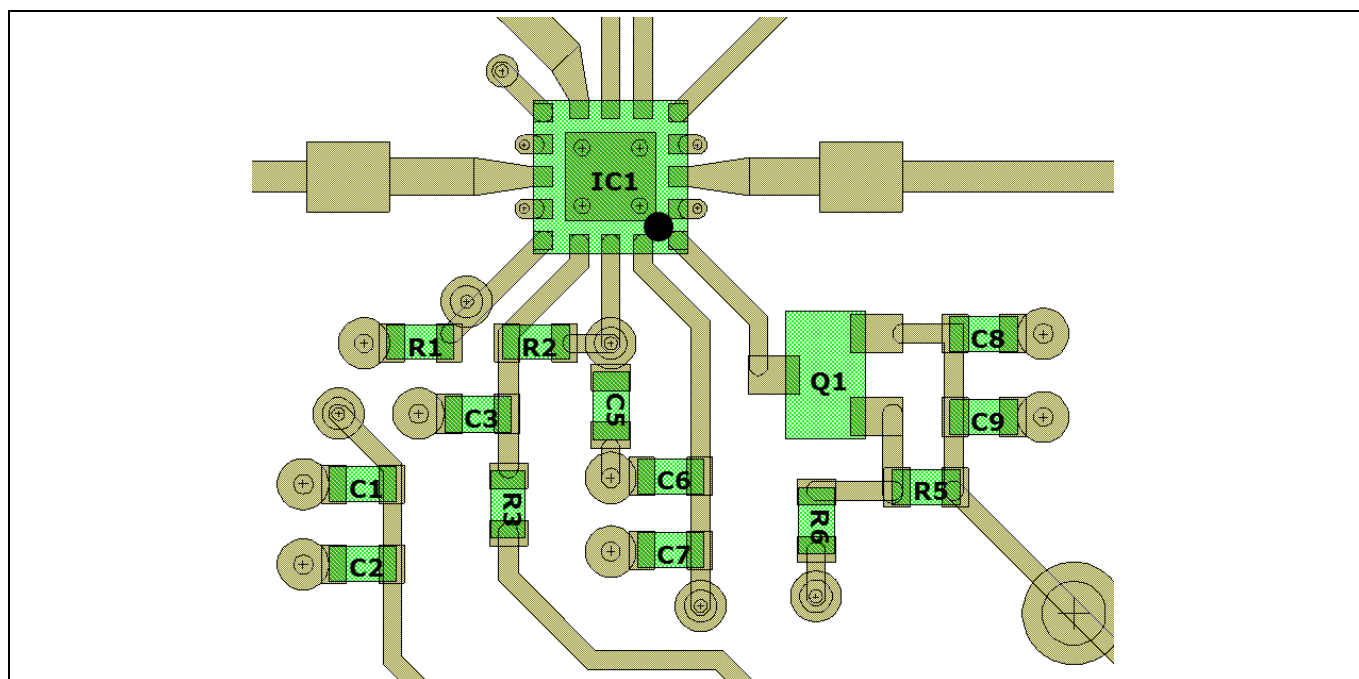


Figure 12 Component placement

Table 3 Bill of materials (BOM)

Designation	Part type	Value	Package	Manufacturer
C1, C5, C8	Chip capacitor	1 μ F	0402	Various
C2, C3, C6, C7, C9		DNP	0402	
R1	Chip resistor	16 k Ω	0402	Various
R2,R3	Chip resistor	0 Ω	0402	Various
R5	Chip resistor	100 k Ω	0402	Various
R6	Chip resistor	1 k Ω	0402	Various
Q1	p-MOSFET	BSS209PW	SOT-323	Infineon
IC1	Radar MMIC	BGT24LTR11N16	TSNP-16-9	Infineon

3.2 Matching structures

 


Figure 13 Matching structures on a Ro4350B substrate with a thickness of 0.254

3.3 Layout

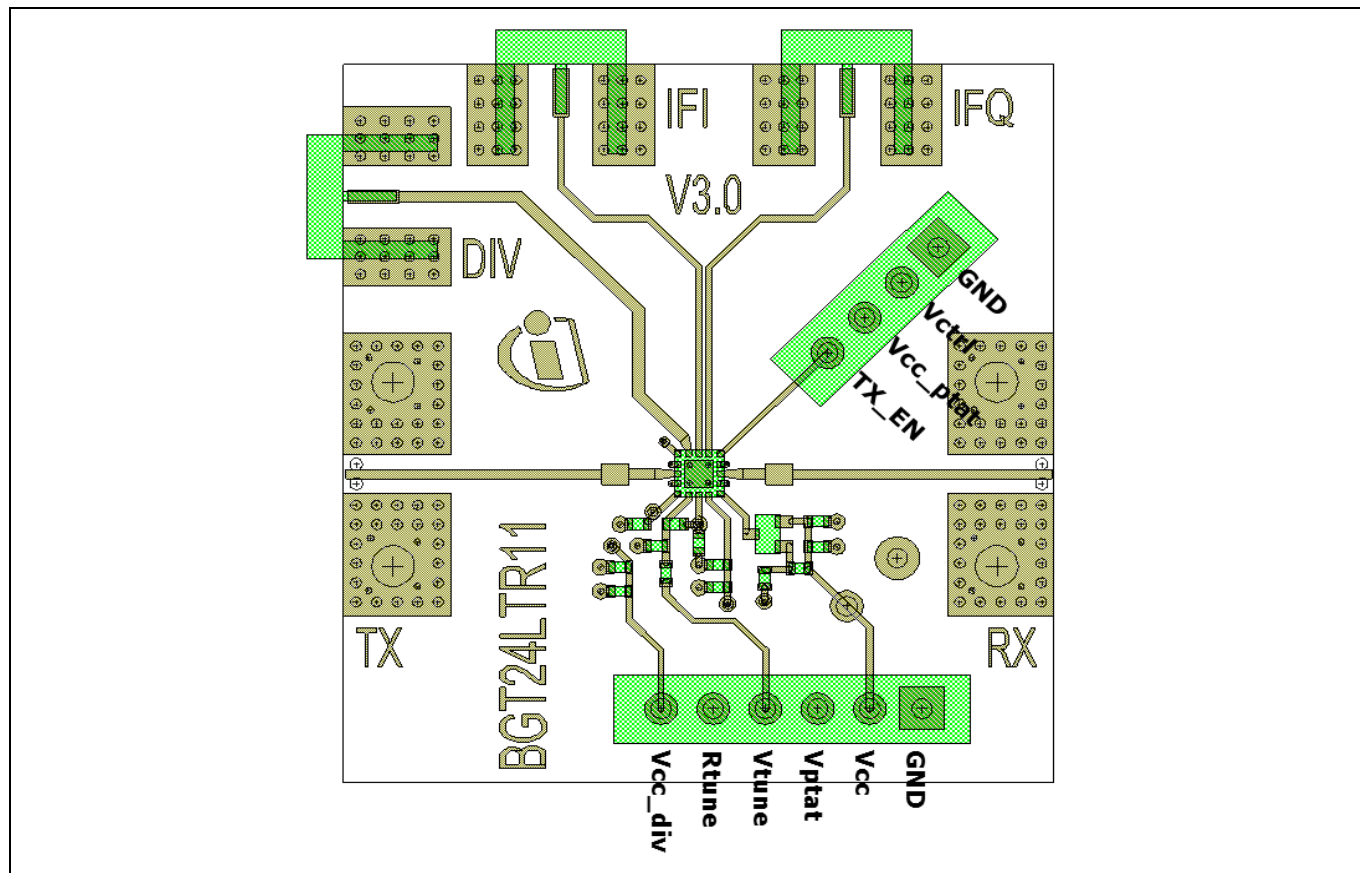


Figure 14 Layout with description of pin headers

 


Figure 15 Layer stackup

3.4 Layout version improving TX to RX isolation

The isolation between the TX port and the RX port on the standard evaluation board is typically about 25 dB. This isolation can be improved to 35 dB by adding a grounded length of line at the ground pins next to the TX output pin, as shown in [Figure 16](#). Details of the used compensation structures can be found in [Figure 17](#).

Table 4 TX to RX isolation

	Standard evaluation PCB	PCB with compensation structures
TX to RX isolation (in dB)	25	35

 


Figure 16 Addition of compensation structures to increase TX to RX isolation

 


Figure 17 Compensation structures in detail – all dimensions in mm

4 VCO control

4.1 VCO control using PTAT

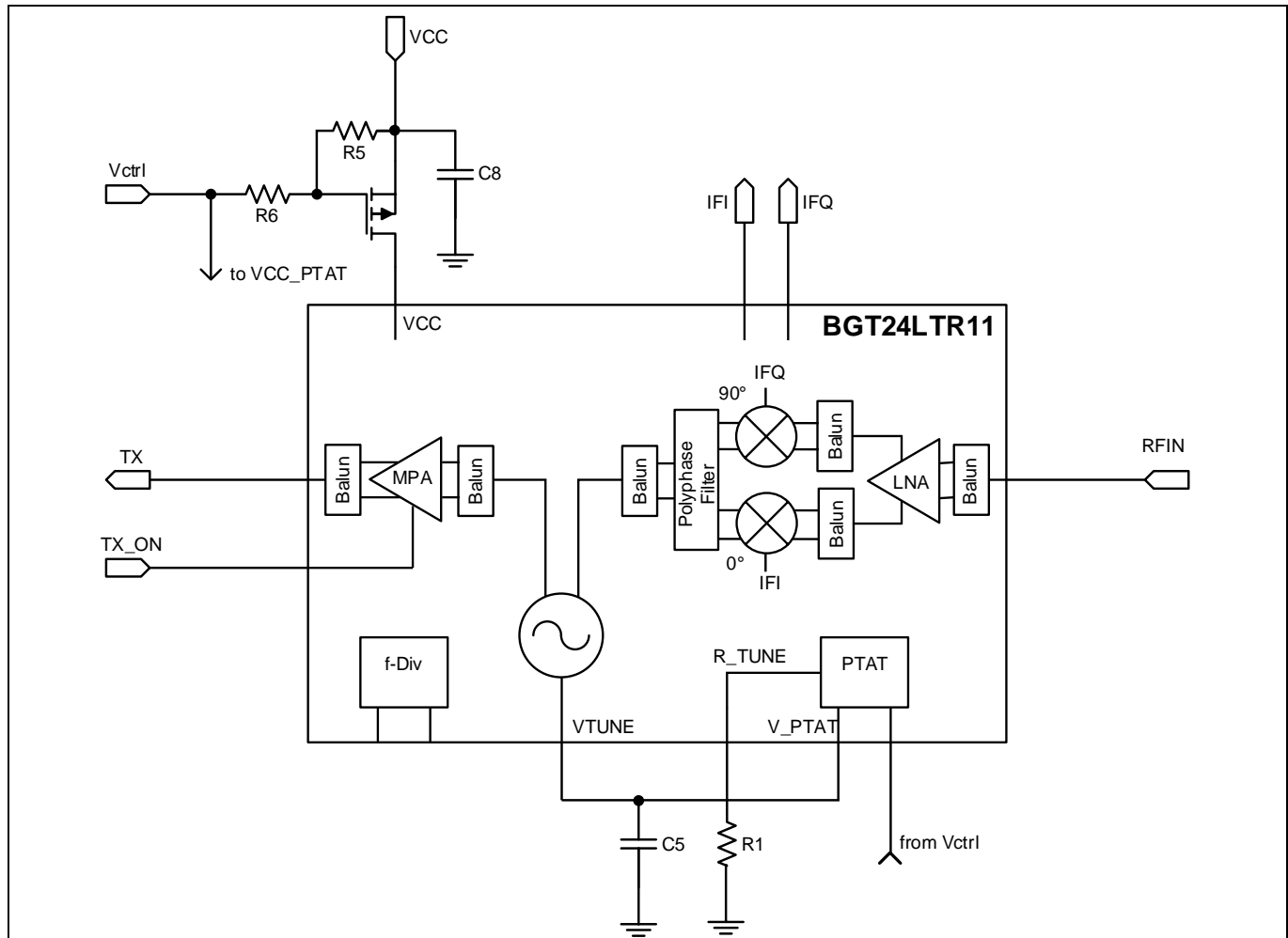


Figure 18 Block diagram of using V_{PTAT} to keep BGT24LTR11 in the ISM band

BGT24LTR11 was designed to keep its transmit frequency inside the ISM band without the need for a dedicated frequency control circuit like a PLL or an LUT based control of V_{TUNE} . In Doppler radar mode, frequency adjustment via V_{PTAT} is the most efficient way.

Exact frequency control in Doppler radars in the 24 GHz ISM band is not really necessary for most applications. If we assume the transmit frequency to be at the lower edge of the band while it is actually at the upper edge, the introduced error is only 0.8%. However, it is necessary that the TX signal stays inside the ISM band under all conditions.

The analog V_{PTAT} control signal forces the VCO into the opposite direction in case of temperature drift. Doing so, the temperature effect of the VCO is strongly reduced. $R1$ adjusts the relative level of V_{PTAT} . To buffer and reduce noise on V_{tune} (V_{PTAT}), capacitor $C5$ (big capacitor) is charged by V_{PTAT} while the rest of the chip is turned OFF to save power during duty cycle OFF time. Going into duty cycle ON mode, the chip is fully supplied and VCC_{PTAT} (via V_{ctrl}) is disconnected to drive V_{TUNE} from $C5$.

VCO control

There are two reasons for toggling VCC and VCC_PTAT:

- Turning off VCC and VCC_PTAT reduces current consumption (45 mA and 1.5mA, respectively)
- The PTAT source generates noise at its output when running, and this noise on the tuning voltage will degrade the signal-to-noise ratio (SNR) of the system. However, for some short range this SNR might still be acceptable.

Operation:

1. TX_ON = 0 V. Disables TX output to prevent out of band emissions.
2. Vctrl = 3.3 V. This turns on the PTAT source (VCC_PTAT = 3.3 V) while VCC line for the entire RF stage including the VCO is disconnected from the power supply.
3. Wait for C5 to be charged. At the start-up of the system when the capacitor is fully discharged, this will require a longer time. During normal operation, the capacitor is only slightly discharged and will be very quickly recharged.
4. Vctrl = 0 V. Turn off PTAT and turn on the rest of the chip (RF with VCO).
5. Wait for VCO to settle its frequency. Settling time of the VCO is maximum 100 ns.
6. TX_ON = 3.3 V. Enables TX output.
TX_ON should be delayed by about 200ns vs. RF section ON (Vctrl = 0 V) to keep TX signal clean.
7. Sample IF frequency.
8. Go to 1.

Further reduction of the power consumption is possible by introducing a time frame when both VCC and VCC_PTAT are disconnected. This would mean that VCC_PTAT needs to be disconnected from Vctrl and one more independent GPIO pin needs to be available at the microcontroller unit (MCU) in the system.

4.2 VCO control using a PLL

A PLL can be connected to the BGT24LTR11 to control the VCO as shown in Figure 19.

To implement this, the frequency divider needs to be set to a ratio of 16 by connecting VCC_PTAT to GND.

The VCO output is split into the TX antenna path and the local oscillator (LO) path. Furthermore, the VCO output signal gets divided by a factor of 16 (prescaler), producing a 1.5 GHz divider output signal for the PLL.

In the PLL, further dividers (N-divider) are applied to the input divider signal to further reduce the frequency. The phase detector (PD) in PLL compares the N-divider output signal with the reference from a crystal oscillator to control the PLL charge pump (CP). The CP_{out} is converted into an analog VCO tuning signal (VTUNE) via the loop filter (LF). VTUNE finally controls the VCO frequency to achieve a full signal fit between N-divider output signal and the reference signal to achieve a frequency and phase lock.

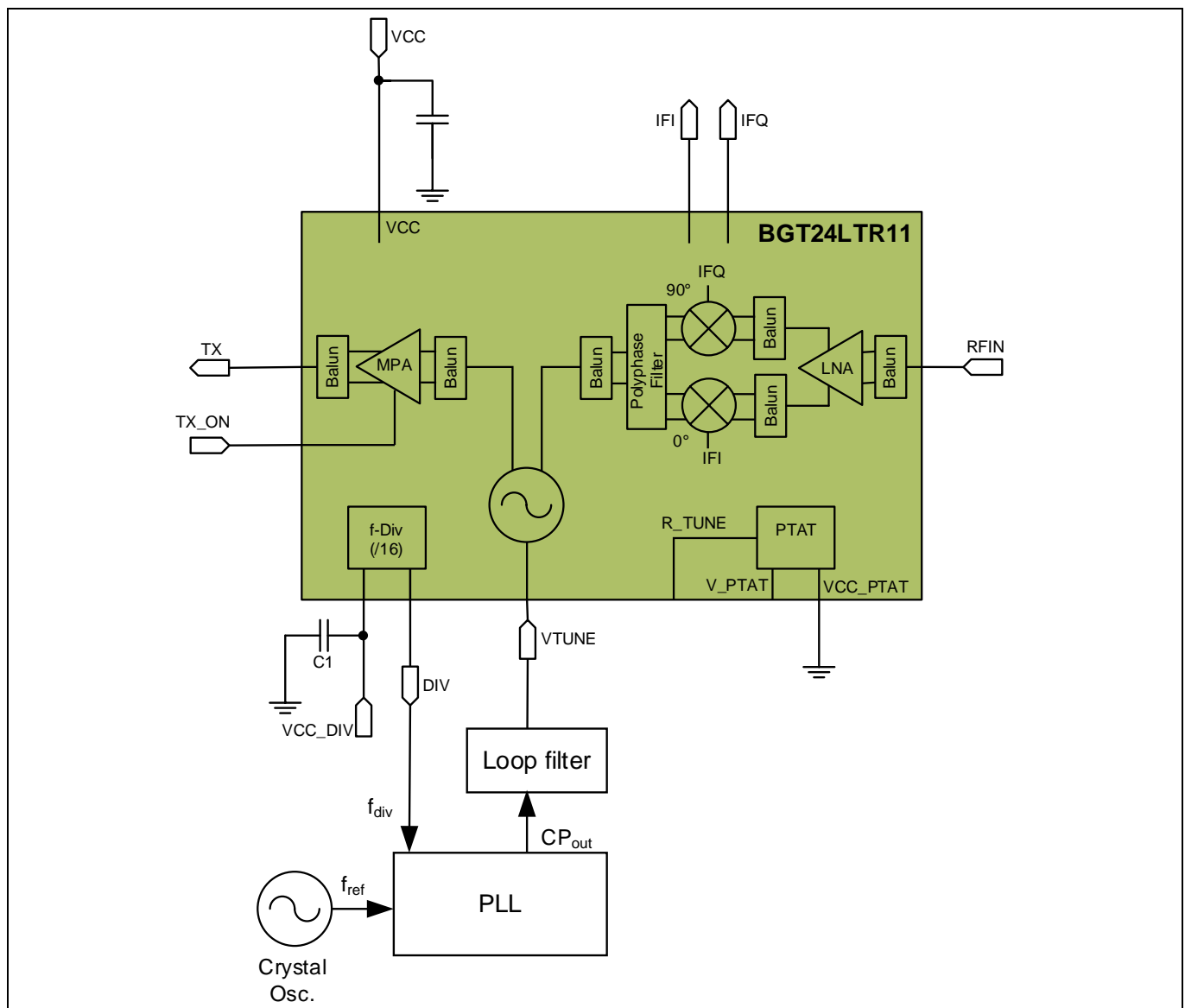


Figure 19 Block diagram of VCO control using a PLL

Figure 20 shows a block diagram on how to set up the system.

- Connect the VCC_DIV and VCC_PTAT to VCC to set the divider ratio to 8192.
- Connect the divider output to a Capture & Compare Unit (CCU) of the MCU to determine the frequency of the oscillator.
- Connect the MCU's digital-to-analog converter (DAC) output to the V_TUNE of BGT24LTR11 through a 2-stage RC filter to provide a tuning voltage to the VCO.
- The 2-stage RC DAC filter is required to filter the noise and reject the higher unwanted frequencies. It should be placed as close to the VCO V_TUNE input as possible.
- The design of this RC DAC filter is critical to avoid VCO modulation with noise and spurs. For a stepped-FMCW approach, the DAC filter needs to be optimized for the update rate based on the chirp time (T_c) and number of samples per chirp (N_{samples}). For example, for a $T_c = 1500$ ms and $N_{\text{samples}} = 256$, the update rate is $1500 \text{ ms} / 256 = 6 \mu\text{s}$ (step-time). Therefore, the RC time constant for the DAC filter should be designed to settle at $5 \mu\text{s}$ (90...95% of the desired voltage step). This lets the DAC's output voltage and consequently the VCO frequency to be in a steady state at the end of step-time when the baseband analog-to-digital converter (ADC) is triggered for measurement.
- As an option, connect the V_PTAT output from BGT24LTR11 to an ADC channel of the MCU to determine the temperature of the chip. This would allow compensating the frequency shift due to temperature changes and would reduce the need to re-calibrate the SW PLL very frequently.

4.3.2 Concept

As shown in Figure 20, the DAC of the MCU is used to generate a tuning voltage for the VCO input. V_{tune} is generated by the DAC for the start frequency and then filtered in the RC-filter (2 stages). According to the V_{tune} input, the VCO produces the TX/LO signal. The VCO signal is also fed into a frequency divider and gets divided by a factor of 8192. This divided signal is captured by the CCU in the MCU. The divider output signal is measured by counting the number of rising/falling (or both) edges of the MCU's master clock inside a certain number of divider output signal periods (counting gate). The measured frequency is then compared with the required start frequency ($24.025 \text{ GHz} / 8192 = 2.9327 \text{ MHz}$). The difference between the measured and required frequency is then evaluated in the decision function. Depending on the result, the bit value gets adapted, and the loop starts again until the measured and wanted frequency to agree within a certain margin. This routine is repeated for the stop frequency as well ($24.225 \text{ GHz} / 8192 = 2.9571 \text{ MHz}$).

Note: To prevent out of band emissions, a guard band of 25 MHz between ISM band edges and the Start/Stop frequency of the stepped-FMCW sweep is implemented. Therefore, the chirps have a bandwidth of 200 MHz ($24.025 \text{ GHz} - 24.225 \text{ GHz}$) and calibration is done every frame. The guard band would change depending on the circuitry implemented and how often the calibration is done.

Note: The 200 MHz bandwidth is split up into a certain number of points per chirp (N_{samples}). N_{samples} is related to unambiguous range and therefore impacts the maximum range ($R_{\text{max}} = N_{\text{samples}} \cdot \Delta R$), where R_{max} is the maximum achievable range and ΔR is the range resolution.

User guide to BGT24LTR11N16

XENSIV™ 24 GHz radar sensor

VCO control

 


Figure 21 Decision function

The length of the counting gate has a strong impact on the accuracy of the VCO frequency measurement. At the start and at the end of the counting gate (N times the period of the divider output signal), there is a systematic error caused by the period of the MCU master clock. Longer counting gate time (i.e., a greater number of periods of the MCU master clock – e.g., 80 MHz – are counted) results in a lower impact of this systematic error on VCO frequency measurement accuracy. However, longer counting gate time results in a longer ON time for the BGT24LTR11 and impacts the overall power consumption.

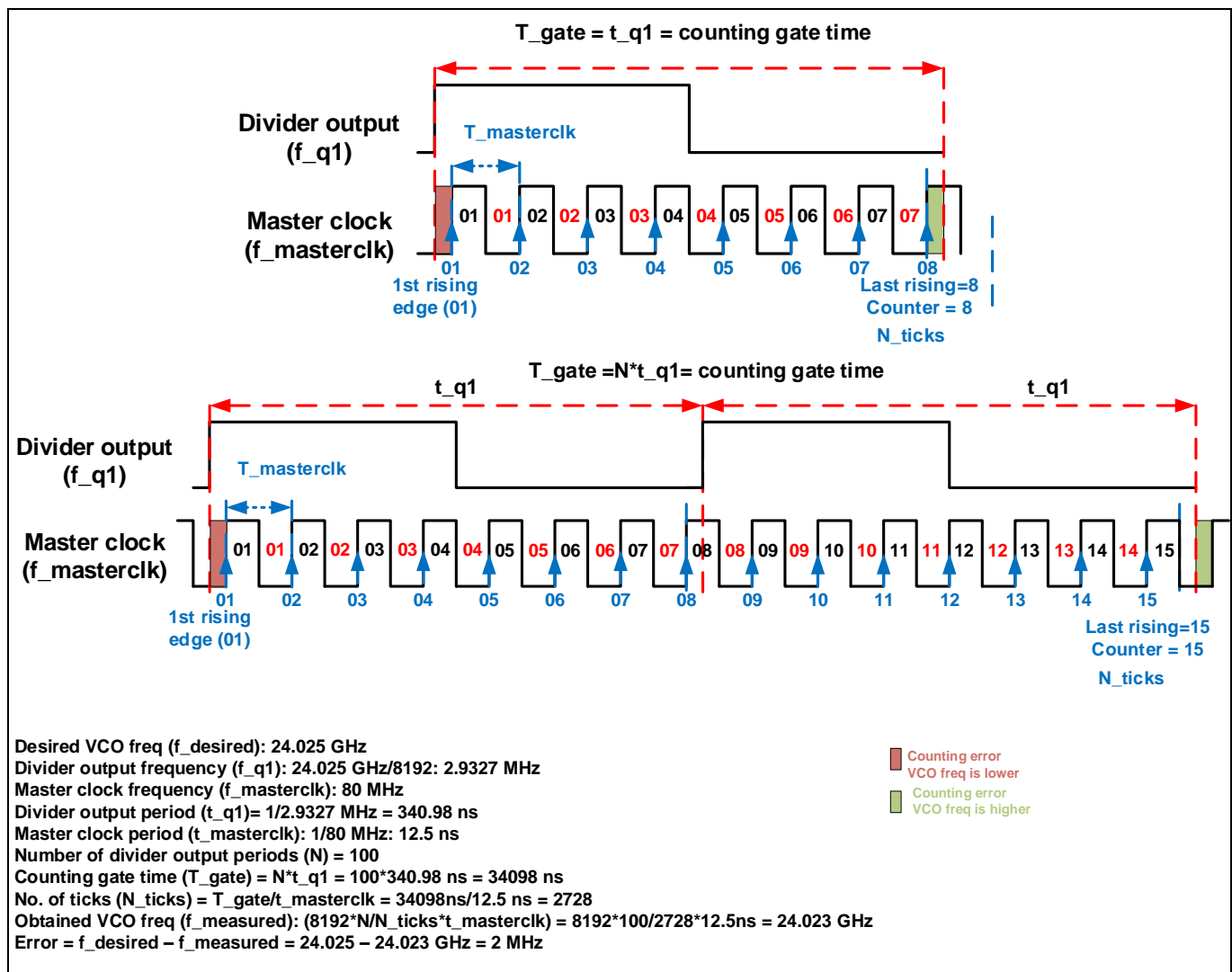


Figure 22 Systematic timing error at the start and the end of the counting gate

VCO control

For a divider output frequency of ~3 MHz and an MCU master clock of 80 MHz, we recommend counting over 100 periods ($N=100$) of the divider output signal, to get a maximal frequency measurement error < 10 MHz.

Another way to reduce this systematic timing error would be to increase the master clock frequency (for example, a master clock of 120 MHz instead of 80 MHz will reduce the error as the T_{clock} time will be reduced from 12.5 ns to 8.3 ns, and the maximal frequency measurement error is < 6 MHz). However, higher master clock frequency leads to higher power consumption by the microcontroller.

*Note: To stay inside the ISM band during the frequency search process, the smart search for the start frequency always begins with a DAC value generating a VCO frequency **above** the desired start frequency. Similarly, stop frequency search should begin **below** the desired stop frequency.*

With the achieved start- and stop frequency DAC values (and V_{tune} values) a linear interpolation can be done and an LUT “DAC value vs. VCO Frequency” is generated. The contents of the LUT are clocked (e.g., via DMA) to the DAC and hence provide the modulation of the VCO.

To further improve the linearity of the chirps, it is possible to do a search for three or more frequency points and perform a polynomial approximation between these points to fit the V_{tune} vs. VCO Frequency in a more precise non-linear LUT. Also, by utilizing the chip’s temperature information (e.g., via PTAT), the LUT can be re-calibrated only when there is a change in the chip’s temperature. This would reduce the need to calibrate the LUT very frequently.

4.3.3 Operation

1. To get the best frequency measurement accuracy (No VCO pulling effect), TX should remain ON during the frequency search process. VTUNE must keep the VCO in the ISM band all the time by following the ‘smart search’ methodology from section 4.3.2.
2. Check the temperature of the chip using the V_{PTAT} . (if implemented)
3. Set the DAC to a fixed starting value for start frequency search to generate a VTUNE voltage for the VCO.
4. CCU measures the frequency of the divider output signal. The desired start frequency is already known and compared with the measured frequency. The DAC value is then adjusted using a decision function to achieve the best possible match for the desired frequency. (iterative frequency search process)
5. Once the DAC value for the start frequency is found, repeat the steps 3 and 4 to search the appropriate DAC value for the stop frequency.
6. Using these start and stop DAC values, generate an LUT that gives the DAC values corresponding to different VCO frequencies.
7. Use the generated LUT for the modulation of the VCO by clocking the LUT values (e.g., via DMA) to the DAC. Feed the DAC output to the DAC filter. After the DAC filter output has settled on the step, take the ADC measurement, and then move the DAC to the next LUT step, creating a stepped-FMCW chirp.
8. Check the temperature of the chip. If the temperature changed, or it is the beginning of a new frame go to 1 else go to 7 to generate the next chirp.

References

- [1] Infineon Technologies AG. *BGT24LTR11N16 MMIC datasheet*; [Available online](#)

Revision history

Document revision	Date	Description of changes
1.30	2017-11-03	Initial release
1.40	2019-07-09	8 f: Corrections to PTAT source Section 4: Detailed description of the VCO control through PTAT, PLL and Software-controlled loop
1.50	2023-02-14	Miscellaneous document cleanup updates

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2023-02-14

Published by

Infineon Technologies AG

81726 Munich, Germany

**© 2023 Infineon Technologies AG.
All Rights Reserved.**

Do you have a question about this document?

Email: erratum@infineon.com

Document reference

UG133248

Important notice

The information given in this document shall in no event be regarded as a guarantee of conditions or characteristics ("Beschaffheitsgarantie").

With respect to any examples, hints or any typical values stated herein and/or any information regarding the application of the product, Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind, including without limitation warranties of non-infringement of intellectual property rights of any third party.

In addition, any information given in this document is subject to customer's compliance with its obligations stated in this document and any applicable legal requirements, norms and standards concerning customer's products and any use of the product of Infineon Technologies in customer's applications.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

Warnings

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.