




Driving circuit examples of laser diodes

May. 21, 2020
Optical module Business Unit
Photonics Div.
Product Development Dept. 1

Two way of driving LDs; ACC & APC



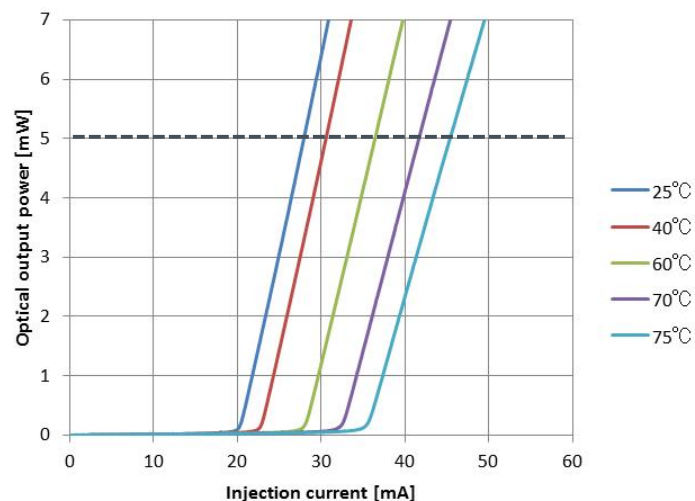Graph 1. injection current vs optical output power




When a constant current is injected, optical output power; P_o of LD changes by the temperature. The example when 30mA is injected to LD on graph1 is as follows. If case temperature; T_c is 25 degrees Celsius, P_o becomes about 6mW. If T_c is 60 degrees, P_o might be about 1mW. If T_c is over 70 degrees, P_o is only LED light.

In other words, if **auto current control; ACC** is adopted, it is possible to destroy LD by over power and to use no LD light.

Therefore ROHM recommend **auto power control; APC**. When photo diode is built in LD, P_o is known by monitor current; I_m . It is designed to keep almost same value regardless of T_c . If the injection current to LD on graph 2 is changed with keeping I_m constant, P_o becomes 5mW regardless of T_c .

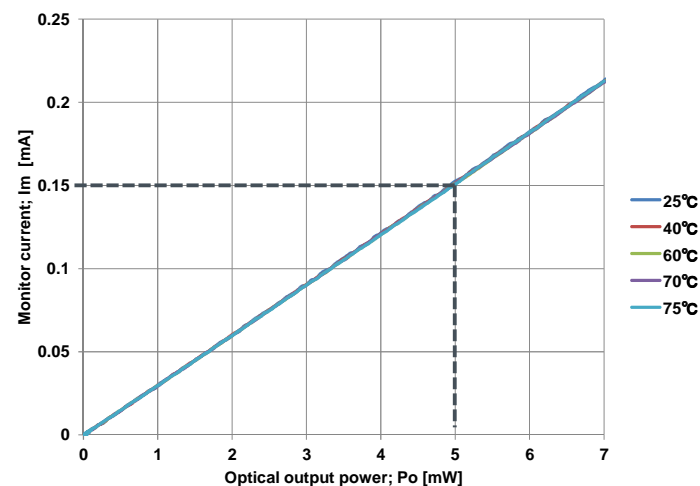Graph 2. optical output power vs monitor current




Mark	LD common	PD common
M	cathode	cathode
N	anode	cathode
P	cathode	anode

polarity

shown by the sixth character from the left of the type name.

It is ROHM original mark.


ACC (電流一定) 回路例

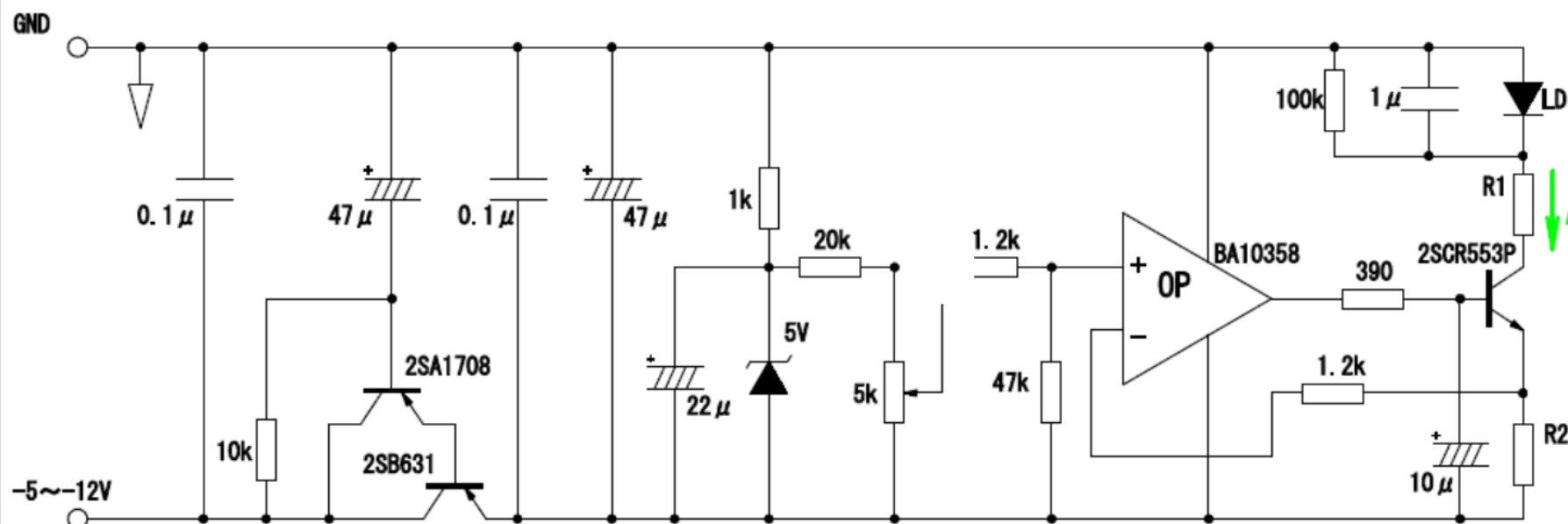


The optical output of the laser diode varies largely by the ambient temperature even when using a constant current.

Therefore an **APC circuit** (as described in the following sections) which is not influenced by an ambient temperature is used.

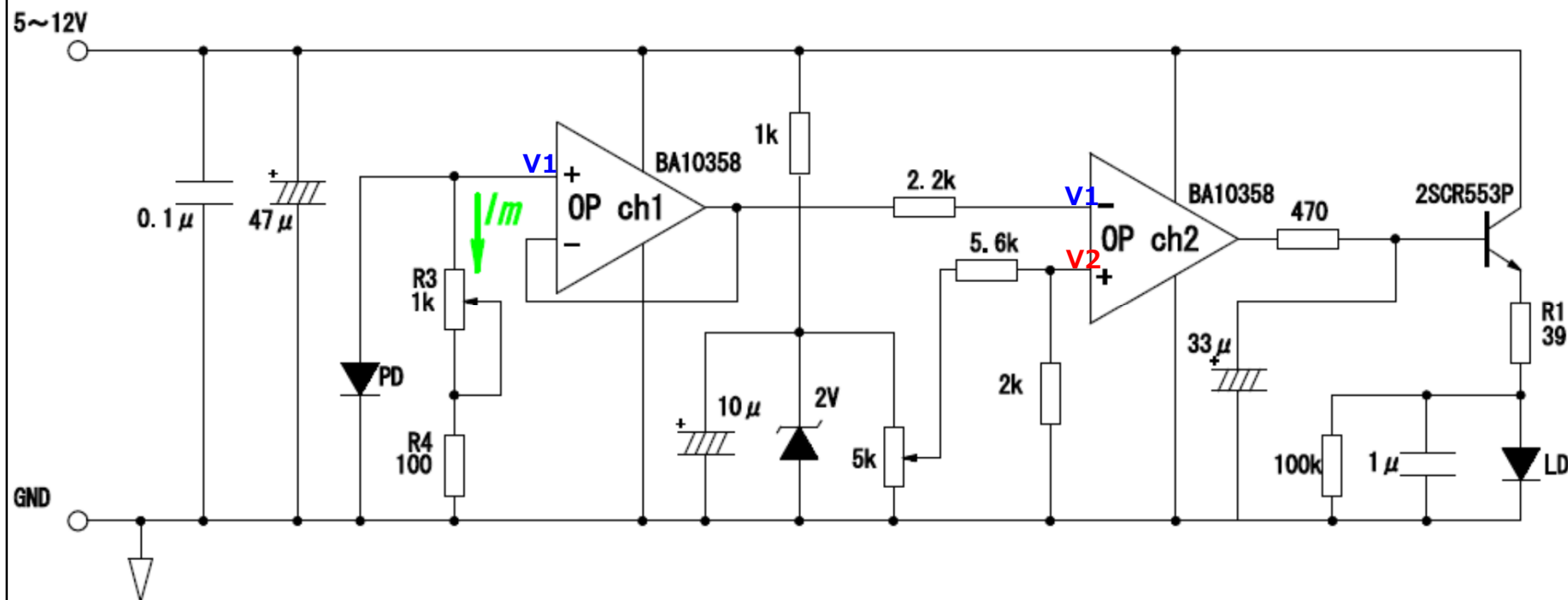Auto Power Control drive circuit example for M type LDs



M type

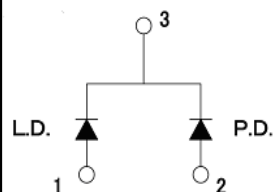

When LD is turned on, monitor current (I_m) flows.

I_m is proportional to the amount of light.


And Voltage become: $V1 = I_m(R3 + R4)$.

At same time, reference voltage $V2$ is generated by zenner diode and volume.


OP2 always control the base current for output transistor so that it is always $V1 = V2$ and constant current flows into LD.

Note) $V1$ must not exceed 0.5V

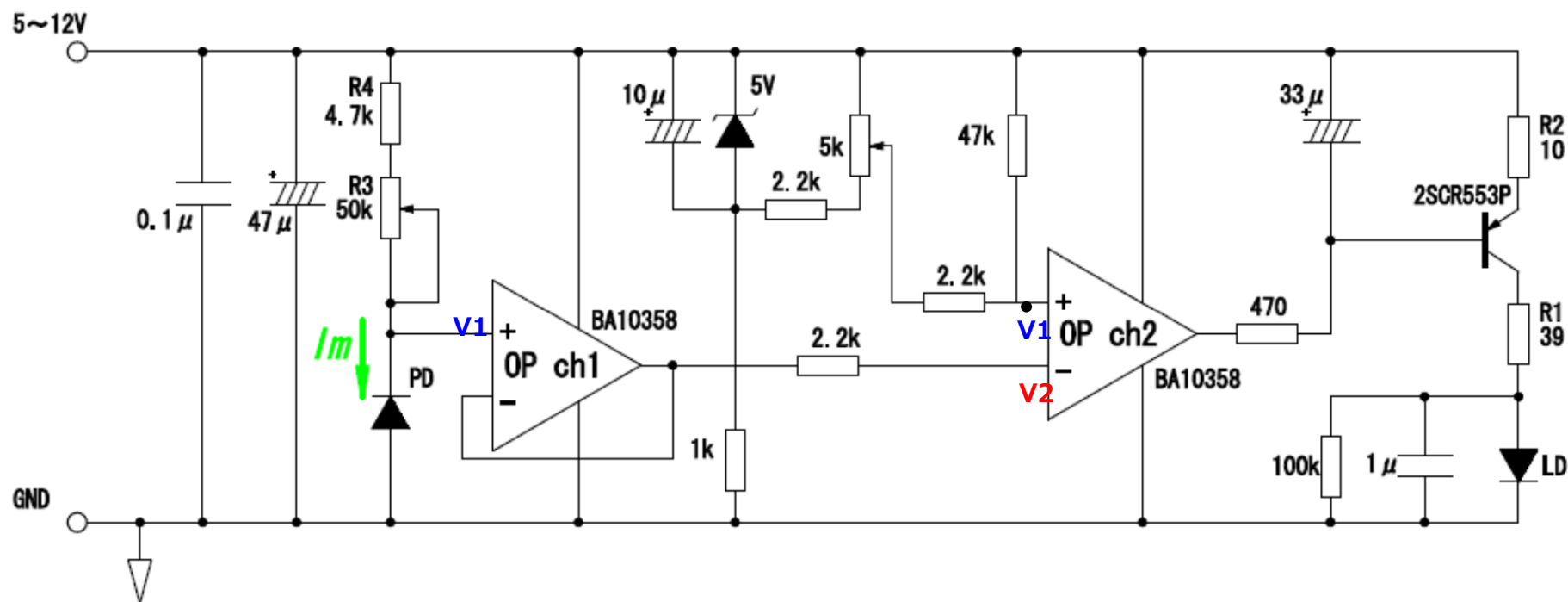Auto Power Control drive circuit example for P type LDs



P type

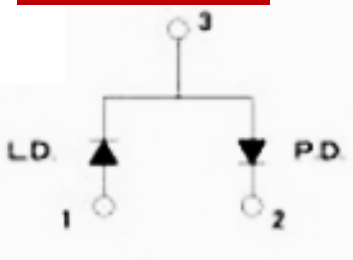

When LD is turned on, monitor current (I_m) flows.


I_m is proportional to the amount of light.

And Voltage become: $V1 = I_m(R3 + R4)$.


At same time, reference voltage $V2$ is generated by zenner diode and volume.

OP2 always control the base current for output transistor so that it is always $V1 = V2$ and constant current flows into LD.

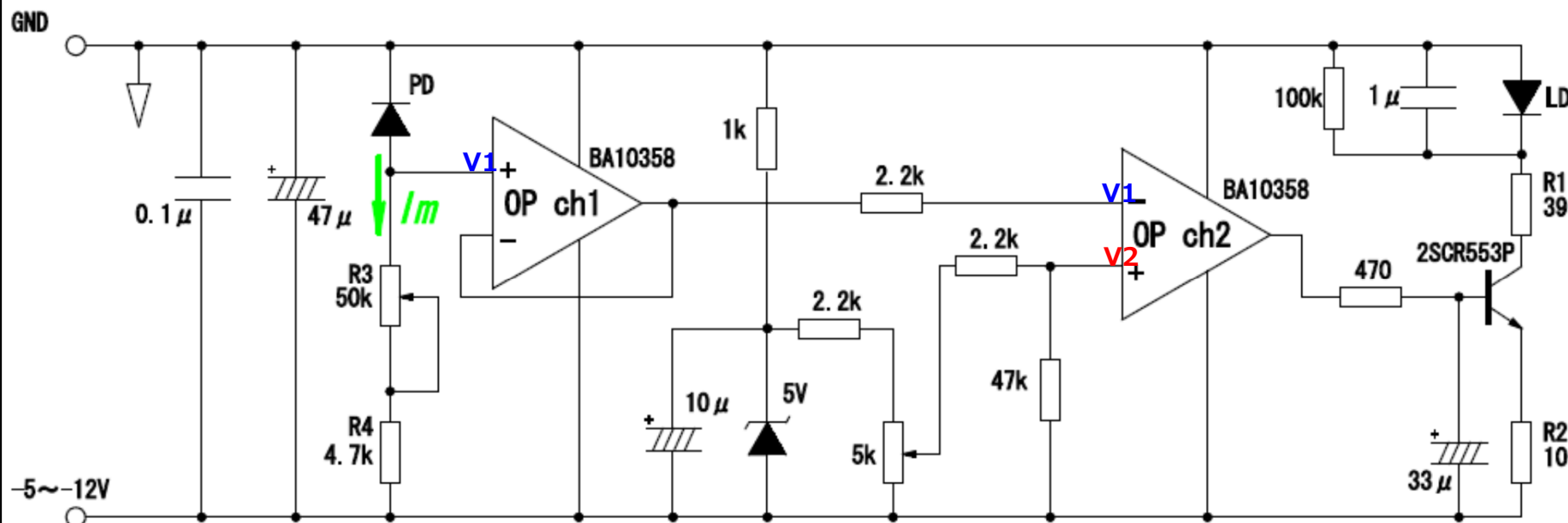Auto Power Control drive circuit example for N type LDs



N type

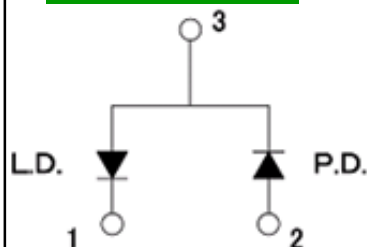

When LD is turned on, monitor current (I_m) flows.


I_m is proportional to the amount of light.

And Voltage become: $V1 = I_m(R3 + R4)$.


At same time, reference voltage $V2$ is generated by zenner diode and volume.

OP2 always control the base current for output transistor so that it is always $V1 = V2$ and constant current flows into LD.

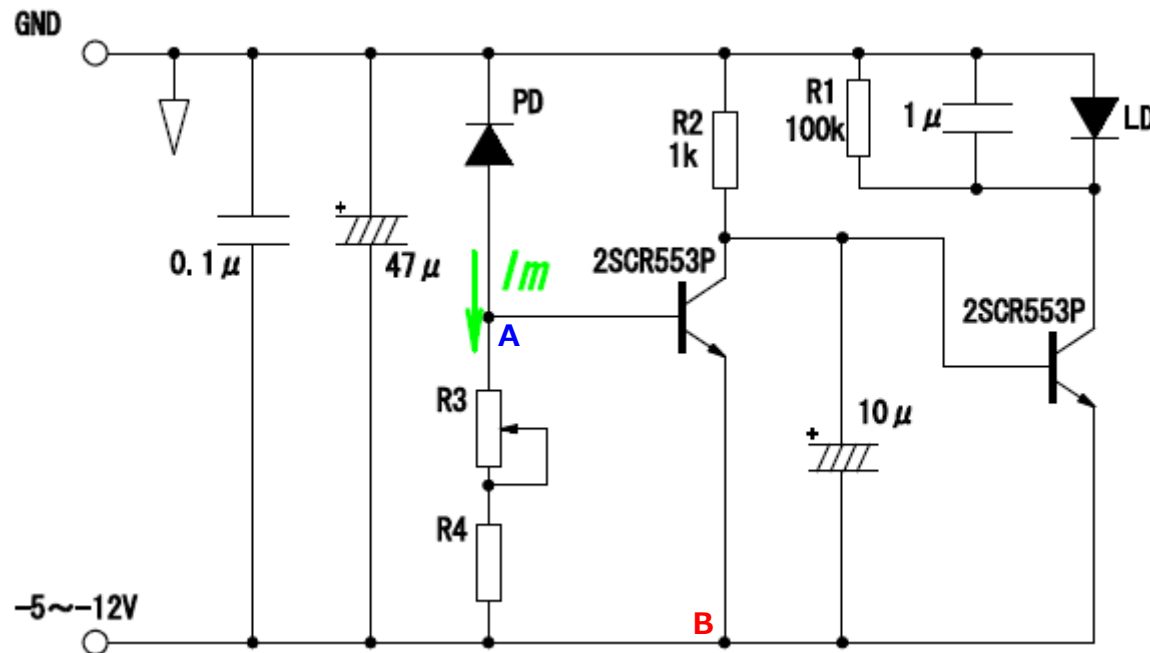Auto Power Control drive circuit example for N type LDs (without Op-amp.)



N type

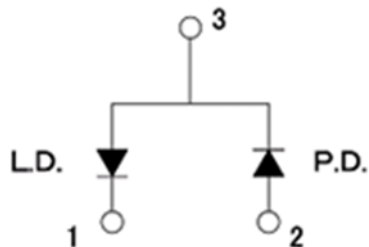

The voltage between A-B will be the one between the base-emitter of the transistor.
(It's about 0.55V in the case of an upper figure.)

For example

Po adjustment area : 0.5- 2 mW

Im of that case : 0.018 - 0.072mA

$$R4 = 0.55/0.072 = 7.64 \quad [\text{k}\Omega]$$

$$R3+R4 = 0.55/0.018 = 30.6 \quad [\text{k}\Omega]$$

$$\therefore R3 = 22.9 \quad [\text{k}\Omega]$$

