

# Designing a Qi-compliant receiver coil for wireless power systems, Part 1

By **Bill Johns**, *Applications Engineer*,  
**Tony Antonacci**, *System Engineer*,  
 and **Kalyan Siddabattula**, *System Engineer*

## Overview

The implementation of the Wireless Power Consortium’s (WPC’s) Qi standard<sup>1</sup> brings wireless power to many different end applications. The receiver (Rx) coil for each application may have different geometries and/or power requirements. Since the Rx coil is a key component in a successful and efficient design of a Qi-compliant Rx and there are many design options and trade-offs to consider, the designer must take a careful and methodical approach when realizing a solution. This article provides the technical insight needed to realize a successful Rx-coil design. It covers the Qi-compliant system model as a basic transformer; Rx-coil measurements and system-level influences; and methods of qualifying a design for successful operation. It is assumed that the reader has a general understanding of the Qi-compliant inductive power system. Background information can be found in Reference 2.

## Qi-compliant system as a transformer

For many near-field wireless power systems such as the one specified by the WPC, the behavior of the magnetic power transfer can be modeled by a simple transformer. A traditional transformer usually has a single physical structure with two windings around a core material that is highly permeable compared to air (Figure 1). Since the traditional transformer uses a highly permeable material to carry the magnetic flux, most (not all) of the flux produced by one coil couples to the second coil. This coupling, which can be measured through a parameter known as the coupling coefficient, is denoted as  $k$  (a measure that can have a value between 0 and 1).

Three parameters define a two-coil transformer:

$L_{11}$  is the self-inductance of coil 1.

$L_{22}$  is the self-inductance of coil 2.

$L_{12}$  is the mutual inductance of coils 1 and 2.

The coefficient for coupling between the two coils can be formulated as


$$k = \frac{L_{12}}{\sqrt{L_{11}L_{22}}} \tag{1}$$

The ideal transformer then can be modeled by using a coupled inductor as shown in Figure 2.


Using the voltage and current relationship of an inductor can provide the nodal equations of this two-coil transformer:

$$V_1 = L_{11} \frac{di_1}{dt} + L_{12} \frac{di_2}{dt} \tag{2a}$$


**Figure 1. Traditional transformer with one physical structure**

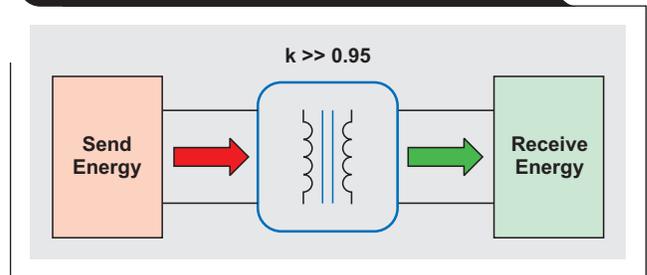

**Figure 2. Ideal model of a traditional transformer**

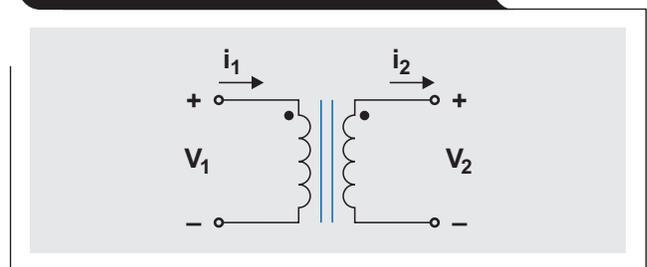

**Figure 3. Cantilever model of a traditional transformer**

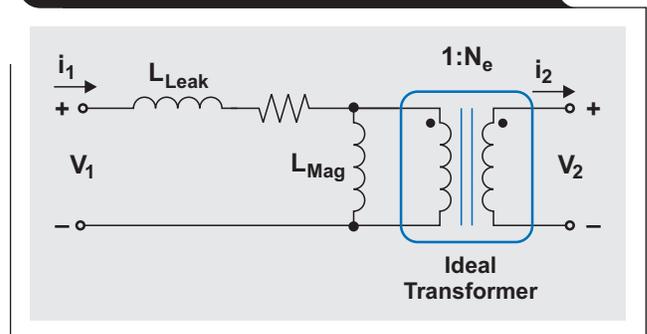

$$V_2 = L_{22} \frac{di_2}{dt} + L_{12} \frac{di_1}{dt} \tag{2b}$$

For circuit analysis, the model in Figure 2 can be represented by what traditionally is referred to as a cantilever model, shown in Figure 3. Here the magnetic coupling and mutual inductance are simplified to leakage and magnetizing inductances. This allows the physical nature of the

coupling to be understood through a circuit implementation. For the ideal transformer, the turns ratio is calculated by using the following equations:

$$N_e = \frac{1}{k} \sqrt{\frac{L_{22}}{L_{11}}} \quad (3a)$$

$$L_{Mag} = k^2 L_{11} \quad (3b)$$

In a tightly coupled system, the leakage inductance is a small percentage of the magnetizing inductance, allowing this parameter to be neglected for a first-order approximation. In addition to high coupling, the series resonant capacitors utilized in the Qi-compliant system reduce the effect of leakage inductance. Therefore, the voltage gain from the primary coil to the secondary coil can be approximated for the first order as

$$\frac{V_2}{V_1} \propto k \sqrt{\frac{L_{22}}{L_{11}}} \quad (4)$$


The transformer in a Qi-compliant system consists of two separate physical devices, the transmitter (Tx) and the receiver (Rx), each with an isolated coil. When a Tx and Rx are placed near one another, they form a coupled-inductor relationship, simply modeled as a two-coil transformer with an air core (Figure 4). The shielding material on both sides serves as a magnetic-flux short. This allows the magnetic field lines (flux) to be contained between the two coils. Figure 5 illustrates a 2D simulation of the magnetic field lines found during typical operation.

For a typical Qi-compliant system, the coupling coefficient ( $k$ ) is much lower than for a traditional transformer. A traditional transformer has coupling in the range of 0.95 to 0.99. For example, 95 to 99% of the magnetic flux couples to the secondary coil; whereas, for a Qi-compliant system, the coupling coefficient is on the order of 0.2 to 0.7, or 20 to 70%. For the most part, the Qi standard attempts to mitigate this lower coupling with a series resonant cap on the Tx and Rx that can compensate for the leakage inductance at resonance.


### Electrical requirements of the Rx coil

In some Rx ICs, the target voltage of the dynamically controlled rectifier varies as a function of the output current. Since the rectifier output dictates the voltage gain needed across the transformer, the highest output voltage on the rectifier must be considered along with the output load, or demand for output power. As shown in Figure 6, the rectifier output varies from ~7 to 5 V over a 1-A load, which sets the required voltage gain across the transformer. It is important to ensure that the Rx coil, when tuned per the WPC specification (see the section “Tuning the Rx coil” later in this article), can achieve this voltage demanded by the Rx IC.


**Figure 4. Simple inductively coupled transformer with an air core**

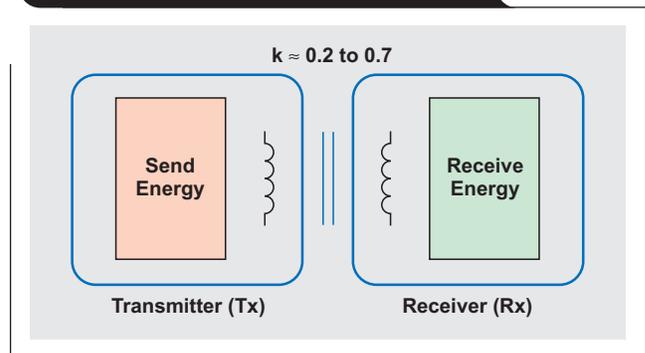

**Figure 5. Example magnetic field lines between two mutually coupled coils**

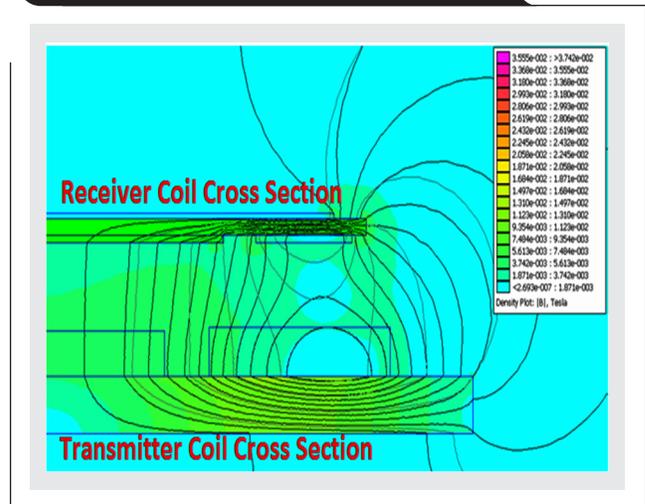

**Figure 6. Rectifier output versus load**

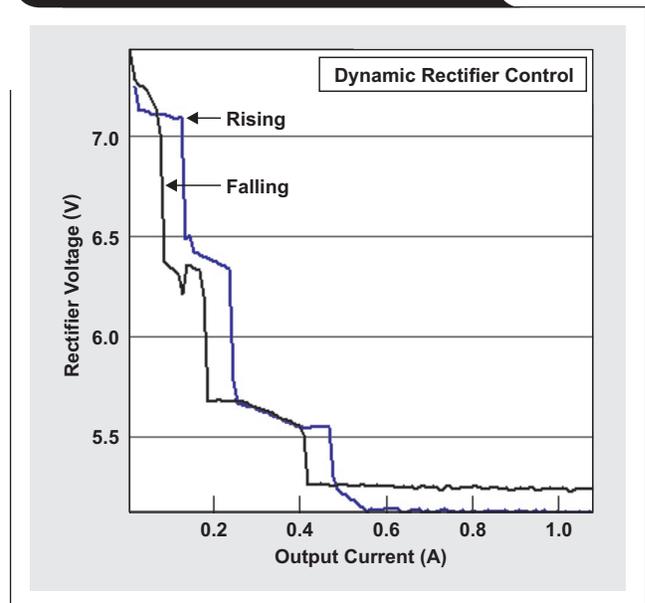

The flowchart in Figure 7 illustrates a recommended approach for specifying a new Rx coil. The design flow has limited choices for the shield, the wire gauge, and the number of turns. Each of these will be discussed next.

### The shield

The shield has two primary functions: (1) providing a low-impedance path for the magnetic flux so that very few flux lines impinge upon surrounding metallic objects, and (2) permitting a higher-inductance coil to be realized with fewer turns so that excessive resistance is not introduced (from additional turns).

Thick shields, which can absorb a large amount of magnetic flux (i.e., they have a high flux saturation point), can be used to prevent heating in the material behind the Rx coil. Thick shields also are less susceptible to drops in efficiency than thinner shields when they encounter a Tx or Rx with a magnet used for alignment. (See the section “Measuring the Rx-coil inductance” later in this article for details on this effect.) Typical materials from vendors such as Vishay, TDK, Panasonic, E&E, Elytone, and Mingstar can help minimize efficiency degradation. Note that high-permeability ferrite materials, such as powdered iron, don’t always perform better than distributed-gap materials. Although ferrite materials have a high permeability, they exhibit a lower flux saturation point when the shield thickness is reduced. This factor must be carefully considered.

### The Rx-coil wire gauge

The choice of wire gauge for the Rx coil is based on cost versus performance. Large-diameter wire or bifilar wire (two parallel wires) can provide high efficiencies but is costly and can result in thick Rx-coil designs. For instance, a PCB coil might be cheaper in overall cost but incurs a much higher equivalent series resistance than a bifilar counterpart.


### The number of turns

Once the wire and shield have been chosen, the number of turns determines the Rx-coil inductance. Coil inductance and coupling determine the voltage gain observed at the Rx’s rectifier output as well as the total available power to the Rx. This voltage-gain target is shown in Figure 6.

Three procedures offer a general approach to determine the inductance target:

1. The Tx’s type-A1 coil should be used as the basis for the primary coil’s characteristics (for example, 1500-mm<sup>2</sup> area, 24- $\mu$ H inductance, and 19-V primary voltage).
2. When a shield material with a permeability significantly higher than air ( $>20$ ) is used, the coil area is a good proxy for the coupling coefficient. Note that this only applies to planar coils with either a single layer or two layers of turns. Exotic coil structures do not utilize this principle. In order to ensure a reasonable coupling and high efficiency, an Rx coil can be used with an area approximately 70 to 80% of the area of A1 coil for a 5-W system. This ensures a coupling coefficient of approximately 50% for most reasonable designs with a distance,

**Figure 7. Flowchart of methodology for Rx-coil design**

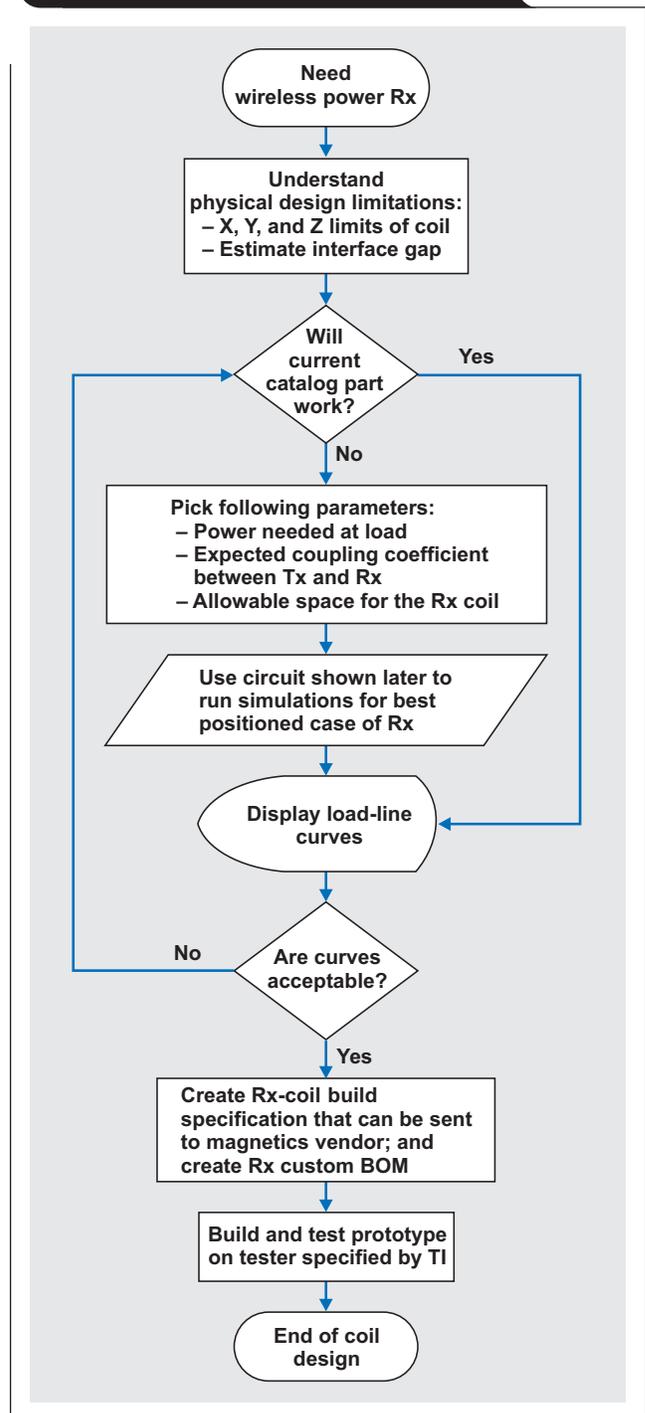

$d_z$ , of up to 5 mm between the Tx and Rx coils as specified by the WPC.

3. The desired voltage gain is determined based on the average expected rectifier voltage—for example, 6 V found in the plot in Figure 6. In this example case, the voltage gain is  $\sim 0.32$  (6 V/19 V).

A typical design for a 5-V/5-W output-voltage system shows that with the coupling coefficient around 0.5, a secondary inductance of about 10  $\mu\text{H}$  is sufficient to produce the target voltages required. There are two relationships to consider in the system design:

$$V_2 \propto kV_{\text{IN}}\sqrt{\frac{L_{22}}{L_{11}}} \quad (5a)$$

$$L_{22} \propto N_2^2 \quad (5b)$$

Therefore, if the coupling coefficient is changed from 0.5 to 0.4, the inductance for the same power output can increase by up to 1.6 times the previous inductance. This means that the new inductance is  $\sim 16 \mu\text{H}$ . As shown in Equation 5b, coil inductance is proportional to the number of coil turns squared.

Table 1 shows the secondary inductance and coupling for some common coils designed for the system.

**Table 1. Examples of typical coils**

COIL DIMENSIONS (mm)	TURNS	V <sub>OUT</sub> (V)	P <sub>OUT</sub> (W)	L <sub>22</sub> ( $\mu\text{H}$ )	k
48 × 32	15	5	5	12	~0.6
28 × 14	24	5	2.5	33	~0.25
35 × 35	24	7	5	22	~0.5

One caveat is that these rules of thumb apply to general planar coils and are preliminary, meant to serve as a starting point for a design. The actual design is best optimized by using simulation tools, as shown in the flowchart in Figure 7.

## Measuring the Rx-coil inductance


The Rx-coil inductance is a very important parameter that dictates the electrical response (such as voltage gain and output impedance) of the Rx AC/DC power stage. To preserve a consistent response, the inductance must minimally

vary in different system scenarios. Due to the interoperability nature of the Qi standard, the Rx coil can be placed on many different types of Tx's that may influence the Rx-coil inductance—and hence the electrical response.

Per Section 4.2.2.1 of the WPC specification,<sup>1</sup> the Rx-coil inductance,  $L'_S$ , is measured with the test configuration in Figure 8. The spacer and Tx shield provide a reference to emulate Tx components near the Rx coil. In this test configuration, the Tx shield is a  $50 \times 50 \times 1\text{-mm}$  piece of ferrite material (PC44) from TDK Corporation. The gap  $d_z$  is set to 3.4 mm by means of a nonmetallic spacer. The Rx coil is then placed on the spacer, and  $L'_S$  is measured with a stimulus of 1-V RMS and 100 kHz. In addition, the free-space Rx-coil inductance,  $L_S$ , is measured without the Tx shield.

What is not detailed in the WPC specification is the influence of common system scenarios on the  $L'_S$  and  $L_S$  measurements. The most common influence on these parameters is the presence of a battery behind the Rx coil. Due to the casing material and the battery cell's makeup, the Rx-coil inductance generally is reduced when the battery is placed behind it. In addition to the battery, the presence of a magnet on a Tx-coil structure influences the inductance. (See Section 3.2.1.1.4 of the WPC specification.<sup>1</sup>) The magnet functions as a stressor on the Rx-coil shielding material where the shield's magnetic saturation point is of key interest. If the Rx-coil shielding material saturates when a magnet is present, the coil inductance drops dramatically. Because the Qi standard specifies Tx coil assemblies with and without a magnet, the designer needs to understand how the inductance varies in both scenarios, as any shift in inductance will shift the resonant tuning of the Rx. Note that the test configuration in Figure 8 does not include a magnet. When a magnet is included, its flux density should be between 75 and 150 mT and its diameter should be a maximum of 15.5 mm. This means that the typical 30-mT magnetic field of the Tx coil during power transfer is about 20% of the magnet's field strength.

**Figure 8. Test configuration for measuring Rx-coil inductance ( $L'_S$ )**

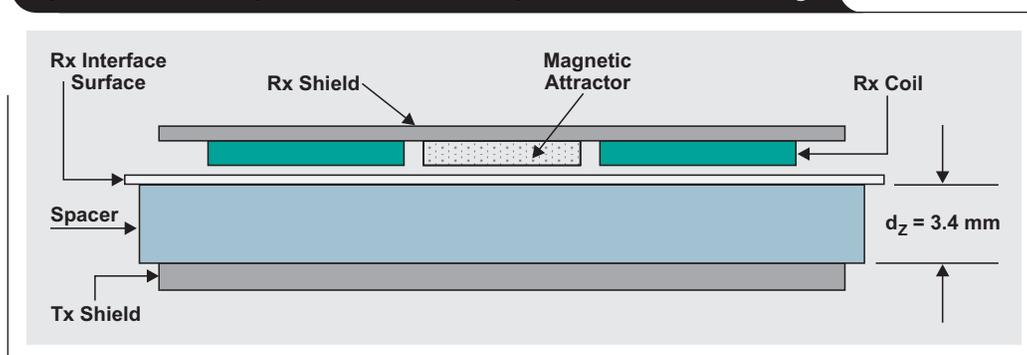

**Table 2. Rx-coil-inductance parameters to be measured during development**

PARAMETER	Rx COIL WITH Tx SHIELD	Rx COIL WITHOUT Tx SHIELD	BATTERY	MAGNET	SUMMARY
L <sub>S</sub> '	Included	—	—	—	Standard L <sub>S</sub> ' measurement
L <sub>S</sub> '_m	Included	—	—	Included	Exposes the effect of the magnet
L <sub>S</sub> '_b	Included	—	Included	—	Exposes the effect of the battery
L <sub>S</sub> '_m_b	Included	—	Included	Included	Exposes the effect of the battery and the magnet together
L <sub>S</sub>	—	Included	—	—	Standard L <sub>S</sub> measurement
L <sub>S</sub> _b	—	Included	Included	—	Exposes the effect of the battery

For the purpose of understanding the performance of the Rx-coil inductance, Table 2 defines parameters in addition to the recommended measurements of L<sub>S</sub>' and L<sub>S</sub>. When the battery is introduced into the measurement, it should be placed in the same orientation/location as it will be in the final system. Note that the materials used in the final industrial design could also influence the final inductance measurement. Therefore, when the tuning circuit is configured, all components of the final industrial design of the mobile device should be used for the final measurement. The measurements found in Table 1 can be used to screen and qualify potential Rx coils.

Table 3 summarizes the measured inductances from an acceptable coil design and the resonant frequency with a fixed series and parallel resonant capacitor. Here L<sub>S</sub>'\_b was used for the capacitor calculations. (See the next section, "Tuning the Rx coil," for details.) Note that the variation could be linearly scaled as a percentage of L<sub>S</sub>' and used as a reference for acceptance of a prototype coil.

**Tuning the Rx coil**

The simplified Rx-coil network consists of a series resonant capacitor, C<sub>1</sub>, and a parallel resonant capacitor, C<sub>2</sub>. These two capacitors make up the dual resonant circuit with the Rx coil (see Figure 9) and must be sized correctly per the WPC specification.

To calculate C<sub>1</sub>, the resonant frequency of 100 kHz is used along with L<sub>S</sub>':

$$C_1 = \frac{1}{(100 \text{ kHz} \times 2\pi)^2 \times L'_S} \tag{6}$$

**Table 3. Measured inductances of a sample coil**

	L <sub>S</sub> '	L <sub>S</sub> '_m	L <sub>S</sub> '_b	L <sub>S</sub> '_m_b	L <sub>S</sub>	L <sub>S</sub> _b
Inductance (μH)	12.9	13.1	10.5	10.6	10.9	9.52
Resonance (kHz)	90.15	89.63	100	99.72	98.15	105.02

To calculate C<sub>2</sub>, a secondary resonance of 1.0 MHz is used along with L<sub>S</sub>. This calculation requires that C<sub>1</sub> be determined first and used in Equation 7:

$$C_2 = \frac{1}{(1.0 \text{ MHz} \times 2\pi)^2 \times \left(L_S - \frac{1}{C_1}\right)} \tag{7}$$

Finally, the quality factor must be greater than 77 and is calculated as


$$Q = \frac{2\pi \times 1.0 \text{ MHz} \times L_S}{R}, \tag{8}$$

where R is the DC resistance of the coil.

**Load-line analysis of the Rx coil**

When choosing an Rx coil, a designer needs to understand the transformer characteristics by comparing the primary and Rx coils via load-line analysis (I-V curves). This analysis captures two important conditions in the Qi-compliant system: (1) operating-point characteristics and (2) transient response. These will be discussed next.

**Figure 9. Dual resonant circuit with Rx coil**

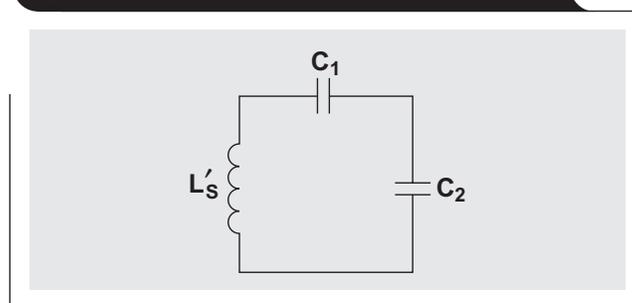

### Operating-point characteristics

An example test configuration for conducting load-line analysis is shown in Figure 10, whose parameters are defined as follows:

$V_{IN}$  is an AC power source that should have a peak-to-peak operation of 19 V.

$C_P$  is the primary series-resonant capacitor (100 nF for type-A1 coil).

$L_P$  is the primary coil of interest (type A1).

$L_S$  is the secondary coil of interest.

$C_1$  is the series resonant capacitor chosen for the Rx coil under test.

$C_2$  is the parallel resonant capacitor chosen for the Rx coil under test.

$C_B$  is the bulk capacitor for the diode bridge.  $C_B$  should be at least 10  $\mu$ F at 25 V.


V is a Kelvin-connected voltage meter.

A is a series ammeter.

$R_L$  is the load of interest.

The diode bridge should be constructed of Schottky diodes in either a full bridge or a synchronous half bridge with low-side n-type MOSFETs and high-side Schottkys. Three test procedures are used for the analysis:


**Figure 10. Test setup for load-line analysis**

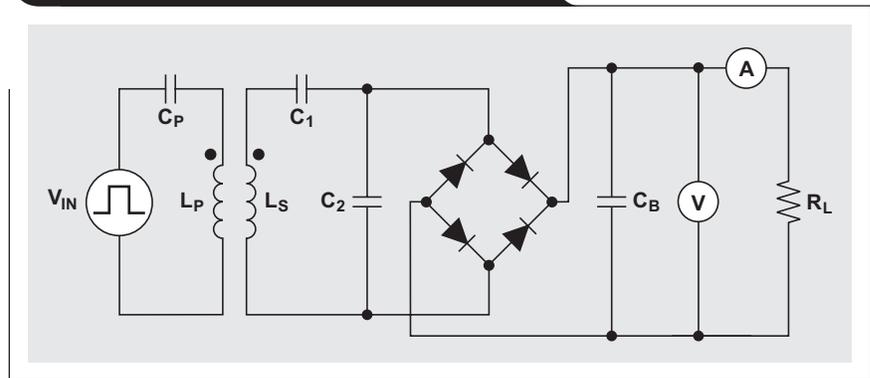

1. A 19-V AC signal is supplied to  $L_P$ , starting at a frequency of 200 kHz.
2. The resulting rectified voltage is measured from no load to the expected full load.
3. The preceding two steps are repeated for lower frequencies, stopping at 110 kHz.

An example load-line analysis is shown in Figure 11. The plot conveys that specific load and rectifier conditions result in a specific operating frequency. For example, at

**Figure 11. Results of example load-line analysis**

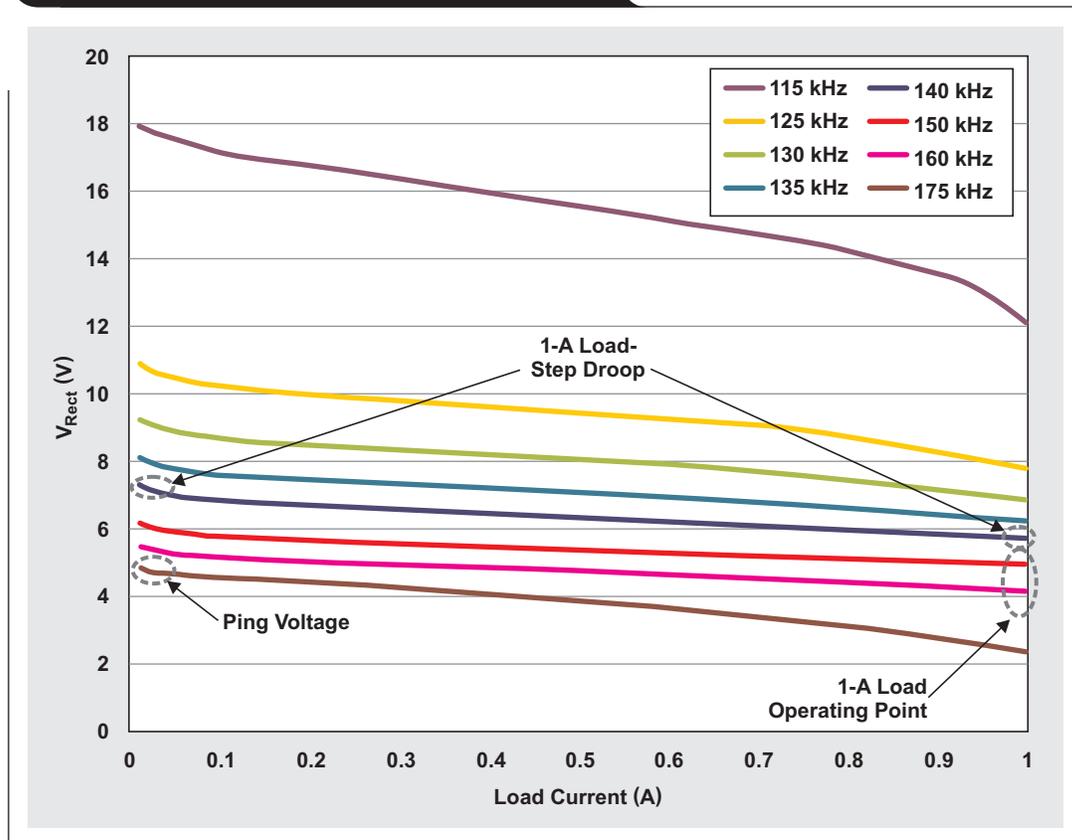

1 A, the target for the dynamic rectifier is 5.15 V. Therefore, the operating frequency is between 150 and 160 kHz, which is an acceptable operating point. If the operating point falls outside the WPC-specified frequency range of 110 to 205 kHz, the system will never converge and will become unstable.

**Transient response**

For transient analysis, there are two major points of interest, shown in Figure 11: (1) the rectifier voltage at the ping frequency (175 kHz), and (2) the rectifier voltage droop from no load to full load at the constant operating point.

In this example, the ping voltage is ~5 V. This is above the  $V_{UVLO}$  of the chip. Therefore, start-up in the Qi-compliant system can be guaranteed. If the voltage is near or below the  $V_{UVLO}$  at this frequency, start-up may not occur.

If the maximum load step is 1 A, the droop in this example is ~1 V with a voltage of 6 V at the 140-kHz load line in Figure 11. To analyze the droop, the 140-kHz load line that starts at 7 V at no load is followed to the maximum load current expected. Droop voltage is the difference between the voltages at the ends of the load line. Acceptable full-load voltage at the selected operating frequency should be above 5 V. If it descends below 5 V, the power-supply output also droops to this level. This type of analysis for transient response is necessary due to the Qi-compliant system's slow feedback response. The analysis simulates the step response that would occur if the system did not adjust the operating point of the resonant transformer.

Note that coupling between the primary and secondary coils worsens with Rx-coil misalignment. Therefore, an additional analysis of the load lines at multiple misalignments is recommended to determine where in the planar space the Rx discontinues operation.

**Conclusion**

This article has shown that traditional transfer fundamentals can be employed to simplify the design of Rx coils for wireless power systems. However, the nature of interoperability and mobile-device characteristics can impose unique

deviations from standard magnetics design practices. Identifying and addressing coil-design details up front increases the probability of greater success on the first pass. The evaluation methods introduced allow specification and characterization of a custom Rx coil in a very methodical approach.

Part 2 of this article series will provide design details of different types of custom Rx coils. The results will exercise the methods and theory presented in Part 1.

**References**

For more information related to this article, you can download an Acrobat® Reader® file at [www.ti.com/lit/litnumber](http://www.ti.com/lit/litnumber) and replace “*litnumber*” with the **TI Lit. #** for the materials listed below.

<b>Document Title</b>	<b>TI Lit. #</b>
1. Wireless Power Consortium, “System Description Wireless Power Transfer, Vol. I, Part 1,” Version 1.1, March 2012 [Online]. Available: <a href="http://www.wirelesspowerconsortium.com/downloads/wireless-power-specification-part-1.html">http://www.wirelesspowerconsortium.com/downloads/wireless-power-specification-part-1.html</a>	—
2. Bill Johns, “An introduction to the Wireless Power Consortium standard and TI’s compliant solutions,” <i>Analog Applications Journal</i> (1Q 2011).....	SLYT401

**Related Web sites**

- [www.ti.com/bqtesla](http://www.ti.com/bqtesla)
- [www.ti.com/product/bq500210](http://www.ti.com/product/bq500210)
- [www.ti.com/product/bq51013A](http://www.ti.com/product/bq51013A)

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>

### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	<a href="http://www.ti.com/asktexas">www.ti.com/asktexas</a>
Direct Email	<a href="mailto:asktexas@ti.com">asktexas@ti.com</a>

### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>
	Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>

### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E is a trademark of Texas Instruments. Acrobat and Reader are registered trademarks of Adobe Systems Incorporated. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46C and to discontinue any product or service per JESD48B. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components which meet ISO/TS16949 requirements, mainly for automotive use. Components which have not been so designated are neither designed nor intended for automotive use; and TI will not be responsible for any failure of such components to meet such requirements.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

**TI E2E Community** [e2e.ti.com](http://e2e.ti.com)