

# AN1362: Si828x XM3 Gate Driver Test Report

This test report documents the testing performed at Skyworks with support from Wolfspeed's XM3 module team. It details the operations of Skyworks' Si828x isolated gate drivers and Wolfspeed's half-bridge Silicon Carbide (SiC) Field Effect Transistor (FET) XM3 module. It reveals the Si828x's robust short-circuit protection feature and the rugged SiC XM3 module, enabling the system to survive and operate well under extreme short-circuit conditions. The test report also includes the Si828x-XM3's performance in switching loss, crosstalk, and common-mode immunity (CMTI) tests in a half-bridge configuration.

#### KEY FEATURES

- Robust short circuit protection and common-mode transient immunity
- High current handling capability and rugged reliability
- Complete modular design in a half-bridge configuration

1

The test platform comprises Skyworks' Si828x-AW-GDB half-bridge gate driver evaluation board (Daughter Card) and Wolfspeed's CIL XM3 Evaluation Board (Motherboard). The XM3 SiC FET module is mounted under Wolfspeed's XM3 Motherboard. The XM3 Mother Board has holes lined up with the XM3 module's terminals and allows Skyworks' Si828x-AW-GDB board on the top to plug directly onto the XM3 module on the bottom. This design provides the optimum interconnection between the Si828x gate drivers and the XM3 module to minimize parasitic inductance in the gate driver circuits.



# **Table of Contents**

1.	Test Circuits
	1.1 Si828x Isolated Gate Driver
	1.2 XM3 Module
	1.3 Wolfspeeds CIL XM3 Evaluation Board Motherboard
2.	Short Circuit Testing
	2.1 Test Setup
	2.2 Short Circuit Test Results
3.	Crosstalk
	3.1 Crosstalk Board Setup
	3.2 Crosstalk Test Results
4.	Switching Loss Testing
	4.1 Switching Loss Board Setup
	4.2 Switching Loss Test Results
5.	Conclusion

# 1. Test Circuits

#### 1.1 Si828x Isolated Gate Driver

Skyworks' Si828x family are full-featured isolated gate drivers. The Si828x has different variants to support a wide range of power switching circuits. The Skyworks Si828x-AW-GDB evaluation board includes the Si8285 to drive the high-side XM3 SiC FET and the Si8284 to drive the low-side XM3 SiC FET. The Si8284 also has an integrated dc-dc controller that operates with an external transformer circuit to generate bias voltages for the low- and high-side gate drivers. An external current booster circuit consisting of bipolar transistors is included on the Si828x-AW-GDB board to amplify the Si828x's ±4 A gate current drive to ±15 A in order to drive the large XM3 SiC FET module (see Figure 1.3 Si828x Enhanced Gate Drive Circuits, including Current Booster on page 5).



Figure 1.1. Si8285 High-Side Gate Driver



Figure 1.2. Si8284 Low-Side Gate Driver with DC-DC Controller (RSN and ESW Pins)



Figure 1.3. Si828x Enhanced Gate Drive Circuits, including Current Booster



Figure 1.4. Si8284 DC-DC External Circuits

![](_page_5_Figure_3.jpeg)

Figure 1.5. Si828x-AW-GDB Evaluation Board

For more information on the Si828x's advanced gate drive capabilities, see "AN1288: Si828x External Enhancement Circuits".

#### 1.2 XM3 Module

Wolfspeed's CAB450M12XM3 half-bridge SiC module was evaluated in this test. It has the following electrical rating: Rds-on =  $3.7 \text{ m}\Omega$ ,  $V_{DS} = 1.2 \text{ kV}$ ,  $I_{DS} = 450 \text{ A}$ . For more details about this module, go to https://www.wolfspeed.com/xm3-power-module-family.

![](_page_6_Picture_3.jpeg)

Figure 1.6. Wolfspeed's CAB450M12XM3 Half-Bridge SiC Module

AN1362: Si828x XM3 Gate Driver Test Report • Test Circuits

# 1.3 Wolfspeeds CIL XM3 Evaluation Board Motherboard

The figure below shows a simplified schematic of Wolfspeed's KIT-CRD-CIL12N-XM3 evaluation board. The board's layout is optimized for low parasitic inductance (Figure 8) with minimum interconnect trace distances between the bulk capacitors, the high-frequency bypass capacitors, and the high bandwidth current measurement via current viewing resistor (CVR). Finally, the board has a Kelvin high-frequency  $V_{DS}$  voltage measurement point BCN connector to simplify the  $V_{DS}$  oscilloscope probe connection and connection points for the inductor,  $L_{O}$ .

![](_page_7_Figure_3.jpeg)

Figure 1.7. Wolfspeed's KIT-CRD-CIL12N-XM3 Simplified Schematic

![](_page_7_Figure_5.jpeg)

Figure 1.8. Wolfspeed's KIT-CRD-CIL12N-XM3 CIL Evaluation Board

For more information on Wolfspeed's KIT-CRD-CIL12N-XM3 CIL Evaluation Board and the test apparatus, see the CIL CPWR-AN31 User Guide.

AN1362: Si828x XM3 Gate Driver Test Report • Short Circuit Testing

# 2. Short Circuit Testing

The short circuit testing was performed by creating a low-impedance connection across the low-side XM3 half-bridge SiC FET module, as shown in the figures below. This simulates a washer short condition where a piece of electrically conducting wire or a washer falls between the V– and VMID terminals of the XM3 module. The high-side SiC short condition is not possible due to the position of the XM3 terminals. A physical washer short across the high-side (V+ to MID) is not feasible; therefore, testing on the high-side short condition was not conducted.

#### 2.1 Test Setup

VDDB Due to the XM3's sizable gate charge characteris-DSAT Thtics, the Si828x circuits have some external com-VMI To Drive<u>r 2</u> ponents to increase the current drive and provide VDDB control to the XM3 SiC FET gates. Below are short RI 01 VH descriptions of the external components: Ē 1. Q1 and Q2: Increase current drive Si8284 **S1** RH Driver 1 Shorting l**⊲**j2 RI: sets DESAT detection timing Wire RL 02 3. RSS: set soft shutdown timing RSS (washer short) 4. RH: sets turn-on switching speed U3 5. RL: set turn-off switching speed M\_CLMP

Figure 2.1. Simplified Schematic of the Driver Circuit and a Shorted Upper SiC MOSFET

- VSSB

![](_page_8_Picture_6.jpeg)

+ RAIL

Cooper bus short across the low-side XM3 half-

nals)

bridge SiC FET module (Half-Bridge - to MID termi-

#### Figure 2.2. Low-Side Short Circuit Setup with Large Copper Bus Bar

The Si828x gate driver circuits can be tuned to provide robust protection against short-circuit conditions. The tuning process requires selecting the component, described in the simplified driver circuit schematic above, to achieve a DESAT response time of less than 1  $\mu$ s (from the time the I<sub>DS</sub> current goes above 0 A and back to 0 A) while ensuring that the I<sub>DS</sub> peak current and the V<sub>DS</sub> voltage spike levels stay below the XM3's rating. This tuning process is documented in AN1288: Si828x External Enhancement Circuits.

#### 2.2 Short Circuit Test Results

Table 2.1 DESAT Test Results on page 10 and the following scope plots summarize three data points for consideration. Notice from the data in the table that the values of RI control the Si828x detection time directly. Additionally, since the  $I_{DS}$  peak current is directly proportional to the detection time,  $I_{DS}$  peak current is also affected by the value of RI. The RSS value controls the SSD duration (Soft Shutdown duration) and the V<sub>DS</sub> voltage spike. The RSS value has some effect on the IDS peak current as well.

Due to the optimized layout of the KIT-CRD-CIL12N-XM3 CIL evaluation board plus the XM3 module's internal low parasitic inductance, the  $V_{DS}$  voltage spike is insignificant in all tests cases. This low-voltage spike allows short circuit tests at 1 kV dc rail. Bear in mind that application circuits with larger parasitic inductance induce higher voltage spikes; therefore, larger RSS or reduced operating dc rail may be required to ensure that the  $V_{DS}$  voltage spike is kept below the XM3 voltage rating.

Si828x DESAT performance for all test cases summarized in the table below demonstrates that the Si828x protected the XM3 well. However, for slightly lower power dissipation (larger RSS value), the Skyworks Si828x-AW-GDB evaluation board is built with the component values listed in Figure 2.3.

Figure #	RI	R <sub>SS</sub>	R <sub>H</sub>	RL	Response	Detection	SSD	+ DC Rail	V <sub>DS</sub> Spike	I <sub>DS</sub> Peak
2.2	3.3 kΩ	4.02	1	1	800 ns	320 ns	800 ns	1000 V	1040 V	900 A
2.3	2.2 kΩ	1	1	1	560 ns	280 ns	600 ns	1000 V	1075 V	650 A
2.4	2.2 kΩ	4.02	1	1	625 ns	280 ns	800 ns	1000 V	1040 V	675 A

![](_page_9_Figure_6.jpeg)

Table 2.1. DESAT Test Results

Figure 2.3. Si828x 800 ns DESAT response time with RI = 3.3 kΩ, RH = RL = 1 Ω, RSS = 4.02 Ω

![](_page_10_Figure_1.jpeg)

Figure 2.4. Si828x 560 ns DESAT response time with RI = 2.2 k $\Omega$ , RH = RL = 1  $\Omega$ , RSS = 1  $\Omega$ 

![](_page_11_Figure_1.jpeg)

Figure 2.5. Si828x 625 ns DESAT response time with RI = 2.2 k $\Omega$ , RH = RL = 1  $\Omega$ , RSS = 4.02  $\Omega$ 

### 3. Crosstalk

In the XM3 half-bridge power circuit shown in the figure below, the S1 and S2 switching devices are stacked up in series and are connected to the high voltage Vdc. In this configuration, there must be only one switching device in the on-state at any point in time. If both S1 and S2 are on simultaneously, substantial current flow from Vdc through S1 and S2 can cause excessive power loss and possible damage to the S1 and S2 (a condition known as a current shoot-through). The PWM signals that drive the gates of S1 and S2 are conditioned to absolutely avoid turning on both S1 and S2 at the same time. However, during S2 high-speed turn-on (S1 is turning off), the voltage at the MID terminal is rapidly going toward Vdc + (large dv/dt) and induces Miller current flow through the gate of S1, across RL and generates a positive voltage at the gate of S1. Depending on the dv/dt level and the total impedance in series with RL, the Miller voltage spike can become larger than the gate threshold voltage (Vth), turn on S1 momentarily, and cause shoot-through current across S1 and S2. A similar condition occurs in the opposite switching condition when S1 turns on while S2 turns off and can cause a shoot-through condition as well.

The Si828x gate driver has bipolar power supplies to provide a negative voltage to the gate of S1 or S2 in the Off state to alleviate the effect of the Miller voltage spike. It is essential to validate that the Miller voltage spike at the gate can never go above the XM3 gate threshold voltage.

#### 3.1 Crosstalk Board Setup

The figure below illustrates the crosstalk test circuit. In this test, S1 was held in the Off state while a function generator controlled the gate of S2. The gate voltage of S1 was monitored while S2 was switched. The current in the inductor Lo grew as S2 was pulsed on multiple times and allowed crosstalk testing at the different current levels.

![](_page_12_Figure_6.jpeg)

Figure 3.1. Crosstalk Test Circuit

AN1362: Si828x XM3 Gate Driver Test Report • Crosstalk

#### 3.2 Crosstalk Test Results

The following scope plots show the behavior of the lower gate S1 as the upper S2 SiC FET is turned on.

![](_page_13_Figure_3.jpeg)

Figure 3.2. Crosstalk Test RH = RL = 1  $\Omega$ , V<sub>DS</sub> = 600 V, Lo = 14  $\mu$ H

![](_page_13_Figure_5.jpeg)

Figure 3.3. Crosstalk Test RH = RL = 1  $\Omega$ , V<sub>DS</sub> = 600 V, Lo = 14 $\mu$ H, I<sub>DS</sub> = 400 A (Zoomed)

![](_page_14_Figure_1.jpeg)

Figure 3.4. Crosstalk Test RH = RL = 1  $\Omega$ , V<sub>DS</sub> = 800 V, Lo = 14 $\mu$ H

![](_page_14_Figure_3.jpeg)

Figure 3.5. Crosstalk Test RH = RL = 1  $\Omega$ , V<sub>DS</sub> = 800 V, I<sub>DS</sub> = 400A, Lo = 14  $\mu$ H (Zoomed)

![](_page_15_Figure_1.jpeg)

Figure 3.6. Crosstalk Test RH = RL = 0  $\Omega$ , V<sub>DS</sub> = 600 V, Lo = 14 $\mu$ H

![](_page_15_Figure_3.jpeg)

Figure 3.7. Crosstalk Test RH = RL = 0  $\Omega$ , V<sub>DS</sub> = 600 V, I<sub>DS</sub> = 400A, Lo = 14  $\mu$ H (Zoomed)

![](_page_16_Figure_1.jpeg)

Figure 3.8. Crosstalk Test RH = RL = 0  $\Omega$ , V<sub>DS</sub> = 800 V, Lo = 14  $\mu$ H

![](_page_16_Figure_3.jpeg)

Figure 3.9. Crosstalk Test RH = RL = 0  $\Omega$ , V<sub>DS</sub> = 800 V, Lo = 14  $\mu$ H (Zoomed)

AN1362: Si828x XM3 Gate Driver Test Report • Crosstalk

The table below summarizes the crosstalk test data. It shows that even under extreme conditions with 0  $\Omega$  gate resistors and dv/dt = 25 V/ns the driver can keep the low-side XM3 SiC MOSFET safely turned off at < -2 V, which is well below the minimum XM3 threshold voltage of Vth = 2 V.

Figure #	R <sub>H</sub>	RL	Vdc (V)	IDS (A)	dv/dt (kV/ns)	VG-max (V)
15	1	1	600	200	17	-2.2
15 (Z)	1	1	600	400	16	-2.4
16	1	1	800	200	16	-2.4
16 (Z)	1	1	800	400	16	-2.4
17	0	0	600	200	25	-1.9
17 (Z)	0	0	800	400	23.5	-2.1
18	0	0	600	200	23	-2.2
18 (Z)	0	0	800	400	23	-2.2

# Table 3.1. Crosstalk Test Results

# 4. Switching Loss Testing

Switching loss testing was performed using a double-pulse test circuit, as illustrated in the figure below. This test measures the XM3 power loss during switching. Compared to the data sheet's XM3 switching loss, it verifies that the gate drivers have sufficient source and sink current capability to drive the XM3 SiC FET module with minimum switching loss.

![](_page_18_Figure_3.jpeg)

Figure 4.1. Switching Loss Test Circuit

#### 4.1 Switching Loss Board Setup

In this test, S1 and S2 were driven by a two channel function generator to build up current through the air-core Lo inductor. Every time S1 is switched on (S2 is switched off), the current in Lo is ramped up and when S1 is switched off (S2 is switched on), Lo current is maintained through S2. This cycle is repeated multiple times to facilitate switching loss measurement on S1 at different current levels.

AN1362: Si828x XM3 Gate Driver Test Report • Switching Loss Testing

#### 4.2 Switching Loss Test Results

An oscilloscope was used for switching loss measurements. The oscilloscope's math function integrates the product of S1's  $V_{DS}$  and  $I_{DS}$  over time to provide switching loss data. The scope image in the following figure indicates that S1 was turned on five times to ramp the  $I_{DS}$  current for switching loss measurement.

![](_page_19_Figure_3.jpeg)

Figure 4.2. Switching Loss Test RH = RL = 1  $\Omega$ , I<sub>DS</sub> = 0 A-760 A, Lo = 14  $\mu$ H (V<sub>DS</sub> = 600 V)

![](_page_20_Figure_1.jpeg)

Figure 4.3. Eoff Loss RH = RL = 1  $\Omega,$  I\_DS = 520 A, Lo = 14  $\mu H,$  (V\_DS = 600 V)

![](_page_20_Figure_3.jpeg)

Figure 4.4. Switching Loss vs. Drain Current RH = RL = 1  $\Omega$  (V<sub>DS</sub> = 600 V)

![](_page_21_Figure_1.jpeg)

Figure 4.5. Eoff Loss RH = RL = 1  $\Omega$ , I<sub>DS</sub> = 520 A, Lo = 14  $\mu$ H (V<sub>DS</sub> = 800 V)

![](_page_21_Figure_3.jpeg)

Figure 4.6. Switching Loss vs. Drain Current RH = RL = 1  $\Omega$  (V<sub>DS</sub> = 800 V)

![](_page_22_Figure_1.jpeg)

Figure 4.7. Eon Loss RH = RL = 0.5  $\Omega,$   $I_{DS}$  = 440 A (V\_{DS} = 600 V)

![](_page_22_Figure_3.jpeg)

Figure 4.8. Switching Loss vs. Drain Current RH = RL = 0.5  $\Omega$  (V<sub>DS</sub> = 600 V)

![](_page_23_Figure_1.jpeg)

Figure 4.9. Eon Loss RH = RL = 0.5  $\Omega$ , I<sub>DS</sub> = 480A (V<sub>DS</sub> = 800 V)

![](_page_23_Figure_3.jpeg)

Figure 4.10. Switching Loss vs. Drain Current RH = RL =  $0.5 \Omega$  (V<sub>DS</sub> = 800 V)

![](_page_24_Figure_1.jpeg)

Figure 4.11. Eon Loss RH = RL =  $3.3 \Omega$  (V<sub>DS</sub> = 600 V)

![](_page_24_Figure_3.jpeg)

Figure 4.12. Switching Loss vs. Drain Current RH = RL = 3.3  $\Omega$  (V<sub>DS</sub> = 800 V)

![](_page_25_Figure_1.jpeg)

Figure 4.13. Switching Loss vs. Drain Current RH = RL = 3.3 Ohm (V<sub>DS</sub> = 800 V)

![](_page_25_Figure_3.jpeg)

Figure 4.14. Switching Loss vs. Drain Current RH = RL = 3.3 Ohm (V<sub>DS</sub> = 800 V)

The following figures summarize total switching loss versus gate resistors at 600 V and 800 V, respectively. These switching loss results demonstrate the effect of different gate resistances on the switching losses and confirm that the Si828x gate driver circuit can drive the SiC FETs with a low, 0.5 gate resistor.

![](_page_26_Figure_1.jpeg)

Figure 4.15. Total Switching Loss vs. Rg (RH = RL),  $V_{DS}$  = 600 V

![](_page_26_Figure_3.jpeg)

Figure 4.16. Total Switching Loss vs. Rg (RH = RL),  $V_{DS}$  = 800 V

## 5. Conclusion

The above data demonstrate that the Skyworks Si828x gate driver circuits perform well with the Wolfspeed XM3 SiC FET module in critical characterization tests. The Si828x's DESAT protection circuit has a fast response time (less than 1 $\mu$ s) to minimize I<sub>DS</sub> peak current and power dissipation on the XM3 module and reliably protects it under repeated extreme shorted conditions. The Si828x's DESAT circuits also provide flexible control, so designers can set the response timing, soft shutdown timing, and voltage spike levels for optimized protection.

The Skyworks Si828x driver was tested with the Wolfspeed 1.2 kV, 450 A CAB450M12XM3 SiC module and demonstrated sufficient drive strength to switch the part quickly, minimizing switching loss. The switching loss data with Rg =  $0.5 \Omega$  looks similar to the switching loss in the CAB450M12XM3 data sheet. Furthermore, the Si828x demonstrated immunity to both crosstalk and high common-mode transients present in a hard-switched SiC FET topology, and the Miller Clamp and negative gate bias eliminated dv/dt-induced turn-on. The specific Skyworks drivers evaluated in this test were the Si8284 and the Si8285, but the entire Si828x series of drivers offers the same short-circuit protection and CMTI capabilities.

Together, Skyworks' Si828x family of drivers and Wolfspeed's XM3 SiC module tested in this report enable high-efficiency, robust power conversion.

![](_page_28_Picture_0.jpeg)

![](_page_28_Picture_1.jpeg)

![](_page_28_Picture_2.jpeg)

![](_page_28_Picture_3.jpeg)

Support & Resources skyworksinc.com/support

#### Copyright © 2022 Skyworks Solutions, Inc. All Rights Reserved.

Information in this document is provided in connection with Skyworks Solutions, Inc. ("Skyworks") products or services. These materials, including the information contained herein, are provided by Skyworks as a service to its customers and may be used for informational purposes only by the customer. Skyworks assumes no responsibility for errors or omissions in these materials or the information contained herein. Skyworks may change its documentation, products, services, specifications or product descriptions at any time, without notice. Skyworks makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Skyworks assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Skyworks products, information or materials, except as may be provided in Skyworks' Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. SKYWORKS DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. SKYWORKS SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Skyworks products are not intended for use in medical, lifesaving or life-sustaining applications, or other equipment in which the failure of the Skyworks products could lead to personal injury, death, physical or environmental damage. Skyworks customers using or selling Skyworks products for use in such applications do so at their own risk and agree to fully indemnify Skyworks for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Skyworks products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Skyworks assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Skyworks products outside of Skyworks' published specifications or parameters.

Skyworks, the Skyworks symbol, Sky5<sup>®</sup>, SkyOne<sup>®</sup>, SkyBlue<sup>™</sup>, Skyworks Green<sup>™</sup>, Clockbuilder<sup>®</sup>, DSPLL<sup>®</sup>, ISOmodem<sup>®</sup>, ProSLIC<sup>®</sup>, and SiPHY<sup>®</sup> are trademarks or registered trademarks of Skyworks Solutions, Inc. or its subsidiaries in the United States and other countries. Third-party brands and names are for identification purposes only and are the property of their respective owners. Additional information, including relevant terms and conditions, posted at www.skyworksinc.com, are incorporated by reference.

> Skyworks Solutions, Inc. | Nasdaq: SWKS | sales@skyworksinc.com | www.skyworksinc.com USA: 781-376-3000 | Asia: 886-2-2735 0399 | Europe: 33 (0)143548540