

Power Management for Integrated RF ICs

By Qui Luu

As more building blocks are added to a radio-frequency integrated circuit (RFIC), more sources of noise coupling arise, making power management increasingly important. This article describes how power-supply noise can affect the performance of RFICs. The [ADRF6820](#) quadrature demodulator with integrated phase-locked loop (PLL) and voltage-controlled oscillator (VCO) is used as an example, but the results are broadly applicable to other high-performance RFICs.

The power-supply noise can degrade linearity by creating mixing products in the demodulator and degrade phase noise in the PLL/VCO. A detailed power evaluation is accompanied by recommended power designs using low-dropout regulators (LDOs) and switching regulators.

With its dual supply and high level of RF integration, the ADRF6820 provides an ideal vehicle for discussion. It uses a similar active mixer core as the [ADL5380](#) quadrature demodulator and the identical PLL/VCO cores as the [ADRF6720](#), so the information presented can be applied to those components. In addition, the power-supply design can be applied to new designs requiring 3.3-V or 5.0-V supplies with similar power consumption.

The ADRF6820 quadrature demodulator and synthesizer, shown in Figure 1, is ideally suited for next-generation communication systems. The feature-rich device comprises a high-linearity broadband I/Q demodulator, an integrated fractional-N PLL, and a low-phase-noise multicore VCO. It also integrates a 2:1 RF switch, a tunable RF balun, a programmable RF attenuator, and two LDOs. The highly integrated RFIC is available in a 6-mm × 6-mm LFCSP package.

 


Figure 1. ADRF6820 simplified block diagram.

Power-Supply Sensitivities

The blocks most affected by power-supply noise are the mixer core and the synthesizer. Noise coupled into the mixer core creates unwanted products that degrade linearity and dynamic range. This is especially critical for a quadrature demodulator because the low-frequency mixing products fall within the band of interest. Similarly, power-supply noise can degrade the phase noise of the PLL/VCO. The effect of unwanted mixing products and degraded phase noise are common to most mixers and synthesizers, but the exact

level of degradation is determined by the architecture and layout of the chip. Understanding these power-supply sensitivities allows a more robust power design that optimizes performance and efficiency.

Quadrature Demodulator Sensitivities

The ADRF6820 uses a double-balanced [Gilbert cell](#) active mixer core, as shown in Figure 2. Double-balanced means that both the LO and RF ports are driven differentially.

 


Figure 2. Gilbert cell double-balanced active mixer.

After a filter rejects the high-order harmonics, the resulting mixer outputs are the sum and difference of the RF and LO inputs. The difference term, also called the IF frequency, lies within the band of interest, and is the desired signal. The sum term falls out of band and gets filtered.

$$V(t) = \frac{2V_{RF}}{\pi} [\cos(w_{RF}t - w_{LO}t) + \cos(w_{RF}t + w_{LO}t)]$$

Ideally, only the desired RF and LO signals are presented to the mixer core, but this is rarely the case. Power-supply noise can couple into the mixer inputs and manifest itself as mixing spurs. Depending on the source of the noise coupling, the relative amplitudes of the mixing spurs may vary. Figure 3 shows a sample mixer output spectrum and where the mixing products may reside due to power-supply-noise coupling. In the figure, CW corresponds to a continuous wave or sinusoidal signal that couples on to the power-supply rail. The noise may be the clock noise from a 600-kHz or 1.2-MHz switching regulator, for example. The power-supply noise can cause two different problems—if the noise couples to the mixer outputs, the CW tone will appear at the output with no frequency translation; if the coupling occurs at the mixer inputs, the CW tone will modulate the RF and LO signals, producing products at $IF \pm CW$.

 


Figure 3. Sample mixer output spectrum with power-supply noise coupling.

These mixing products can be close to the desired IF signal, so filtering them out becomes difficult, and dynamic range loss is inevitable. This is especially true for quadrature demodulators because their baseband is complex and centered around dc. The demodulation bandwidth of the ADRF6820 spans from dc to 600 MHz. If a switching regulator with noise at 1.2 MHz powers the mixer core, undesired mixing products will occur at $IF \pm 1.2$ MHz.

Frequency Synthesizer Sensitivities

The references provided at the end of the article offer valuable information on how power-supply noise affects integrated PLL and VCOs. The principles apply to other designs with the same architecture, but nonidentical designs will need their own power evaluation. For example, the integrated LDO on the ADRF6820's VCO power-supply offers more noise immunity than a PLL power-supply that does not use an integrated LDO.

ADRF6820 Power-Supply Domains and Current Consumption

To design the power-management solution, first examine the RFIC's power domains to determine which RF blocks are powered by which domain, the power consumption of each domain, the operational modes that affect the power consumption, and the power-supply rejection of each domain. Using this information, sensitivity data for the RFIC can be collected.

The major functional blocks of the ADRF6820 each have their own power pins. Two domains are powered from the 5-V supply. VPMX powers the mixer core, and VPRF powers the RF front-end and input switches. The remaining domains are powered from the 3.3-V supply. VPOS_DIG powers an integrated LDO, which outputs 2.5 V to power the SPI interface, the PLL's Σ - Δ modulator, and the synthesizer's FRAC/INT dividers. VPOS_PLL powers the PLL circuitry, including the reference input frequency (REFIN), phase-frequency detector (PFD), and the charge pump (CP). VPOS_LO1 and VPOS_LO2 power the LO path, including the baseband amplifier and dc bias reference. VPOS_VCO powers another integrated LDO, which outputs 2.8 V to power the multicore VCO. This LDO is important for minimizing the sensitivity to power-supply noise.

The ADRF6820 is configurable in several operational modes. It consumes less than 1.5 mW in normal operational mode with a 2850-MHz LO. Decreasing the bias current reduces both power consumption and performance. Increasing the mixer bias current makes the mixer core more linear and improves IIP3, but degrades the noise figure and increases power consumption. If noise figure is of key importance, the mixer bias current can be reduced, decreasing the noise within the mixer core and reducing power consumption. Similarly, the baseband amplifiers at the output have variable current drive capabilities for low impedance output loads. Low output impedance loads require higher current drive and consume more power. The data sheet provides tables showing power consumption for each of the operational modes.

Measurement Procedure and Results

Noise coupling on the power rail produces undesired tones at CW and $IF \pm CW$. To mimic this noise coupling, apply a CW tone to each power pin and measure the amplitude of the resulting mixing product relative to the input CW tone. Record this measurement as the power-supply rejection in dB. The power-supply rejection varies with frequency, so sweep the CW frequency from 30 kHz to 1 GHz to capture the behavior. The power-supply rejection over the band of interest determines whether filtering is required. The PSRR is calculated as:

$$CW\ PSRR\ in\ dB = \text{input CW amplitude (dBm)} - \text{measured CW feedthrough at I/Q output (dBm)}$$

$$(IF \pm CW)\ PSRR\ in\ dB = \text{input CW amplitude (dBm)} - \text{measured IF} \pm CW\ feedthrough\ at\ I/Q\ output\ (dBm)$$

$$(IF + CW)\ in\ dBm = (IF - CW)\ dBm, \text{ as CW tones modulated around the carrier have equal amplitudes.}$$

Lab Setup

Figure 4 shows the lab setup. Apply a 3.3-V or 5-V dc source to the network analyzer to produce a swept continuous sinusoidal signal with a 3.3-V or 5-V offset. Apply this signal to each of the power rails on the RFIC. Two signal generators provide the RF and LO input signals. Measure the output on a spectrum analyzer.

 


Figure 4. ADRF6820 PSRR measurement setup.

Measurement Procedure

The amplitude of the undesired mixing products depends on the chip's power-supply rejection, and the size and location of the decoupling capacitors on the evaluation board. Figure 5 shows the amplitude of the (IF + CW) tone at the output given a 0-dB sinusoidal signal on the power pin. With no decoupling capacitors, the amplitude of the undesired tone was between -70 dBc and -80 dBc. The data sheet recommends a 100-pF capacitor adjacent to the device on top of the board and a 0.1- μ F capacitor on the back. The resonance of these external decoupling capacitors can be seen in the graph. The transition at 16 MHz is due to the resonance of the 0.1 μ F capacitor with a 1-nH parasitic inductance. The transition at 356 MHz is due to the resonance of the 100-pF capacitor with 2 nH of parasitic inductance from both capacitors. The transition at 500 MHz is due to the resonance of the 100-pF capacitor with a 1-nH parasitic inductance.

 


Figure 5. Effects of decoupling capacitor resonance on IF \pm CW.

Results

The amplitudes of the interfering signal (CW) on the power-supply rail and the modulated signals (IF \pm CW) were measured at the baseband outputs. Noise was introduced to the power rail under test, while the other power supplies remained clear. Figure 6 shows the amplitude of the (IF \pm CW) tone when a 0-dB sinusoidal signal was injected on the power pin and swept from 30 kHz to 1 GHz. Figure 7 shows the feedthrough from the CW tone to the baseband outputs.

 


Figure 6. PSRR of the (IF \pm CW) tone.

 


Figure 7. PSRR of the CW tone.

Analysis

The plots provide invaluable data on the supply sensitivities at each power pin. VPOS_PLL has the worst power-supply rejection and is therefore the most sensitive power node. This power pin powers the PLL circuitry, including the reference input frequency, phase-frequency detector, and the charge pump. These sensitive function blocks determine the accuracy and phase performance of the LO signal, so any noise coupled on them propagates directly to the output.

Under the same reasoning, it can be argued that the VCO power-supply is also a critical node. The plots show that VPOS_VCO has much better rejection than VPOS_PLL. This is a result of the internal LDO that actually powers the VCO. The LDO isolates the VCO from noise on the external pin and also provides it with a fixed-noise spectral density. The PLL power supply has no LDO, making it the most sensitive power rail. Thus, isolating it from potential noise coupling is critical for optimal performance.

The PLL loop filter attenuates high CW frequencies, so the sensitivity on VPOS_PLL is poor at low frequencies and slowly improves as the frequency sweeps from 30 kHz to 1 GHz. At higher frequencies the amplitude of the interfering tone gets attenuated and the power level injected into the PLL is substantially lower. Thus, VPOS_PLL shows better high-frequency power-supply rejection than the other power domains. The loop filter components were configured for 20 kHz, as shown in Figure 8.

The power rails, listed from most sensitive to least sensitive, are: VPOS_PLL, VPOS_LO2, VPOS_VCO, VPOS_LO1, VPOS_DIG, VPMX, and VPRF.

 


Figure 8. PLL loop filter configured for a 20-kHz loop bandwidth.

Power-Supply Design

With a good understanding of the maximum power consumption of the ADRF6820 in its various modes and the sensitivity of each power domain, power-management solutions were designed using both switching regulators and LDOs to determine the feasibility of both power solutions. First, a 6-V source was regulated to 5 V and 3.3 V for the ADRF6820 power rails. Figure 9 shows the power design for the 5-V power-supply for VPMX and VPRF. The **ADP7104** CMOS LDO can deliver up to 500 mA load current. The **ADP2370** low quiescent current step-down (buck) switching regulator can operate at 1.2 MHz or 600 kHz. Additional filtering was added to the switching regulator output to

attenuate the switching noise. The ADP2370 can deliver up to 800 mA load current. The ADRF6820's 5-V rail can be sourced by either the ADP7104 or the ADP2370. Additional decoupling and filtering is applied to each power pin.

Figure 10 shows the 3.3-V power design. The source voltage is still 6.0 V, but an additional LDO steps the source down to an intermediate voltage before it gets regulated down to 3.3 V. The extra stage is required to reduce power loss, as a 6-V source regulated directly down to 3.3-V would operate at 55% maximum efficiency. An intermediate stage is not necessary for the switching regulator path because its pulse-width modulation (PWM) architecture minimizes power loss.

 


Figure 9. 5-V power design.

 


Figure 10. 3.3-V power design.

The 3.3-V design allowed for more experimentation. In addition to sourcing the 3.3-V rail with either an LDO or a switching regulator, the VPOS_PLL rail has additional LDO options and the VPOS_DIG rail has an optional isolated LDO. As the PLL power-supply is the most sensitive, three power solutions were tried, each with different output noise: the ADP151 3.3-V ultralow-noise CMOS LDO with 9 μ V rms output noise; the ADP7104 3.3-V low-noise CMOS LDO with 15 μ V rms output noise; and the ADP2370 3.3-V buck regulator. We want to determine the highest level of power-supply noise that will still maintain the required phase-noise performance. Is the highest performance, lowest noise LDO an absolute necessity?

The ADP121 3.3-V low-noise CMOS LDO was also tried on the VPOS_DIG power rail to determine if digital noise would affect performance. The digital power rail tends to be noisier than the analog supplies due to switching on the SPI interface. We want to determine if the digital 3.3-V power-supply will require its own LDO or if it can be coupled directly to the analog power-supply. The ADP121 was chosen as a low-cost solution.

 


Figure 11. Integrated phase noise using the ADP151 and ADP7104.

 


Figure 12. Integrated phase noise using the ADP151 and ADP2370.

Conclusions and Power Design Recommendations

For VPOS_PLL, the most sensitive power-supply rail, the low-cost ADP151 LDO achieves the same phase noise as the ADP7104 high-performance, low-noise LDO, as shown in Figure 11. Performance was degraded when the ADP2370 switching regulator was used, however, as shown in Figure 12. The noise hump is caused by the switching regulator, and can be seen on its output, as shown in Figure 13. Thus, VPOS_PLL can tolerate up to 15 μ V rms noise with no degradation in integrated phase noise, but a switching regulator cannot be used to power this pin. No benefit is obtained by using a higher performance, lower noise LDO.

Good phase-noise performance is maintained when either a switching regulator or an LDO powers the remaining supply rails, as shown in Figure 14. The 5-V power-supply pins, VMPX and VPRF, can both be tied together and sourced with a single supply. The 3.3-V power-supply pins, VPOS_LO1, VPOS_LO2, and VPOS_VCO, can also be tied together and sourced by a single supply. VPOS_DIG does not require an independent LDO and can be tied to the analog 3.3-V power-supply.

 


Figure 13. Output spectrum of the ADP2370.

 


Figure 14. Switcher vs. LDO noise figure.

With a 6-V source voltage, the recommended power-supply design, shown in Figure 15, includes the ADP7104 5.0-V and the ADP7104 3.3-V LDOs. This solution uses only LDOs because the source voltage is close to the required supply voltages. The power efficiency is acceptable, so the added cost of filtering components and switching regulators is unnecessary.

With a 12-V source, the recommended power-supply design, shown in Figure 16, includes two switching regulators and an LDO. The source voltage is much larger than the required supply voltages, so the switching regulators are used to improve power efficiency. All of the power pins except for the sensitive VPOS_PLL supply can be sourced from the switching regulators. Either the ADP7104 or ADP151 can be used for VPOS_PLL.

 


Figure 15. Recommended power-supply design for a 6-V source voltage.

 


Figure 16. Recommended power-supply design for a 12-V source voltage.



Qui Luu

Also by this Author

RF-to-Bits Solution Offers Precise Phase and Magnitude Data for Material Analysis

Volume 48, Number 4

Qui Luu [qui.luu@analog.com] is an RF applications engineer at Analog Devices since June 2000. Qui received her B.S.E.E. from Worcester Polytechnic Institute in Worcester, MA, in 2000 and her M.S.E.E. at Northeastern University in Boston, MA, in 2005.

References

Circuit Note CN0147. Powering a Fractional-N Voltage-Controlled Oscillator (VCO) with Low Noise LDO Regulators for Reduced Phase Noise. Analog Devices, Inc., 2010.

Collins, Ian. *Integrated PLLs and VCOs [Part 2]*. Radio-Electronics.com, Nov 2010.

Modulators/Demodulators

Linear Regulators

Switching Regulators