

# SEMICONDUCTORS

## MCU/MPU/DSP

Atmel	194, 195, 196, 197, 198, 199, 200
Blackhawk	201
Cyan	202
Cypress	203, 204, 205, 206, 207
Elprotronic	208
FDI	209
Freescale	210, 211, 212, 213, 214, 215, 216, 217, 218, 219, 220, 221
IAR Systems	222
Infineon	223
Keil	224
Luminary Micro	225
Microchip	226, 227, 228, 229, 230, 231
NEC	223
NXP	232, 233
Parallax	234
Ramtron	235
Silicon Labs	236, 237, 238, 239, 240
SST	241
STMicroelectronics	242, 243, 244
Spectrum Digital	245
Texas Instruments	246, 247, 248, 249, 250, 251
Zilog	252, 253, 254, 255, 256, 257, 258, 259

## Programmiers

B&K Precision	260
EETools	261
Xeltek	262

## Memory

Atmel	263, 264
ON Semiconductor	265, 266, 267
ISSI	268, 269
Microchip	270, 271
Ramtron	272, 273
Seiko	274
Spansion	275
SST	276, 277, 278
STMicroelectronics	279, 280

## Logic - Programmable

Actel	281, 282, 283
Lattice	284, 285, 286
STMicroelectronics	287

## Logic - Standard

Fairchild	288, 289, 290
NXP	291, 292, 293
ON Semiconductor	294, 295
STMicroelectronics	296
Texas Instruments	297, 298, 299, 300, 301, 302
Toshiba	303

## Analog ICs & Mixed Signal

Advanced Linear Devices (ALD)	304
Cirrus Logic	306, 307, 308
Diodes Inc/Zetex	309, 310
Exar	311, 312, 313, 314
Fairchild	315

Freescale	316
Hendon	317
Microchip	318
NXP	319, 320
NJR	321
ON Semiconductor	305, 322, 323
Pericom	324, 325
PLX Technology	326, 327
ROHM	328, 329
Silicon Labs	330
SMSC	331
STMicroelectronics	332, 333, 334, 335, 336
Supertex	337, 338, 339, 340
Teridian	341, 342
Texas Instruments	343, 344, 345, 346, 347, 348, 349, 350, 351, 352, 353, 354, 355, 356, 357, 358
THAT Corporation	359
Vishay/Siliconix	360, 361, 362
Wolfson	363

## Amplifier ICs

Advanced Linear Devices (ALD)	364
Avago	365
CEL	366, 367, 368
Fairchild	369
Microchip	370
NJR	371, 372
ON Semiconductor	373
STMicroelectronics	374, 375, 376, 377
Texas Instruments	378, 379, 380, 381, 382, 383, 384, 385, 386, 387
TriQuint - WJ	388

## Power Management

<b>Regulators, References and Comparators</b>	
Diodes Inc	389
Diodes Inc/Zetex	390
Enpirion	391
Exar	392
Fairchild	393, 394, 395, 396
Infineon	397
IXYS	398
Microchip	399, 400
NEC Electronics America	401, 402
ON Semiconductor	403, 404, 405, 406, 407, 408
Power Integration	409, 410
Seiko	411, 412, 413, 414, 415, 416
Silicon Labs	417
STMicroelectronics	418, 419, 420, 421, 422, 423, 424
Texas Instruments	425, 426, 427, 428, 429, 430, 431, 432, 433, 434, 435, 436, 437, 438, 439
Vishay/Siliconix	440

## Discrete Semiconductors

<b>Diodes and Rectifiers</b>	
Avago	441
Bourns	442
Central	443, 444

Comchip	445, 446, 447
Diodes Inc	448, 449, 450, 451, 452
Diodes Inc/Zetex	453
Eupec	454
Fairchild	455, 456, 457, 458, 459, 460
Infineon	461, 462
IXYS	463
MCC	464
NXP	465, 466
ON Semiconductor	467, 468, 469, 470
ROHM Semiconductor	471
STMicroelectronics	472
Toshiba	473
Vishay General Semiconductor	474, 475, 476, 477, 478
Vishay Semiconductor	479, 480, 481, 482, 483, 484, 485

## Transistors

CEL	486, 487
Central	488, 489
Diodes Inc	490
Diodes Inc/Zetex	491, 492, 493, 494
Fairchild	495, 496, 497, 498, 499
Infineon	500
NXP	501
ON Semiconductor	502, 503, 504, 505, 506
ROHM Semiconductor	507, 508, 509
STMicroelectronics	510, 511
Toshiba	512

## MOSFETs

Advanced Linear Devices (ALD)	513
Diodes Inc/Zetex	514, 515
Fairchild	516, 517, 518, 519
Infineon	520, 521, 522, 523, 524
ON Semiconductor	525, 526
STMicroelectronics	527, 528
Supertex	529, 530
Toshiba	531
Vishay Semiconductor	532, 533, 534, 535, 536
Vishay/Siliconix	537, 538, 539, 540, 541, 542, 543, 544

## Thyristors

Bourns	545, 546
Littelfuse	547, 548, 549, 550, 551
ON Semiconductor	552
STMicroelectronics	553, 554

## Transient Protection

Bourns	555
CMD	556, 557, 558
Fairchild	559
Littelfuse	560, 561, 562
ON Semiconductor	563
Tyco/Raychem	564
STMicroelectronics	565, 566
Vishay Semiconductor	567, 568
Vishay General Semiconductor	569, 570, 571, 572