

# SEMICONDUCTORS

## MCU/MPU/DSP

Atmel.....	194, 195, 196, 197, 198, 199, 200
Blackhawk.....	201
Cypress.....	202, 203, 204, 205
Energy Micro.....	206
Elprotronic.....	207
FDI.....	208
Freescale.....	209, 210, 211, 212, 213, 214, 215, 216, 217, 218, 219, 220, 221
IAR Systems.....	222
Keil.....	223
Code Red.....	224
Embedded Artists.....	224
Microchip.....	225, 226, 227, 228, 229
NXP.....	230, 231, 232
Parallax.....	233
Ramtron.....	234
Signum Systems.....	235
Silicon Labs.....	236, 237, 238, 239, 240, 241
STMicroelectronics.....	242, 243, 244
Spectrum Digital.....	245
Olিমex.....	246
Texas Instruments.....	247, 248, 249, 250, 251, 252, 253
Zilog.....	254, 255, 256, 257

## Programmiers

B&K Precision.....	258
EETools.....	259
Xeltek.....	259, 260

## Memory

Apacer.....	261
Atmel.....	262
Cypress.....	263, 264, 265
Greenliant.....	266, 267
ISSI.....	268
Microchip.....	269, 270, 271, 272
ON Semiconductor.....	273, 274, 275
Ramtron.....	276, 277
Seiko.....	278
Spansion.....	279
STMicroelectronics.....	280, 281

## Logic - Programmable

Lattice.....	282, 283, 284
Microsemi.....	285, 286, 287

## Logic - Standard

Fairchild.....	288, 289
NXP.....	290, 291, 292, 293, 294
ON Semiconductor.....	295, 296
STMicroelectronics.....	297
Diodes Inc.....	297
Texas Instruments.....	298, 299, 300, 301, 302, 303, 304

## Analog ICs and Mixed Signal

Advanced Linear Devices (ALD).....	305
Arctic Silicon Devices.....	306
Cirrus Logic.....	307, 308, 309
Cypress.....	310, 311
Diodes Inc/Zetex.....	312, 313
Exar.....	314, 315, 316, 317
Fairchild.....	318

Freescale.....	319
Kionix.....	320
Maxim.....	321, 322, 323, 324, 325, 326, 327, 328, 329, 330, 331, 332, 333, 334, 335, 336, 337, 338, 339, 340, 341, 342
Microchip.....	343, 344
NXP.....	345, 346, 347, 348, 349
ON Semiconductor.....	350, 351, 352
Pericom.....	353, 354
PLX Technology.....	355, 356
ROHM Semiconductor.....	357, 358
Silicon Labs.....	359, 360
SMSC.....	361
STMicroelectronics.....	362, 363, 364, 365, 366
Supertex.....	367, 368, 369
Teridian.....	370, 371
Texas Instruments.....	372, 373, 374, 375, 376, 377, 378, 379, 380, 381, 382, 383, 384, 385, 386
THAT Corporation.....	387
Vishay/Siliconix.....	388, 389, 390
Wolfson.....	391

## Amplifier ICs

Advanced Linear Devices (ALD).....	392
Avago.....	393
Renesas/CEL.....	394, 395, 396
Fairchild.....	397
Infinion.....	397
Maxim.....	398, 399, 400
Microchip.....	401
NJR.....	402
ON Semiconductor.....	403
STMicroelectronics.....	404, 405, 406
Texas Instruments.....	407, 408, 409, 410, 411, 412, 413, 414, 415, 416, 417, 418
TriQuint.....	419

## Power Management

Diodes Inc.....	420
Diodes Inc/Zetex.....	421
Enpirion.....	422
Exar.....	423
Fairchild.....	424, 425, 426, 427
Infinion.....	428
Maxim.....	429, 430, 431, 432, 433, 434, 435, 436, 437, 438, 439, 440
Microchip.....	441, 442
ON Semiconductor.....	443, 444, 445, 446, 447, 448
Power Integration.....	449, 450, 451
Seiko.....	452, 453, 454, 455, 456
Silicon Labs.....	457, 458
STMicroelectronics.....	459, 460, 461, 462, 463, 464, 465
Texas Instruments.....	466, 467, 468, 469, 470, 471, 472, 473, 474, 475, 476, 477, 478, 479, 480, 481, 482, 483, 484
Vishay/Siliconix.....	485

## Discrete Semiconductor

### Diodes and Rectifiers

Avago.....	486
Bourns.....	487
Central.....	488, 489
Comchip.....	490, 491, 492

Diodes Inc.....	493, 494, 495, 496, 497, 498
Diodes Inc/Zetex.....	499
Eupec.....	500
Fairchild.....	501, 502, 503, 504, 505
Genesic.....	506, 507
Infinion.....	508
IXYS.....	510
MCC.....	511
NXP.....	512, 513
ON Semiconductor.....	514, 515, 516, 517
Qsped.....	518
Rectron.....	519
ROHM Semiconductor.....	520
STMicroelectronics.....	521, 522
Toshiba.....	523
Vishay General Semiconductor.....	524, 525, 526, 527
Vishay Semiconductor.....	528, 529, 530, 531, 532, 533

## Transistors

Renesas/CEL.....	534, 535
Central.....	536, 537
Diodes Inc.....	538
Diodes Inc/Zetex.....	539, 540, 541
Fairchild.....	542, 543, 544, 545, 546
Infinion.....	547, 548
NXP.....	549
ON Semiconductor.....	550, 551, 552, 553, 554
ROHM Semiconductor.....	555, 556
STMicroelectronics.....	557, 558
Toshiba.....	559

## MOSFETs

Advanced Linear Devices (ALD).....	560
Diodes Inc/Zetex.....	561, 562
Fairchild.....	563, 564, 565, 566
Infinion.....	567, 568, 569, 570
NXP.....	571
ON Semiconductor.....	572, 573
ROHM Semiconductor.....	574
STMicroelectronics.....	575, 576, 577, 578, 579
Supertex.....	580, 581
Texas Instruments.....	582
Toshiba.....	583
Vishay Semiconductor.....	584, 585, 586, 587, 588
Vishay/Siliconix.....	589, 590, 591, 592, 593, 594, 595, 596, 597, 598

## Thyristors

Bourns.....	597
Littlefuse.....	598, 599, 600, 601
ON Semiconductor.....	602
STMicroelectronics.....	603, 604

## Transient Protection

Bourns.....	605, 606, 607, 608, 609, 610
CMD.....	611, 612, 613
Fairchild.....	614
Littlefuse.....	615, 616, 617, 618
NXP.....	619
ON Semiconductor.....	620
STMicroelectronics.....	621, 622, 623
Texas Instruments.....	624
Vishay Semiconductor.....	625, 626
Vishay General Semiconductor.....	627, 628