

How to Make a Pogo Pin Test Jig

Created by Tyler Cooper



https://learn.adafruit.com/how-to-make-a-pogo-pin-test-jig

Last updated on 2021-11-15 05:53:04 PM EST

Table of Contents

Overview	3
Preparation	3
Arduino Shield Jigs	5
The Code	8
Testing	9
Advanced Pogo Jigs	10
Support Forums	11

Overview




If you end up buying a pick and place to assemble PCBs (or even if you're doing it by hand) you'll need to test out your boards! If you have an assembler do it for you, its still probably a good idea to have a jig you can give them. A good jig will tell you whats going right and whats going wrong.

In this tutorial I will show how I designed a very basic jig with a "tested good" audible indicator. The board its testing is very simple but the basic premise can be expanded to large projects with ease.

Preparation

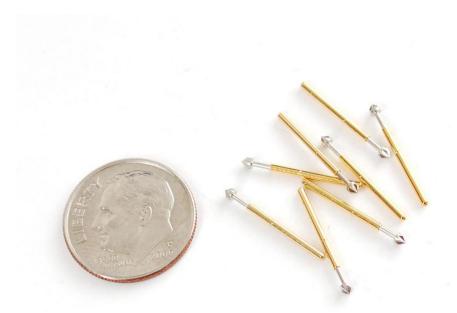I like to use a victim PCB to make jigs - FR4 is strong and you already have a template. You'll also need some standoffs and some pogo pins.



The spring-loaded ('pogo') pins I prefer are about 0.5" long and have a spear point. They also fit snugly into 'standard' 0.035" (0.9mm) drill holes so they are easy to insert and stand up straight. We now carry these pogo pins in the Adafruit shop! (http:// adafru.it/394) They're called "P75-LM" type, you can also pick them up on ebay. I don't use the socket holders because - well - I dont. But if you're building something that will be used for a long time by clumsy people its probably a good idea.

Test Centers - 75mil (1.91mm) 測試中心能 - 75mil (1.91mm)		Test Center 测试中心】	s - 75mil (1.91mm) § - 75mil (1.91mm)
Tip Style (1) 138 82) Fish Fish Fish Fish	0127 P75-T12 0127 0127		Series PL75
R75CR R75CRW	875-WW L=200mm 技術规格簡介	RLTS-VEC Technical Specifications	技術規格简介
Notestmended Maissime Content: 1.9 Strain (75mi) Current Raing: 3: and, continuous Careford Rainstone: 5:0 millionm Recording Halle Size: 4: 3:30mil Strain (75millionm) Regress grave 1:30 (40millionm) Segress grave 1:13 (40millionm) Careford Rainstone 5 milliong (40millionm) Careford Rainstone 5 milliong (40millionm) Segress grave 1:13 (40millionm) Careford Rainstone 5 milliong (40millionm)	重結果用約 長小信令(次):1.91mm(75mi) 鉄営電波:3.92%;通過 鉄営電波:5.92%;通過 柴菜用型:3.25mm 縦営電算:1.35g(Aox) 建設(方):1.35g(Aox) 建設(方):1.35g(Aox) 建設(方):1.55g(Aox) 建設(方):1.55g(Aox) 建設(方):1.55g(Aox) 建設(方):1.55g(Aox) 建築(方):1.55g(Aox) 建築(方):1.55g(Aox) (Aox):1.55g(Aox) (Ao	Russemented 1.9 fram (75ral) Current Rafing 1.8 area, continuous Control Rafing 1.3 area, continuous Mounting Intels Ear. 1.0 millioma Mounting Intels Ear. 1.0 millioma Seriel grave 1.1 Milliona Seriel grave 1.1 Milliona Concestions 1.1 Milliona Seriel grave 1.1 Milliona Seriel grave 1.1 Milliona Seriel grave 1.1 Milliona Seriel grave 1.1 Milliona	#44年月前 最小量中心部:191mm (75mi) 新工業業 新工業業 第二、32元法、道轄 新工業業 支援乳産 1132 (40x) 建築力工 1132 (40x) 建築力工 1132 (40x) 建築力工 1132 (40x) 建築力工 1132 (40x) 建築力工 1132 (40x) 建築力工 1132 (40x) 1132 (40x)
Materials	材料	Materials	材料
Recepted Phosphor Brows or Brass, Gold Plated Central Same, Gold Plated Spring Statistics Section Wire Music Wire, Gold Plated Spring Full-Head Benjium Cooper or Migh Carbon Steel, Rhodium Plated Over Nickel Order Nickel Over Nickel Preducer	田田市 研究成为明、数金 後期間 東京、数金 第 項 不明明明成功功。数金 升 身 研究就明成用效识、数金	Neosphol: :Procephol: Binnan or Binsis, Guld Plated Cented from: Binsis, Guld Plated Spring: Munic Wine or Stammer Stated Wine Guld Plated Planger: :Pul-Hard Bingthill Topping or or High Carloo Binel, Rodium Plated Over Minolain or Gala Plated Over Noisel) Poleto Over Noisel)	推销客。获取式关系。重全 接销局 关系。重全 弹 援 等线或不禁模线。重全 杆 身:使知道的或是收制。就上就就 该可说上就会)

See above for a handy reference diagram for the kinds of heads you can get!

This board already has 4 x 2-56 sized mounting holes so its easy to attach standoffs.



Choose the standoffs so that the tips of the pogo pins are above the standoff part but below the end of the screw.



Arduino Shield Jigs


I will be using <u>an Arduino to make this jig</u> (https://adafru.it/aIH). Arduinos are very standard, easy to power and are a breeze for short projects like this. You'll also want a proto shield PCB (https://adafru.it/aIH)

I think I'll put the victim...like this!




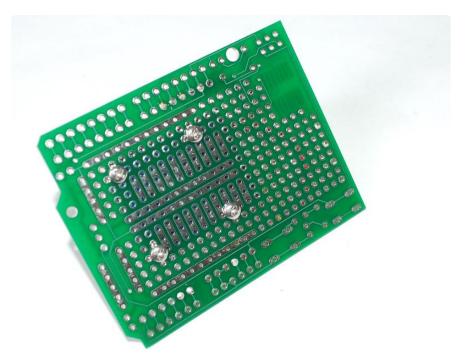Mark and drill the mounting holes - four in this case. Luckily (or on purpose???) I placed the mounting holes on 0.1" boundaries.






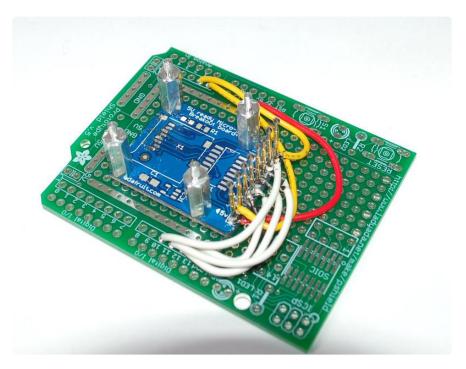Solder wires from each pogo pin to a matching pin on the shield. For this SD card interface I connected the SPI pins to the SPI port. Then the output of the 3.3v regulator goes to an analog pin. I also connected the card detect pin up so I can tell when a board is being tested.



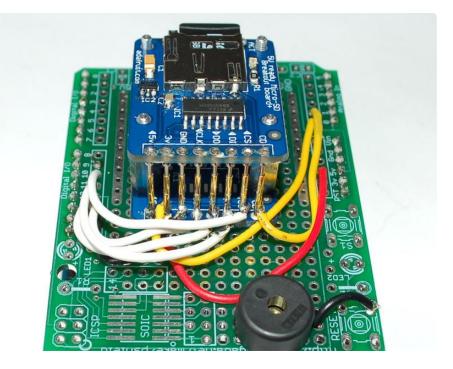A piezo buzzer is connected to pin #9 (underneath the PCB).



The Code

The code for the project is below and available on GitHub.

See the files for this project on GitHub


https://adafru.it/Euf

```
SD card breakout tester!
 Uses fat16lib's fantastic FAT library
 tests:
 1. CD pin works (goes low when card inserted)
 2. 3.3V LDO output is in proper range
 3. Can communicate with card
 */
#include <SD.h>
Sd2Card card;
#define CD 15 // A1 (D15) -> CardDetect
#define LDO 0 // analog 0
  bid setup() {
    // initialize the digital pin as an output:
void setup()
  Serial.begin(9600);
 digitalWrite(CD, HIGH); // pull up on CD
}
void loop()
{
  Serial.println("waiting for SD card detect");
```

```
while (digitalRead(CD)) {
   Serial.print('.');
  delay(100);
  }
  Serial.println("Detected Card!");
  // first check 3.3V regulator
  int a = analogRead(LD0);
  if ((a > 710) || (a < 650)) {</pre>
    // LDO not in the right range
    Serial.println(a);
    return;
  }
  Serial.println("3.3V LDO ok");
  // try to talk to the card
  uint8 t r = card.init(1);
  if (!r) {
    // failed to talk to SD card :(
    Serial.println(r, DEC);
    return;
  }
  Serial.println("Card interface ok");
  // beep to indicate all is good
  tone(9, 4000, 500);
  delay(1000);
}
```

Testing

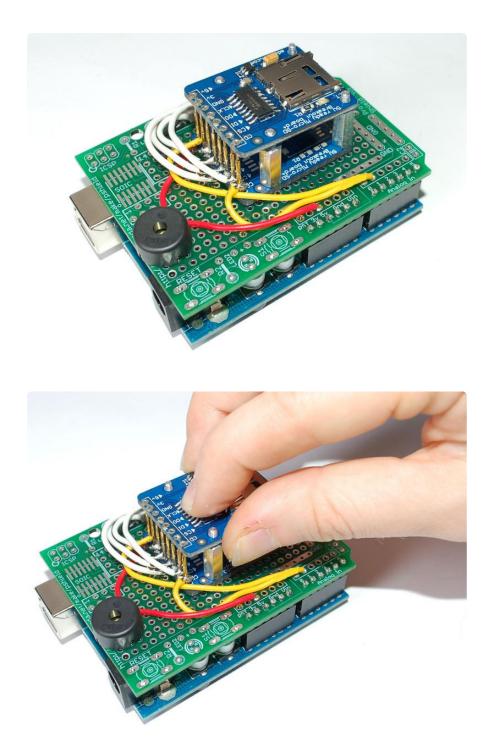Now the fun part! When a board is ready to test, insert a uSD card, and simply slip it into the orienting 'registration' standoffs and press down to make contact with the pogo pins. The Arduino will automatically detect when the CD pin is shorted to ground (good) and begin the test procedure. If all is good, it will beep!



Beep!

Advanced Pogo Jigs

For more complicated projects, you may need to have a complicated testing procedure in which case we can make multi-step testers that also keep the PCB held down with little ears!



(We totally saw this and stole the idea from someone online but we can't find the link anymore, sorry!)

The plastic pieces hold down the PCB against the pogo bed. This tester, when used with a little batch script, performs the following test:

- 1. Reprograms the board's fuses and flash with a bootloader (via the ISP port). For this part we're using the Arduino as an ISP programmer (there's a sketch that does this)
- 2. The computer then bootloads (via USB) a pin-by-pin testing program
- 3. Once the board indicates the test completed, the computer erases the testing program

Support Forums

Support Forums (https://adafru.it/forums)

Mouser Electronics

Authorized Distributor

Click to View Pricing, Inventory, Delivery & Lifecycle Information:

Adafruit: 394